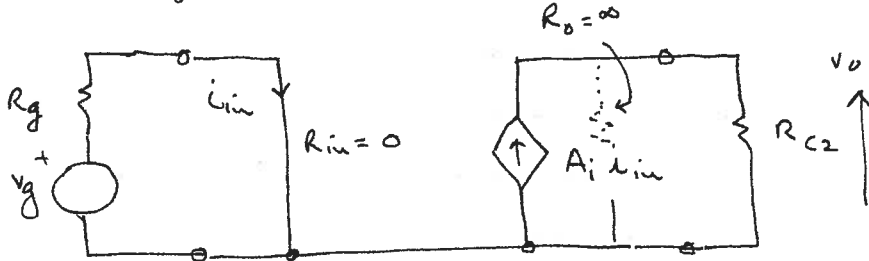


Solutions to Problems: II

2. Feedback is ∞ w/o R_f ; current sensing at o/p } \rightarrow amp tends to
current summing at i/p } ideal current amp
with $R_{in} = 0$; $R_o = \infty$


\therefore Replace by equivalent ckt



$$A_i = \frac{1}{\beta_i} \quad \text{if loop gain } A_i \beta_i \gg 1$$

$$V_o = R_{c2} \cdot A_i \cdot i_{in}; \quad i_{in} = \frac{V_g}{R_g}$$

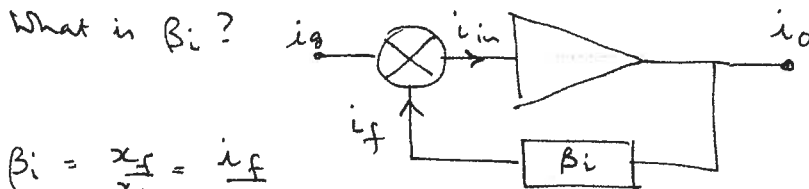
$$\therefore \frac{V_o}{V_g} = \frac{R_{c2} A_i}{R_g}$$



$$\beta_i = \frac{x_f}{x_o} = \frac{i_f}{i_o}$$

in this case.

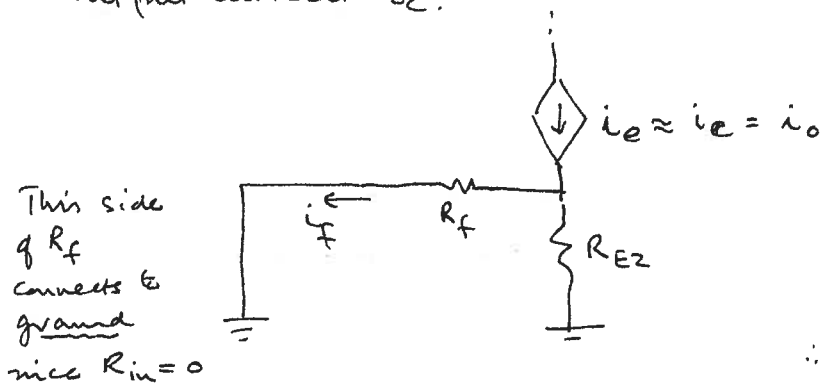Since R_f is actually sensing voltage at emitter of last stage TX, then really sensing emitter current of TX not the collector current which flows thro' load R_{c2} . BUT since $i_c \approx i_e$ to within 1% for TXs with current gain $\beta_{fe} \gg 100$, then can say we are sensing output current i_c .



$$\therefore \beta_i = \frac{i_f}{i_o} = \frac{R_{E2}}{R_{E2} + R_f} \quad \text{by current division}$$

$$\therefore A_i = \frac{1}{\beta_i} = \frac{R_{E2} + R_f}{R_{E2}}$$

$$\therefore \text{so } \frac{V_o}{V_g} = \frac{R_{c2}}{R_g} \cdot \frac{R_f + R_{E2}}{R_{E2}}$$