


Part 20: Effect of feedback on distortion

Negative feedback can reduce the amount of distortion produced by an amplifier.

- 1) What is **distortion**? When output is not a magnified, but otherwise exact copy of input.
- 2) Why does negative feedback affect distortion?

DIFFICULT to explain! – we look at examples. First, look at the Voltage Transfer Curve (VTC) of an amp.


For LINEAR amp, VTC is

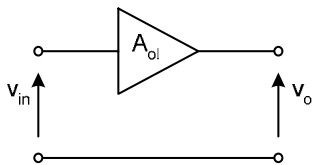



VTC \equiv graph of v_o vs v_{in}

Real amps only approx linear because:


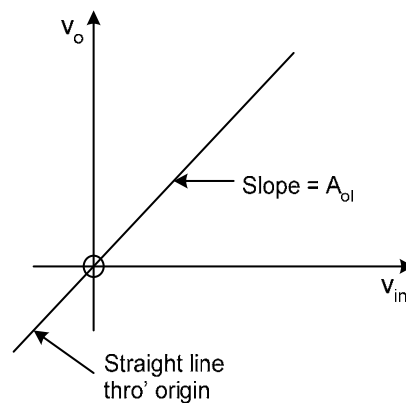
1. Transistors are not very linear devices
2. Output voltage swing is limited by supply rails



VTC of a **real** op-amp looks like

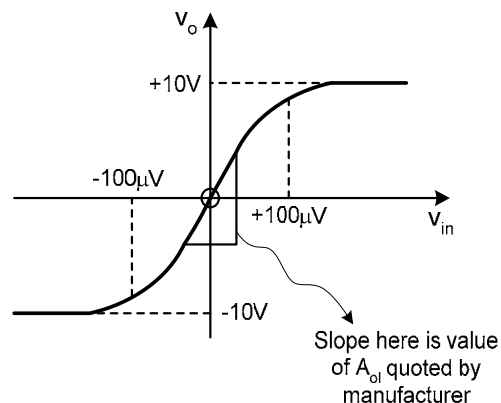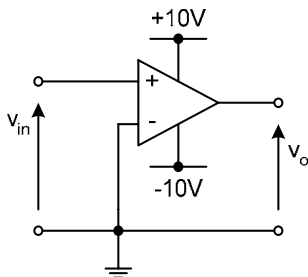

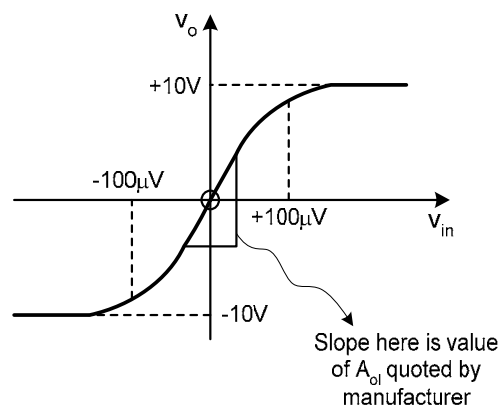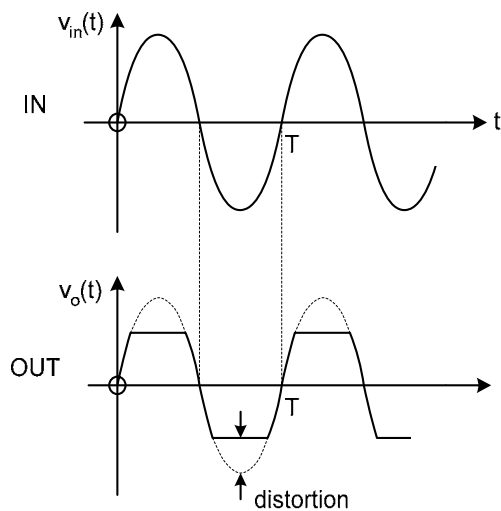For this op-amp, if v_{in} is a sinewave, output will be distorted – having flattened peaks



We should now define gain A_{ol} as


$$A_{ol} = \frac{dv_o}{dv_{in}} \quad - \quad \text{ie as slope of } v_o \text{ vs } v_{in} \text{ curve}$$

- $\therefore A_{ol}$ varies with value of v_{in}


For a real op-amp, A_{ol} then varies as

If we use this op-amp with feedback then since
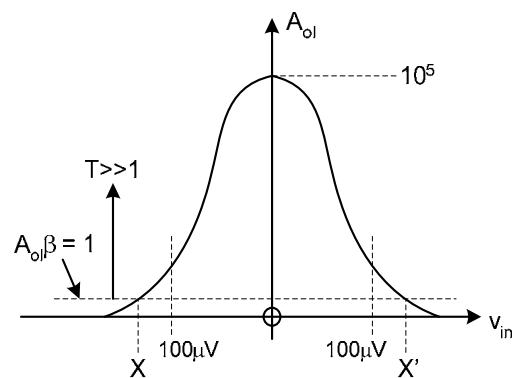
$$A_f \cong \frac{1}{\beta} \quad \text{provided } T \gg 1 \text{ (ie } A_{ol} \beta \gg 1)$$



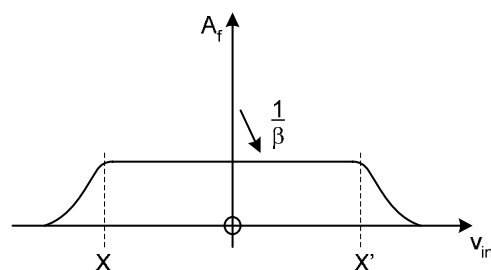Then A_f is **determined** by β in spite of variation of A_{ol} away from origin – we can plot A_f vs v_{in}



So provided, output is not too close to supply rails, distortion is much less (by a factor of $1 + T!$) – gain A_f is **independent** of v_{in} until v_{in} close to X or X'.

Another example

The transistors constitute a class B 'push-pull' power amplifier.

During the positive half cycle: Q_2 is OFF; Q_1 is ON


Provided $v_{oa} > 0.7V$

then output **follows** input ie $v_o = v_{oa} - 0.7$

During $-ve$ half cycle, Q_1 is OFF;

Q_2 is ON provided $v_{oa} < -0.7V$

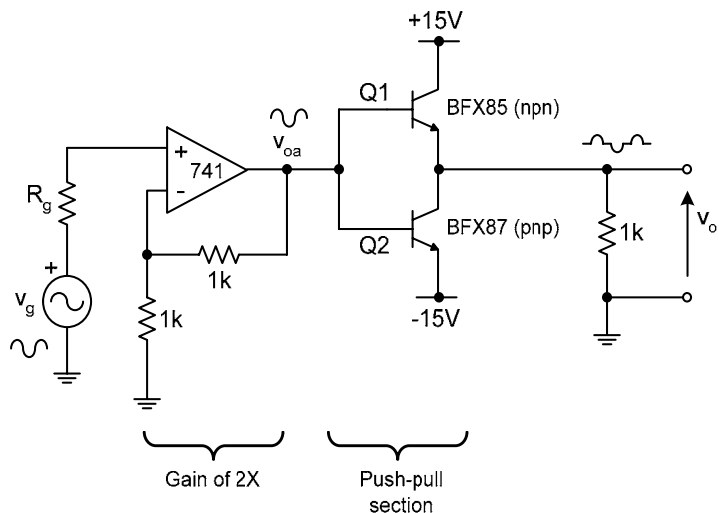
output follows input ie. $v_o = v_{oa} + 0.7V$




When $-0.7V < v_{oa} < +0.7V$
THERE IS NO OUTPUT

- both transistors are OFF
- we get **“Cross-over Distortion”**.


So we expect (see opposite)

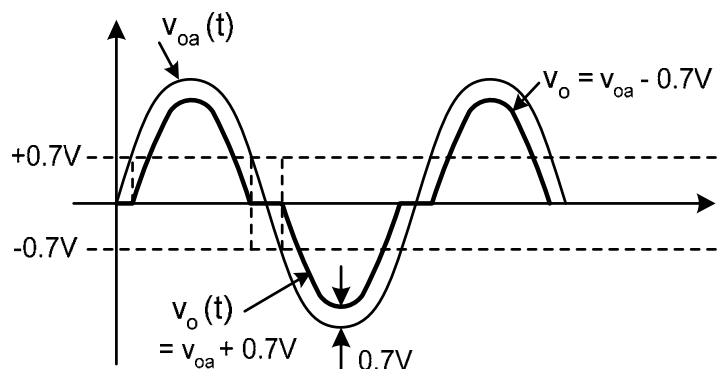

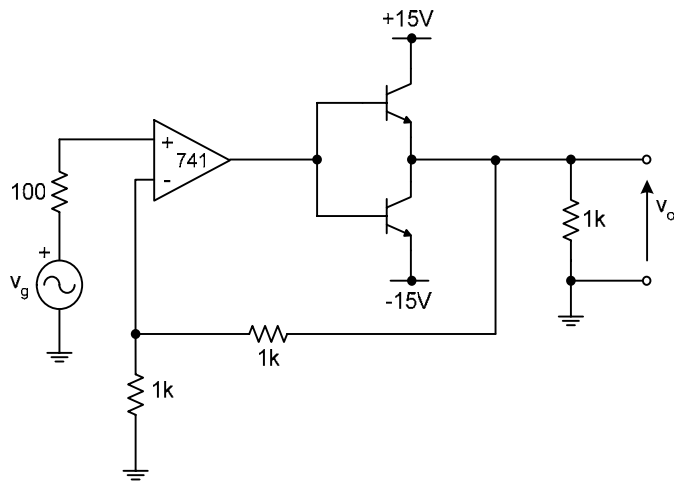BUT if we reconnect amplifier, so that push-pull circuit is **within** feedback loop:




Something almost magical happens!

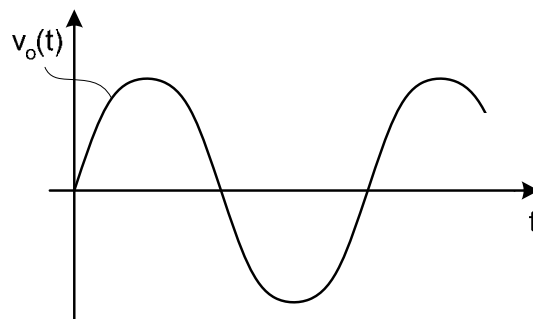

- output practically undistorted!

For this reason, look at op-amp output

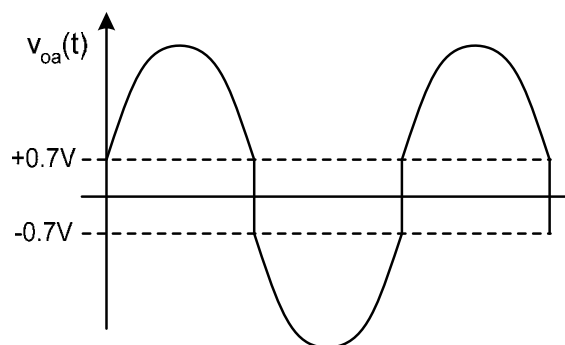

-output jumps between $-0.7V$ & $+0.7V$ levels to force the push-pull amplifier through its “dead band” quickly. Input to push-pull is pre-distorted in order to compensate for the distortion produced by the push-pull. Not really magic – but a pretty smart idea...beat nature at its own game..