

## PART 21: Some Op-amp limitations

Although op-amps with negative feedback operate in a practically ideal way, op-amps do suffer from some "non-idealities" or imperfections.

### Slew-rate limit

This relates to the ability of the op-amp to respond to a signal; that is, it relates to the **transient response** of the opamp.

Consider a test set-up with a unity gain op-amp circuit subject to application of a large signal – a 5V voltage step.

The output cannot instantly respond to such a signal. Indeed the input of the op-amp is over-driven into a 'saturated' mode (recall the transfer characteristic of the op-amp.) We recall the response of a first order circuit to such a response (see Part 9) to be exponential in nature. It turns out however, that op-amps respond in a different manner.

The transient response of an op-amp is in fact **linear** and the gradient is referred to as the **slew rate**. Note that such a response is obtained when a capacitor is charged by a constant current. The capacitor in this case is the large Miller compensation one (C) – see the 741 schematic circuit - the constant current (I) is provided by the current mirror bias circuit at the saturated input stage. Thus we can write:


$$SR \equiv \frac{dV_o}{dt} = \frac{I}{C}$$

For the 741 op-amp  $C = 30\text{pF}$  and  $I \sim 19\mu\text{A}$  giving a SR value of about  $0.6\text{V}/\mu\text{s}$ .

Other op-amps have better SRs – up to  $10\text{V}/\mu\text{s}$

SR depends on both amplitude and frequency

 SR distortion will be apparent from the output waveform



Consider a sine-wave input:  $V_i = V_{mi} \sin(\omega t)$

$$\text{Then } SR = \frac{dV_o}{dt} = \omega V_{mo} \cos(\omega t) \text{ and } SR = \omega V_{mo} = 2\pi f V_{mo} \quad (V_{mo} = \text{Gain} * V_{mi})$$

As long as this value ( $\omega V_{mo}$ ) is less than the SR limit, the output can follow the input.

**Example:** Assume a 741 with the input amplitude such that the output is the same as the power supply value (10V say), then  $V_m = 10\text{V}$ .  $SR = 0$ .

Equate to slew rate:  $\omega V_m = 0.6\text{V}/\mu\text{s}$  that is,  $f = \frac{0.6}{2\pi \times 10^{-6}} \frac{1}{10} = 9.6\text{kHz}$  for the slew rate limited frequency.

Higher frequency signals would be limited and distorted as in the diagram above.


**Exercise:** An operation amplifier with a slew-rate limit of  $1\text{V}/\mu\text{s}$ , is required to amplify a sinusoidal  $100\text{kHz}$  signal. Calculate the maximum amplitude of the output voltage that can be achieved without distortion.

**Solution:** Slew rate  $= dv_o/dt = 1\text{V}/\mu\text{s}$ . For a sinusoidal signal,  $v(t) = V_o \sin(\omega t)$ ;  $dv_o/dt = V_o \omega \cos(\omega t) = V_o \omega$  (maximum)

for a signal frequency of  $100\text{kHz}$ , then  $10^6 = V_o \times 2 \times \pi \times 10^5$  So  $V_o = 1.6$

## The Voltage Offset

Consider:

 


Here  $V_p = V_n = 0$  (tied to ground)

So **ideally** we expect:  $V_o = A_{ol}[V_p - V_n] \equiv 0$

In **practice**, find  $V_o \neq 0$

 
Due to **imbalance** between input stages of op-amp which process  $V_p$  and  $V_n$ , the VOLTAGE TRANSFER CURVE (VTC) for a real op amp might look like:



There is a **shift** (can be to the left OR right) of the VTC away from the origin – called the “input offset voltage”,  $V_{os}$

We can therefore **model** a real op-amp as

 NB  $V_{os}$  is a DC source – always connected to positive (+ve) input by convention, with polarity shown. But note  $V_{os}$  is equally likely to be positive or negative!



The manufacturer usually gives **magnitude** of  $V_{os}$  eg for 741C,  $V_{os} = 2\text{mV}$  typical,  $6\text{mV}$  max. This means ~50% of 741C's tested have  $V_{os}$  between  $-2\text{mV}$  to  $+2\text{mV}$ , but all have  $V_{os}$  between  $-6\text{mV}$  and  $+6\text{mV}$ .


### Errors caused by $V_{os}$


For the non-inverting amp:

We first suppress  $V_g$

To allow us to concentrate on the effect of  $V_{os}$

Replacing real op-amp by its model gives

 

 

Which shows that the output is

$$V_o = \left[ \frac{R_1 + R_2}{R_1} \right] \times V_{os}$$

↑  
Non-inverting gain


If gain is small, so is output offset  $V_o$ ; but if  $R_2 = 10^3 R_1$ , for example, so that gain is  $\sim 1000$ , then  $V_o$  becomes  $\pm 2V$  typical,  $\pm 6V$  maximum for a 741C, **not a small error!**

### The Current Offset


It is always possible by careful selection to find an op-amp with  $V_{os} \approx 0$ . However even this op-amp would suffer from offset problems – but due to **current offsets**.

Suppose, we take an op-amp with  $V_{os} = 0$  and build the following circuit:

 Then, **because input transistors in op-amp MUST be provided with base current in order to operate** -  $I_{Bp}$  &  $I_{Bn}$  - then a voltage is generated across the  $1M\Omega$  resistor which acts as an input to the op-amp, and so it is amplified to give an output,  $V_o$ .




 We might hope to cure this by putting **two** equal resistors in circuit to restore the balance.



These currents are particularly troublesome because they are temperature dependent – the output voltage drifts.

 The effect can be significantly reduced if the circuit is arranged to present the same resistance to both input terminals, for example, in the inverting op-amp circuit, always make  $R_3 = R_1 // R_2$ . (This will be explored further in the next section.)



BUT this only works if  $I_{Bp} = I_{Bn}$  which is rarely the case!

The manufacturer, after measuring a large no. of samples, gives us the average base current


$$I_B = \frac{I_{Bp} + I_{Bn}}{2} \text{ which is called the 'input bias current' on data sheets.}$$

AND they give us the magnitude of the difference between  $I_{Bp}$  &  $I_{Bn}$

ie.  $I_{os} = |I_{Bp} - I_{Bn}| = \text{'input offset current'}$

N.B.  $I_B$  can be either into op-amp or out of op-amp depending on whether input stage is constructed with npn or pnp transistors:

 **For a 741C:**  $I_B = 80 \text{ nA typical}, 500 \text{ nA max}$   
 $I_{os} = 20 \text{ nA typical}, 200 \text{ nA max}$



In the WORST possible case, this means


Either  $I_{BP} = 600 \text{ nA}, I_{BN} = 400 \text{ nA}$  Or  $I_{BP} = 400 \text{ nA}, I_{BN} = 600 \text{ nA}$

Summarise this by saying that in all cases  $I_B - \frac{I_{os}}{2} < I_{BP} < I_B + \frac{I_{os}}{2}$  AND  $I_B - \frac{I_{os}}{2} < I_{Bn} < I_B + \frac{I_{os}}{2}$
 
### Model of a Real Op-Amp including both Voltage and Current offsets

We model current offsets by CURRENT sources:

With current sources of polarity shown, model is of an op-amp with npn input transistors.




### Example: calculation of output offset in general case

Find  $V_o$  for :-

When  $V_g = 0$  in WORST CASE


$R_1 = 45 \text{ k}\Omega; R_2 = 90 \text{ k}\Omega; R_3 = 10 \text{ k}\Omega$ , and

 $V_{os} = 6 \text{ mV}; I_B = 500 \text{ nA}, I_{os} = 200 \text{ nA}$  - all maximum values




## PREPARATION FOR CALCULATION

- suppress  $V_g$  ; insert model

 


**Solution** – using principle of superposition


**Effect of  $V_{os}$  alone**

 


**Effect of  $I_{Bp}$  alone**

 


 Replacing current source by a voltage source gives:-



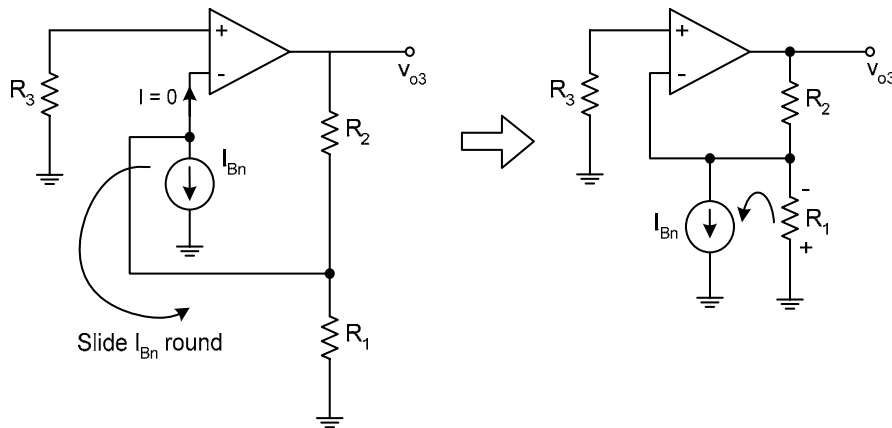**Effect of  $I_{Bn}$  alone**

Now a source transformation:

 

COMBINING contributions gives  $(V_o = V_{o1} + V_{o2} + V_{o3})$


$$\begin{aligned}
 V_o &= \left( \frac{R_1 + R_2}{R_1} \right) [V_{os} - I_{Bp} R_3] + \frac{R_2}{R_1} I_{Bn} R_1 \\
 &= \left( \frac{R_1 + R_2}{R_1} \right) [V_{os} - I_{BP} R_3] + \left( \frac{R_1 + R_2}{R_1} \right) \left( \frac{R_1}{R_1 + R_2} \right) R_2 I_{Bn} \\
 &= \left( \frac{R_1 + R_2}{R_1} \right) [V_{os} - I_{BP} R_3] + \left( \frac{R_1 + R_2}{R_1} \right) R_1 \parallel R_2 I_{Bn} \\
 &= \left( \frac{R_1 + R_2}{R_1} \right) [V_{os} - I_{BP} R_3 + R_1 \parallel R_2 I_{Bn}]
 \end{aligned}$$

NOTE we would get SAME OUTPUT from diagram shown opposite

Provided we take

$$V_{eff} = V_{os} - I_{BP} R_3 + R_1 \parallel R_2 I_{Bn}$$

 = effective input offset voltage – for this amplifier circuit



### CALCULATION OF VALUE OF $V_o$ IN WORST CASE

$$\text{Gain} = \frac{R_1 + R_2}{R_1} = \frac{45k + 90k}{45k} = 3$$

$$R_1 \parallel R_2 = 45k \parallel 90k = 30k \quad \text{From data sheet: } -6mV < V_{os} < 6mV \quad \text{maximum range}$$

$$\text{And since } I_B - \frac{I_{os}}{2} < \left\{ \frac{I_{BP}}{I_{BN}} \right\} < I_B + \frac{I_{os}}{2}, \quad \text{Then } 400nA < \left\{ \frac{I_{BP}}{I_{BN}} \right\} < 600nA$$

$$\text{Find } V_{eff} \text{ first (ie eqn *)}: \quad 30k \times 400nA < R_1 \parallel R_2 I_{Bn} < 30k \times 600nA = 18mV$$

$$(\text{= } 12mV)$$

$$10k \times 400nA < R_3 I_{Bp} < 10k \times 600nA = 6mV$$

$$(\text{= } 4mV)$$


**Combine graphically Draw ranges of each component**

MAX NEG value of  $V_{eff}$  when each component has max neg. value

$$\therefore \text{Max.neg. } V_{eff} = -6mV + 12mV - 6mV = 0$$

MAX POS value of  $V_{eff}$  when each component has max positive value
 
$$\begin{aligned} \text{So max. possible } V_{eff} &= +6mV + 18mV - 4mV \\ &= +20mV \end{aligned}$$




∴ In **worst case**,  $V_o$  lies in range

$$0 \leq V_o \leq 3 \times 20\text{mV}$$

$$\text{ie } 0 \leq V_o \leq 60\text{mV}$$

**MOST LIKELY** value of  $V_o$  is mid-way through

 
this range ie  $V_o$  (max probable) = 30mV



NB If we can adjust  $R_3$ , then chose

$$R_3 = R_1 \parallel R_2$$

 Since in this case range pattern is symmetrical about zero voltage point



$$\text{Min } V_{eff} = -18\text{mV} - 6\text{mV} + 12\text{mV} = -12\text{mV}$$

$$\text{Max } V_{eff} = -12\text{mV} + 6\text{mV} + 18\text{mV} = +12\text{mV}$$


So that output offset voltage is:  $-36\text{mV} \leq V_o \leq 36\text{mV}$  (for a gain of 3x)

And most likely output offset voltage is zero NB Much better than previous case where there was no possibility at all that  $V_o$  could be zero.


### Practical points

It is important to remember that we are dealing here with DC quantities for  $V_{OS}$  and  $I_{Bp}$  and  $I_{Bn}$ . The analysis must consider only DC paths. If capacitors are present then the analysis must treat them as OPEN CIRCUIT because they block DC.

 1) In this circuit we make  $R_3 = R_1 \parallel R_2$  so that the DC paths resistances seen by the bias currents  $I_{Bp}$  and  $I_{Bn}$  are equal




 2) But in this circuit we make  $R_3 = R_2$  because the capacitor blocks the DC path through  $R_1$





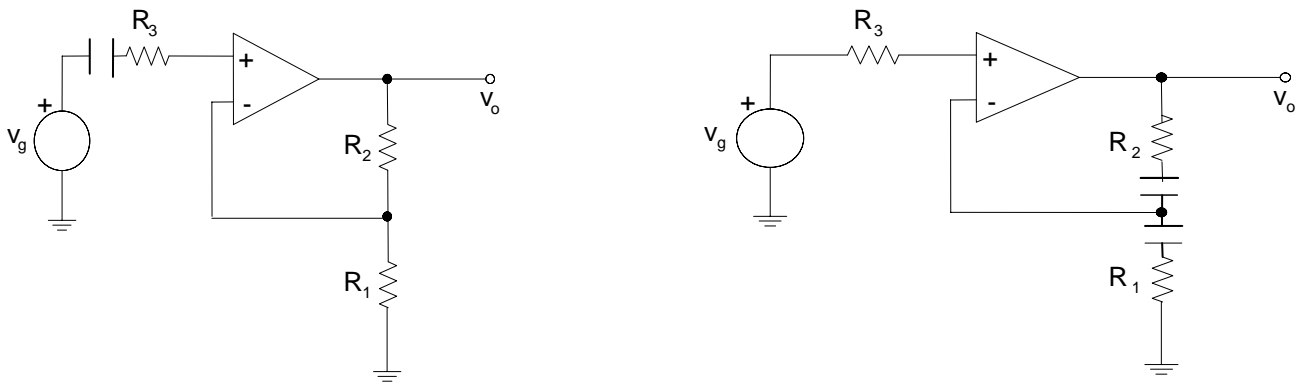**Note that there will be a problem** if no DC paths are provided to one or other of the inputs to allow the bias currents to flow. e.g



The solution would be to place a resistor across at least one of the capacitors, that is large enough not to affect the expected response but small enough to allow the small bias currents to flow without creating a significant DC voltage offset.

**End of Module.....**