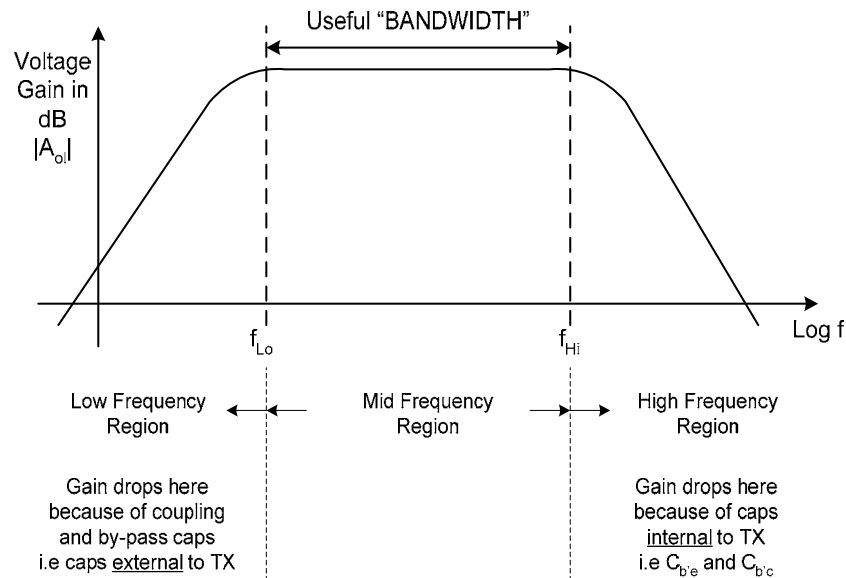


## Part 19: Effect of Negative Feedback on Amplifier Bandwidth

Bandwidth of transistor amplifiers is determined by **CAPACITORS**:



What happens when we apply feedback? How is bandwidth affected?

We can see what happens by considering frequency dependence of the loop gain  $T$

$$\text{Now } |T| \text{ in dB} = 20 \log_{10} |A_{ol} \beta_v|$$

$$= 20 \log_{10} |A_{ol}| + 20 \log_{10} |\beta_v|$$

↑  
This is 1<sup>st</sup> graph

Since  $0 < |\beta_v| < 1$ , then  $20 \log_{10} |\beta_v|$  is **negative**; eg. if  $|\beta_v| = 0.1$ , then  $20 \log_{10} |\beta_v| = -20 \text{ dB}$

So we can construct  $|T|$  vs. frequency curve by **shifting down**  $|A_{ol}|$  curve:


**Note points where**  
 $|T| = 0 \text{ dB} \rightarrow f_1, f_2$

The new amplifier having feedback has a gain (closed loop gain)

$$|A_{fv}| = \frac{1}{|\beta_v|} \left| \frac{T}{1+T} \right|$$


and as usual, if  $|T| \gg 1$  that is,

$$|T| \gg 0 \text{ dB} \text{ then } |A_{fv}| \approx \frac{1}{|\beta_v|} \text{ INDEPENDENT of } |A_{ol}|$$

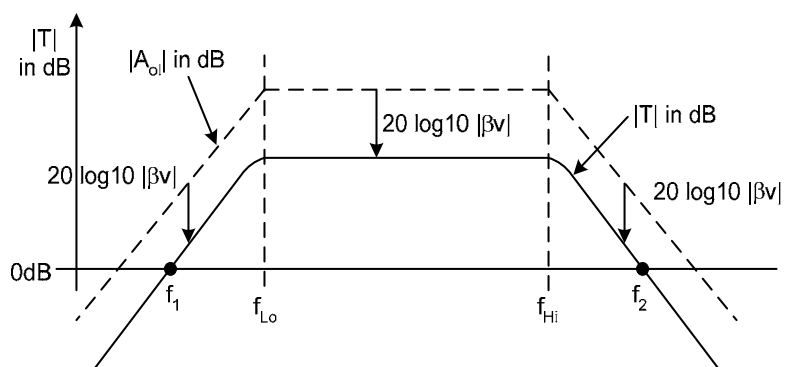

So we can sketch

$|A_{fv}|$  in dB as :

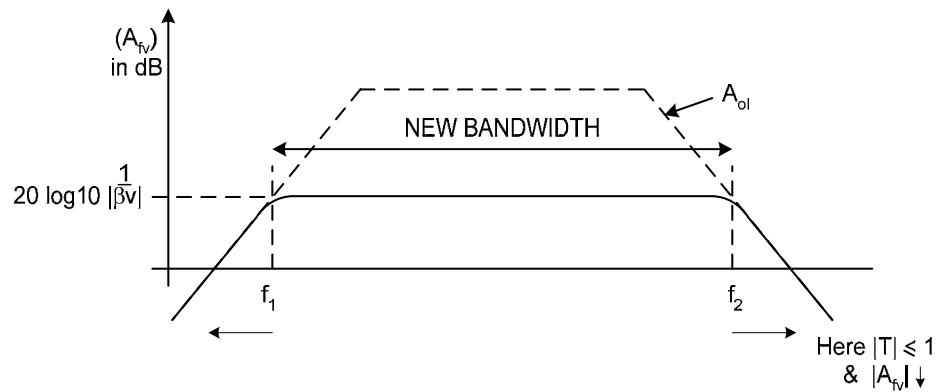

$$\text{OLD Bandwidth} = f_{Hi} - f_{Lo}$$


$$\text{NEW Bandwidth} = f_2 - f_1 \text{ which is } > f_{Hi} - f_{Lo}$$

NEG Feedback has **increased** bandwidth by **trading-off** open loop gain.

**How much bigger is the bandwidth?**

Need to have an analytic expression or a measurement of  $|A_{ol}|$  to decide this

**Particular Example**

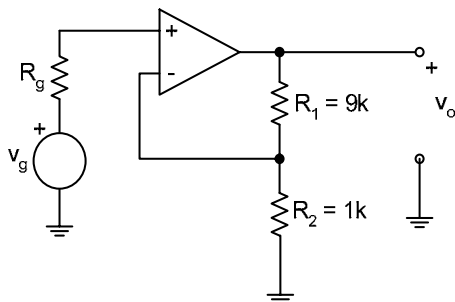

For this NON-INVERTING AMP,

$$\beta_v = \frac{R_2}{R_1 + R_2} = \frac{1k}{1k + 9k} = \frac{1}{10}$$

$$\text{So that ideally } \frac{v_o}{v_g} = A_{fv} = \frac{1}{\beta_v} = 10$$

What is bandwidth?


**Manufacturer specification sheet** gives open loop gain magnitude vs. Frequency (Fig. below)

$$\text{ie. } |A_{ol}| = 2 \times 10^5 = 106\text{dB at } 5\text{ Hz and below}$$

$$\text{but } = 1 = 0\text{dB at } 1\text{MHz}$$

Let us plot, on the same graph, the variation of


$\frac{1}{|\beta_v|}$  with frequency.

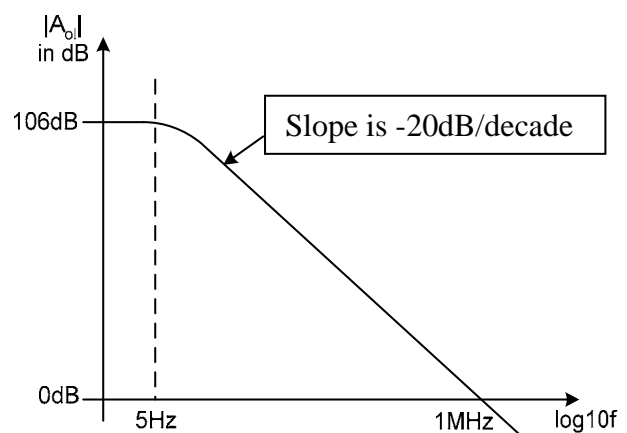

Let us plot, on the same graph, the variation of  $\frac{1}{|\beta_v|}$  with frequency.

$$\text{Since } \left| \frac{1}{\beta_v} \right| = 10, \left| \frac{1}{\beta_v} \right| \text{ in dB} = 20 \log_{10} 10 = 20 \text{ dB}$$

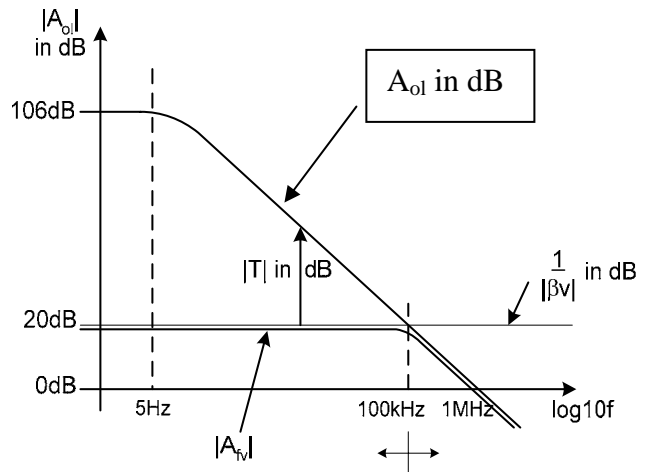**Independent of frequency**- so  $\frac{1}{\beta_v}$  vs freq is a horizontal straight line!



Now notice that the vertical distance between  $|A_{ol}|$  and  $\frac{1}{|\beta_v|}$  curves is the value of  $|T|$  in dB at that frequency.

$$\begin{aligned} \text{To see this: } 20 \log_{10} |A_{ol}| - 20 \log_{10} \frac{1}{|\beta_v|} &= \text{vertical separation} \\ &= 20 \log_{10} |A_{ol} \beta_v| = |T| \text{ in dB} \end{aligned}$$

At point where  $|A_{ol}|$  and  $\frac{1}{|\beta_v|}$  cross,  $|T| = 0 \text{ dB} \equiv 1x$


So from previous argument  $|A_{fv}| = \frac{1}{|\beta_v|}$  below  $100 \text{ kHz}$  where  $|T| \gg 1$

and above  $100 \text{ kHz}$  we have to use the more accurate expression:

$$|A_{fv}| = \frac{1}{|\beta_v|} \left| \frac{T}{1+T} \right| = \left| \frac{A_{ol}}{1+A_{ol}\beta} \right| \rightarrow |A_{ol}| \text{ when } |T| \ll 1$$

**The conclusion** is that  $|A_{fv}|$  follows  $\frac{1}{|\beta_v|}$  curve up to  $100 \text{ kHz}$  and then follows  $|A_{ol}|$  curve.

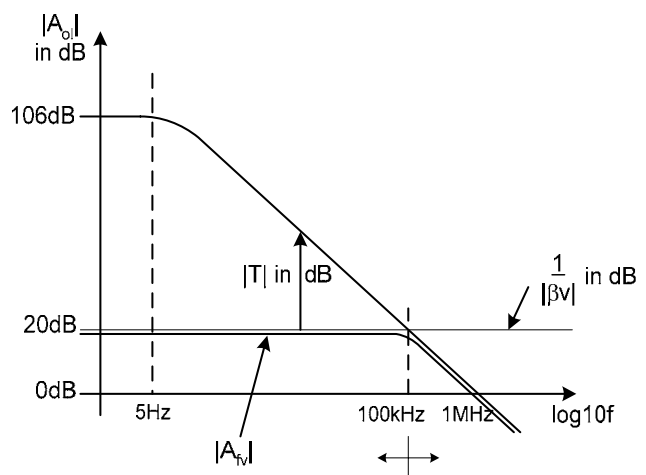Clearly bandwidth is now  $100 \text{ kHz}$



So original gain =  $2 \times 10^5 x$

new gain =  $10x$

Original bandwidth = 5 Hz

New bandwidth = 100kHz

**Gain reduction is by  $2 \times 10^4$  times**

**Bandwidth increase** is by  $\frac{100\text{kHz}}{5\text{Hz}} = 2 \times 10^4$  times

In fact **product** of gain and bandwidth is a **constant** for this type of non-inverting amplifier;  
product = “gain-bandwidth product” – **GBW**

Op-Amp has $2 \times 10^5 \times 5\text{Hz}$	=	1MHz GBW	} The <u>same</u> !
Op-Amp <b>circuit</b> has $10 \times 100\text{kHz}$	=	1MHz GBW	

Why is it that all non-inverting op-amp circuits built with a given op-amp have same GBW?

Because of SHAPE of  $|A_{ol}|$  curve

A slope of -20dB/decade  $|A_{ol}| \propto \frac{1}{f}$  that is  $A_{ol} \times f = \text{Const}$

$\therefore$  All points on the slope have  $|A_{ol}| \times f = \text{Const} = \text{GBW}$

So wherever  $\frac{1}{|\beta_v|}$  intersects  $|A_{ol}|$ , the frequency at the intersection  $\times \frac{1}{\beta_v} (= \text{gain}) = \text{GBW}$