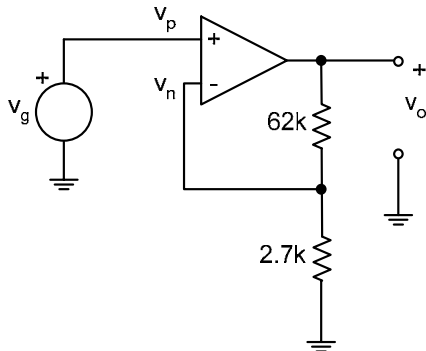


## Part 18: Loop Gain

### How to calculate its value directly

Consider:




1. **V.S.P. Method** gives  $v_n = v_p \equiv v_g$ ;

$$\text{But } v_n = \frac{2.7k}{2.7k + 62k} v_o = \frac{1}{24.0} v_o$$

$$\therefore v_g = \frac{1}{24.0} v_o \quad \text{or} \quad \frac{v_o}{v_g} = 24.0$$

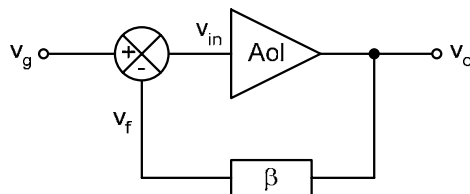2. **Feedback Method**  $A_f \cong \frac{1}{\beta}$


For this circuit; we have voltage **sensing** at output  
voltage **summing** at input



$$A_{ol} = \frac{v_o}{v_{in}}$$

$$\beta = \frac{v_f}{v_o}$$

$\beta$  can be found from

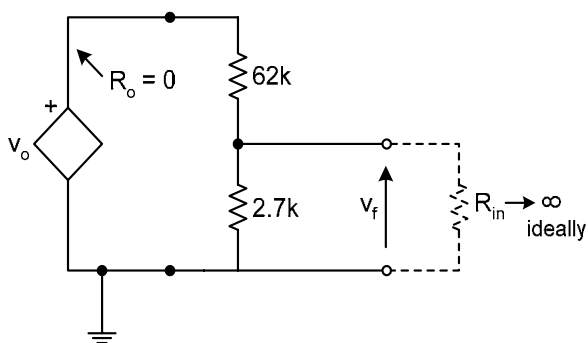

Thevenin equivalent of output

$$\therefore \beta = \frac{2.7k}{2.7k + 62k} = \frac{1}{24.0}$$

Op-amp Neg. fdbk made  $R_o \rightarrow 0$  ideally

$$\& A_f = \frac{v_o}{v_g} = \frac{1}{\beta} = 24.0 \text{ as before}$$

1<sup>st</sup> **method** assumes ideal op-amp with  $A_{ol} = \infty$  (so  $A_{ol} \beta \gg 1$ )

2<sup>nd</sup> **Method**  $T = A_{ol} \beta \gg 1$

What if T is not all that large? Feedback theory tells us that a **better estimate** of gain is

$$A_f = A_{\infty} \frac{T}{1+T}$$

Better estimate
Gain calculated using VSP or  $\frac{1}{\beta}$



### How do we find T?

If we know  $A_{ol}$  &  $\beta$  separately then easy BUT not always easy to find  $A_{ol}$  - especially for transistor circuits (rather than op-amps)

Better to find T directly

Method based on following

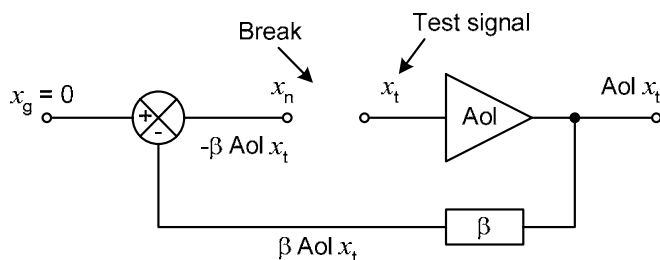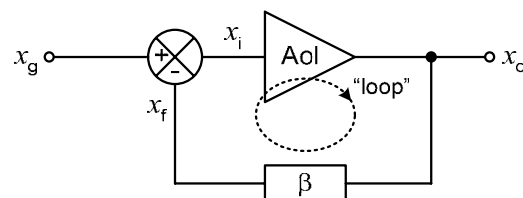- 1) Suppress  $x_g$  (set at zero)
- 2) Break loop at some convenient point
- 3) Inject a test signal  $x_t$



- 4) Trace round loop to find return signal  $x_r$

$$x_r = -\beta A_{ol} x_t$$

Then we see that  $\frac{x_r}{x_t} = -\beta A_{ol} = -T$



Or  $T = -\left(\frac{x_r}{x_t}\right)_{\text{suppressed source}}$

Note

- 1) If  $\frac{x_r}{x_t}$  is not negative, then feedback is positive!
- 2) Doesn't matter where in the loop, the break is made (see 'Problems 1'; solutions on VITAL)

### Application to non-inverting amplifier

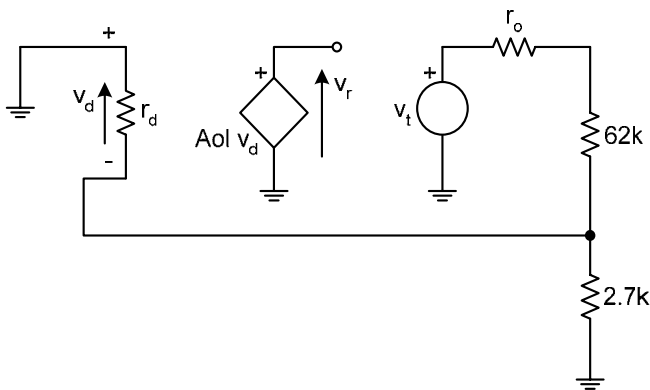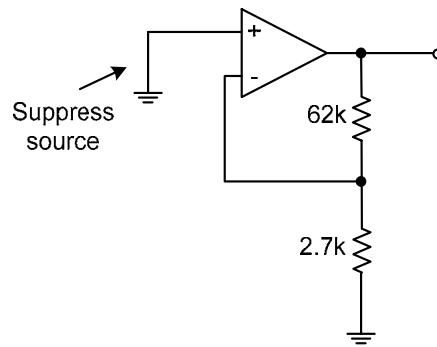1. Replace op-amp by equivalent circuit
2. Make break in circuit:  
[best place to break loop is directly after a generator]
3. Inject test voltage  $v_t$



Now suppose  $r_o=1k\Omega$ ;  $r_d=10k\Omega$ ;  $A_{ol}=10^2$  (not a very good op-amp!)


Easier to see analysis by re-drawing above circuit,

then

$$v_d = -\frac{(2.7k \parallel 10k)}{2.7k \parallel 10k + 62k + 1k} \times v_t$$

$$= -\frac{2.126k}{65.126k} \times v_t = -\frac{1}{30.63} v_t$$
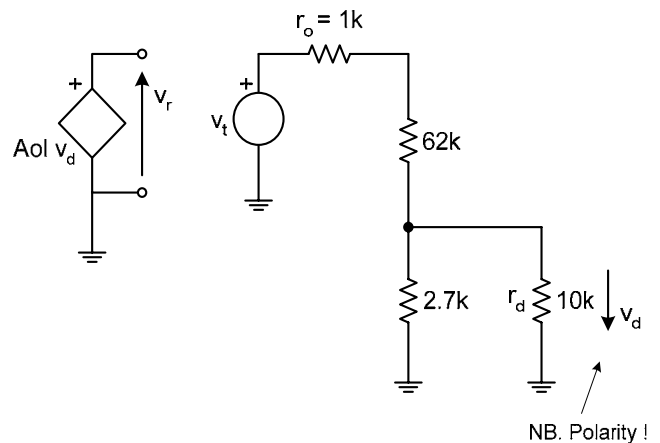
$$\therefore v_r = A_{ol} v_d = -\left(10^2 \times \frac{1}{30.63}\right) v_t \text{ ie } \frac{v_r}{v_t} = -3.264$$



That is,  $T=3.264$

(note earlier method would have given:

$$10^2 \times \frac{1}{24.0} = 4.167 - \text{over-estimate!}$$

$$\therefore \text{A better estimate of gain of this circuit is } A_f = A_{\infty} \times \frac{T}{1+T} = 24.0 \times \frac{3.264}{1+3.264}$$

$$\therefore \frac{v_o}{v_g} = 18.37$$

**Conclusion:**

our calculation of feedback fraction,  $\beta$  is only valid if  $T \gg 1$

We can now make a better estimate of  $R_{in}$

$$R_{in} \cong r_d(1+T) = 10k \times 4.264 = 42.64k$$

$$\text{and } R_o \cong \frac{r_o}{1+T} = \frac{1k}{4.264} = 234.5\Omega$$

**Now repeat the example** with  $A_{ol} = 2 \times 10^5$  (typical value for 741 op-amp)

Performing the previous analysis again gives:

$$\left( \frac{v_r}{v_t} \right)_{\text{suppressed source}} = -8.33 \times 10^3$$

So feedback is negative and  $T = 8.33 \times 10^3$

So a better estimate of the gain is:

$$\frac{v_o}{v_g} = 24.0 \times \frac{8.33 \times 10^3}{1 + 8.33 \times 10^3} = 24.0$$

! ie approximation  $A_f \equiv A_\infty \sim \frac{1}{\beta}$  is a good one!

Can also calculate  $R_{in} = r_d(1+T) = 2M\Omega \times (1 + 8.33 \times 10^3)$

ie  $R_{in} = 16.6 \times 10^9 \Omega$  - **which is big!** (as required for a V-amp)

also, output resistance is

$$R_o = \frac{r_o}{1+T} = \frac{75\Omega}{1 + 8.33 \times 10^3} = 9.00 \times 10^{-3} \Omega \text{ - which is small! (as required for a good V-amp)}$$


**Note that feedback gives very high and very low values for  $R_{in}$  /  $R_o$ — depending on the topology!**

**Another Example**

Inverting amplifier (recall it's a trans-resistance amp.)



$$V.S.P. \rightarrow \frac{v_o}{v_g} = -\frac{10k}{1k} = -10$$

With  $180^\circ$  phase shift

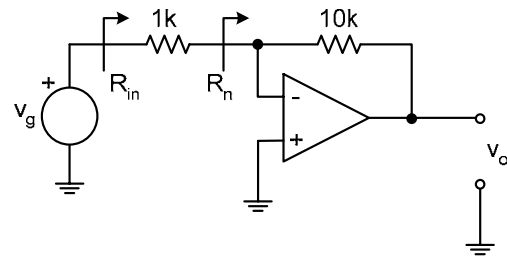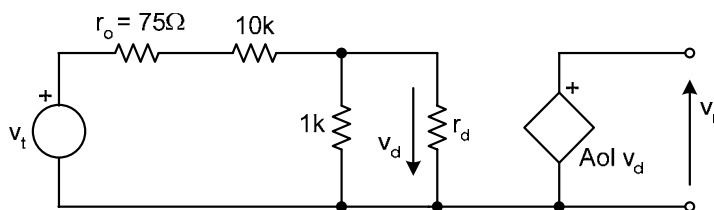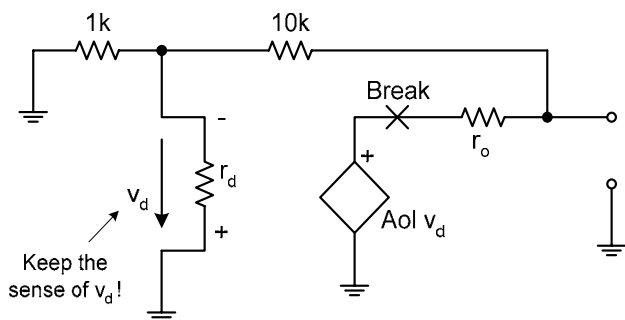**Loop gain?**

Suppress source and use equiv. circuit

Break loop and apply  $v_t$  to produce circuit shown below



$$1k \parallel r_d \cong 1k \quad A_{ol} = 2 \times 10^5$$

$$v_d = -\frac{1k}{1k \parallel 10k + 75} v_t = -\frac{1}{11.075} v_t$$

$$\therefore \frac{v_r}{v_t} = 2 \times 10^5 \times -\frac{1}{11.075} = -1.806 \times 10^4$$

So feedback is negative and loop gain is  $T = 1.806 \times 10^4$

$$\left( \frac{v_o}{v_g} \right)_{\text{better estimate}} = -10 \times \frac{1.806 \times 10^4}{1 + 1.806 \times 10^4} = -10$$

(as expected because  $T$  is so large)

$$R_o = \frac{r_o}{1+T} = 4.15 \times 10^{-3} \Omega - \text{small!} - \text{as expected}$$

$R_n = \frac{10k}{1+A_{ol}} = 0.05 \Omega$  - small! - as expected (because the feedback makes it an 'ideal' transresistance amplifier)

So  $R_{in} = 1k + R_n \sim 1k$  - ie  $R_{in}$  is set by the external resistor!