

Identify the building blocks

Differential amplifier

Two outputs

Two inputs

Ensures a good CMRR - Rejects the CM signals



Temperature compensated current source



Differential amplifier

single output

Emitter-follower to 'match' the stages

- Identify building blocks
- Perform a d.c. analysis
- Perform an a.c. analysis

Simple current mirror

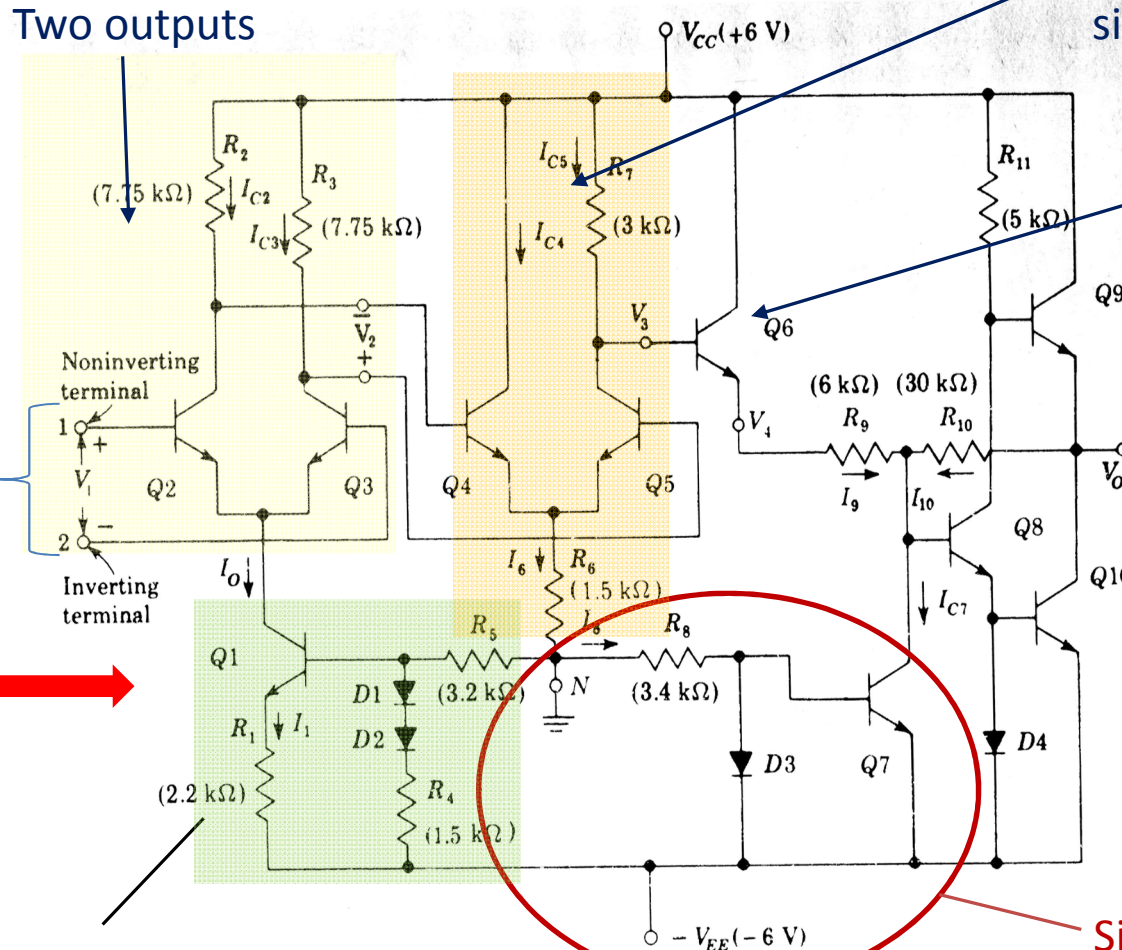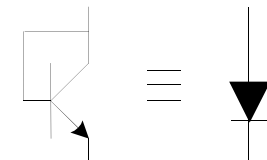

i) Voltage at base of Q1


Voltage drop across resistors?

$$6V - 0.6V - 0.6V = 4.8V$$


$$I = \frac{6 - 0.6 - 0.6}{3.2k + 1.5k} \approx 1mA$$

$$V_{BN1} = -IR_5 = -1mA \times 3.2k \\ = -3.2V$$

$$V_{BN1} = -3.2V$$

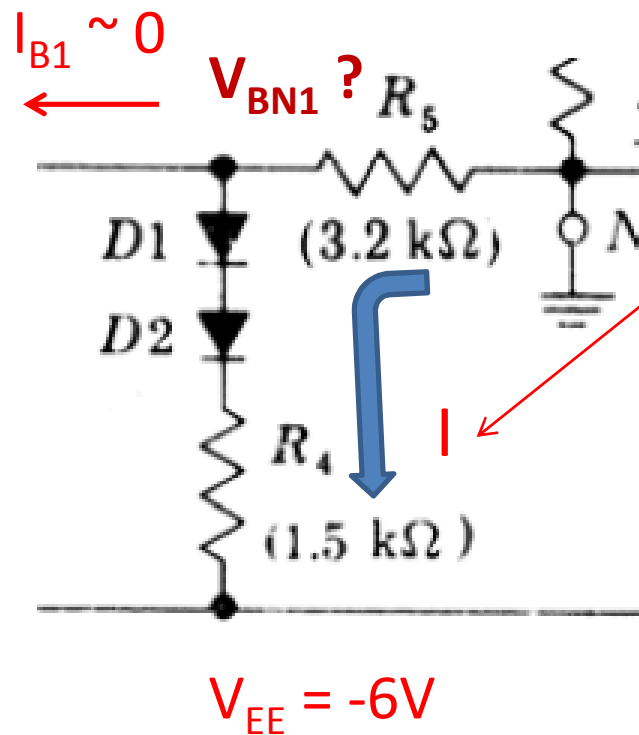

ii) I_1, I_O

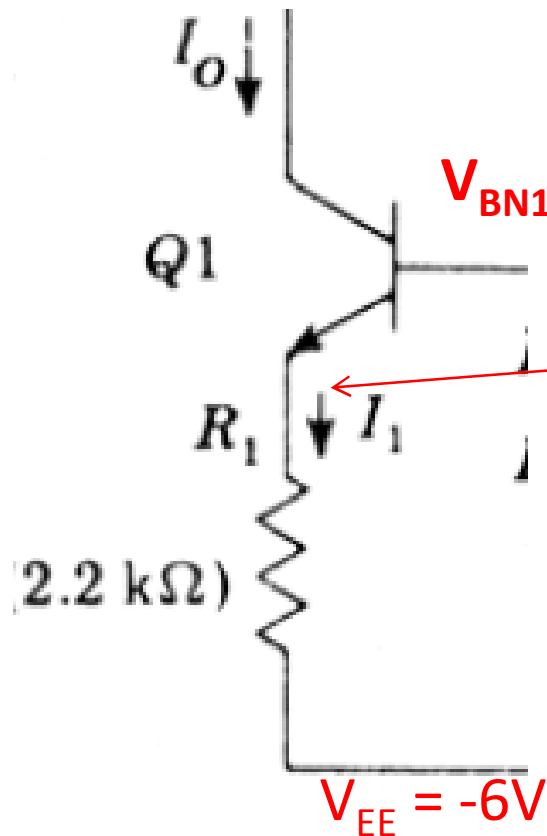

Voltage at emitter of Q_1 ?


$$V_E = V_{BN1} - 0.6$$

$$V_E = -3.8V$$

$$I_1 = \frac{-3.8 - (-6)}{2.2k} = \frac{2.2}{2.2k}$$

$$I_1 = 1mA \sim I_O$$

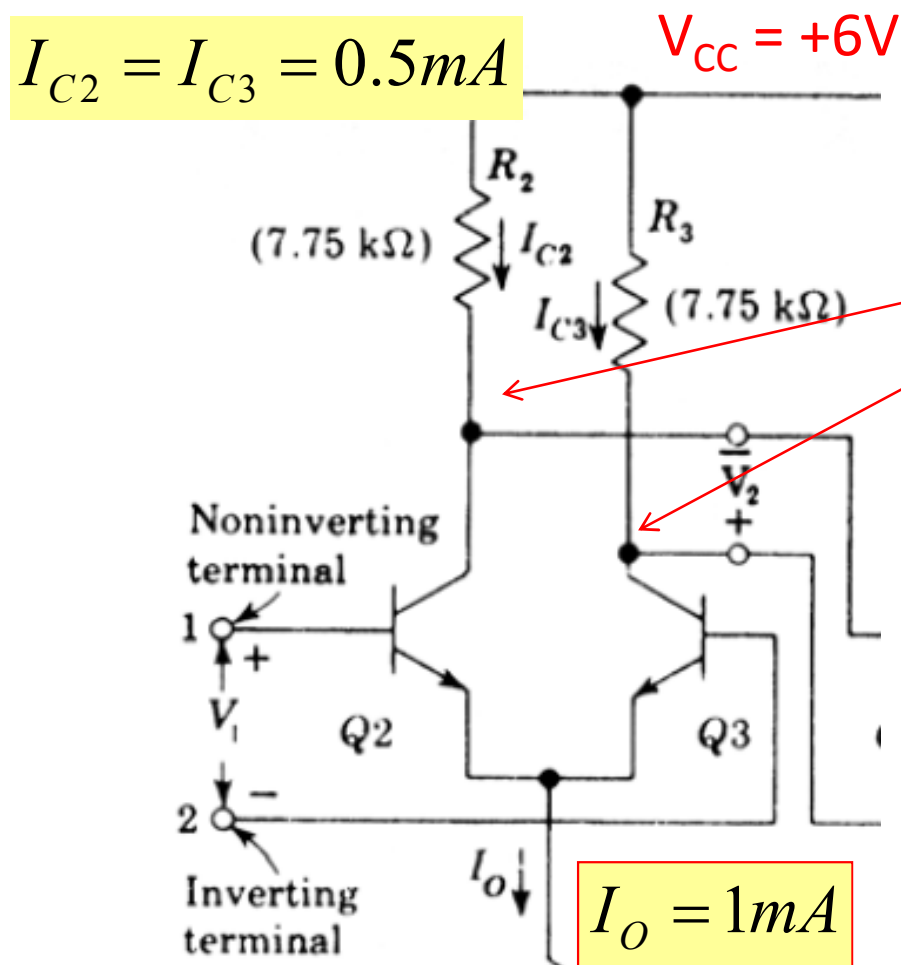- ii) contd. $I_{C2} = I_{C3}$?,
 iii) voltage at base of Q_4 ? ($V_{O1,2}$)



V_{O1} ?

Voltage drop across R_2 ?

$$V_{O1} = V_{O2} = 6 - I_{C2,3} \times 7.75k$$

$$V_{O1} = V_{O2} = 6 - 0.5mA \times 7.75k$$

$$V_{O1} = V_{O2} = 2.13V$$

$$V_{CC} = +6V$$

iv) I_{C4}, I_{C5} ?

Voltage at emitter of $Q_{4,5}$?


$$V_{O1} - 0.6$$

$$= 2.13 - 0.6 = 1.53V$$


I_6 ?


$$I_6 = \frac{1.53}{1.5k} \approx 1mA$$

$$V_{O1} = V_{O2} = 2.13V$$

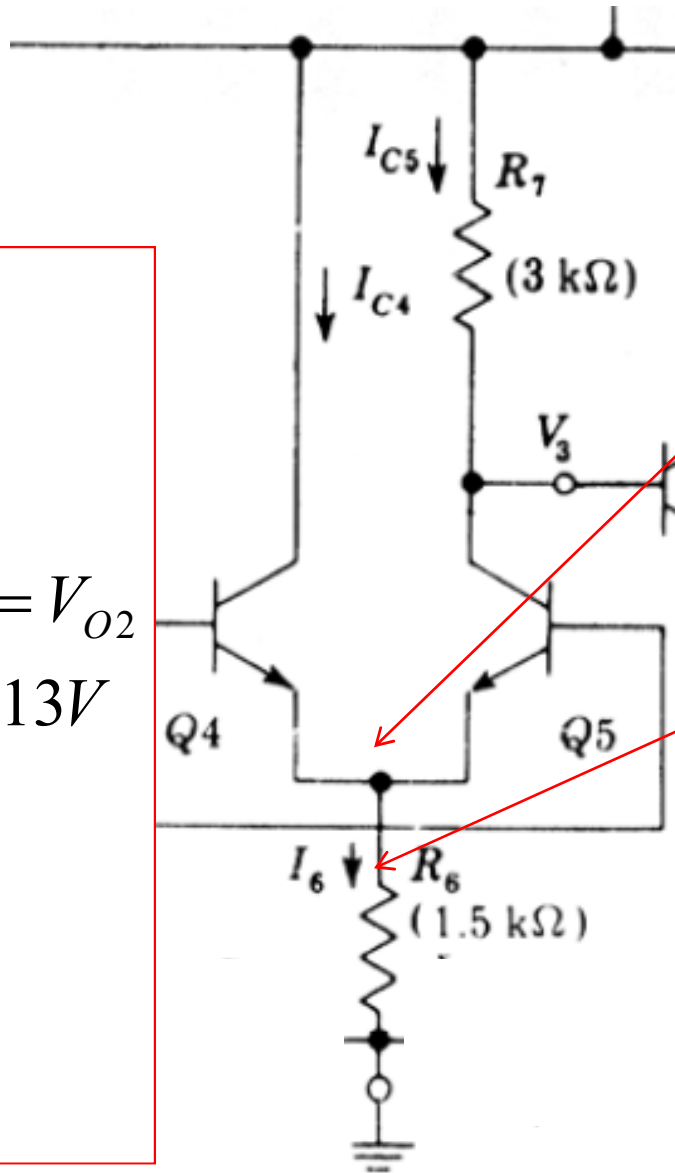

Identify the building blocks

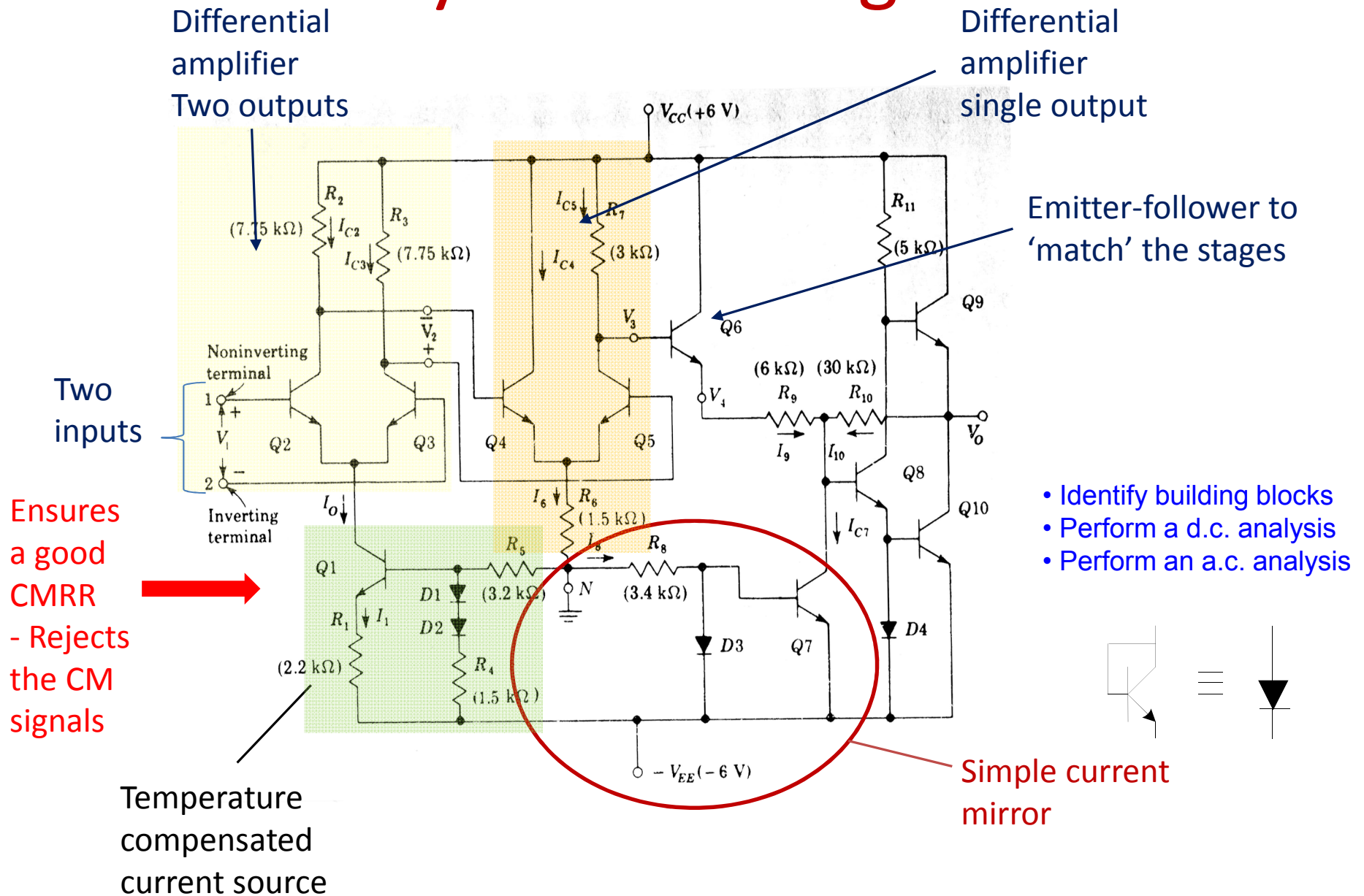

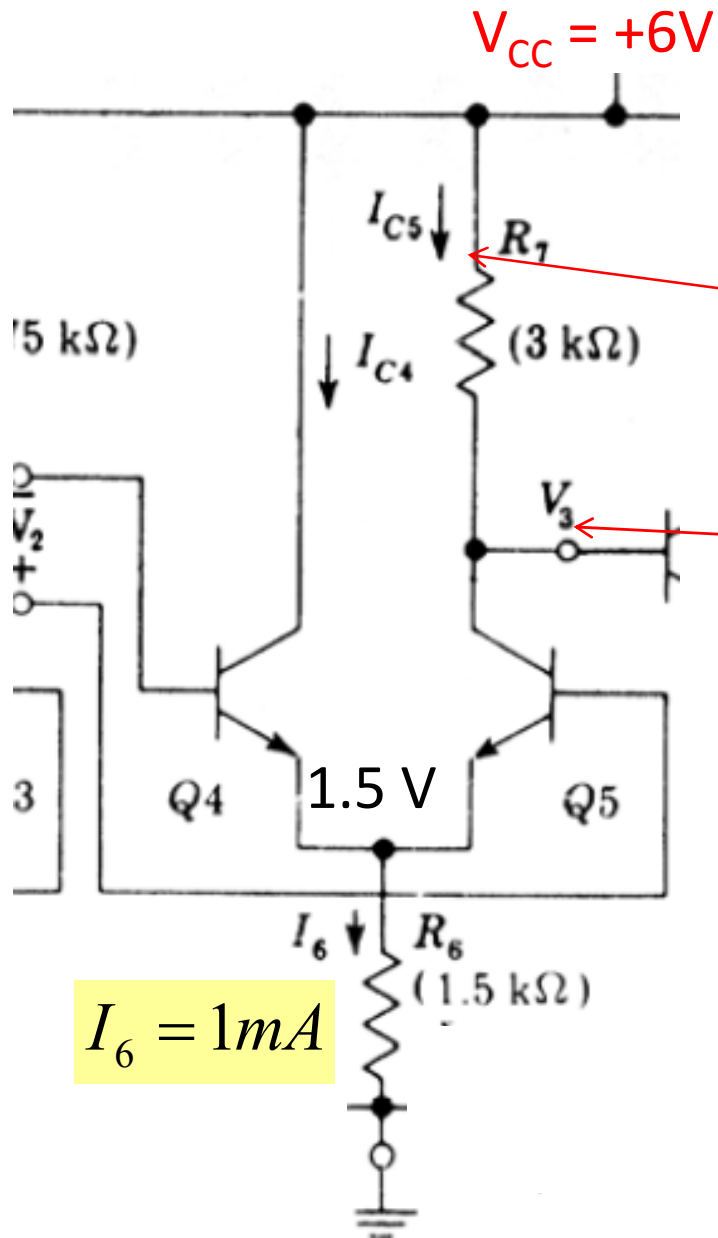

v) V_3 ?

I_{C5} ?


$$I_{C5} \approx \frac{I_6}{2} = 0.5mA$$

V_3 ?

$$V_3 = 6 - I_{C5} \times R_7$$

$$V_3 = 6 - 0.5mA \times 3k = 4.5V$$

v) contd. V_4 ?

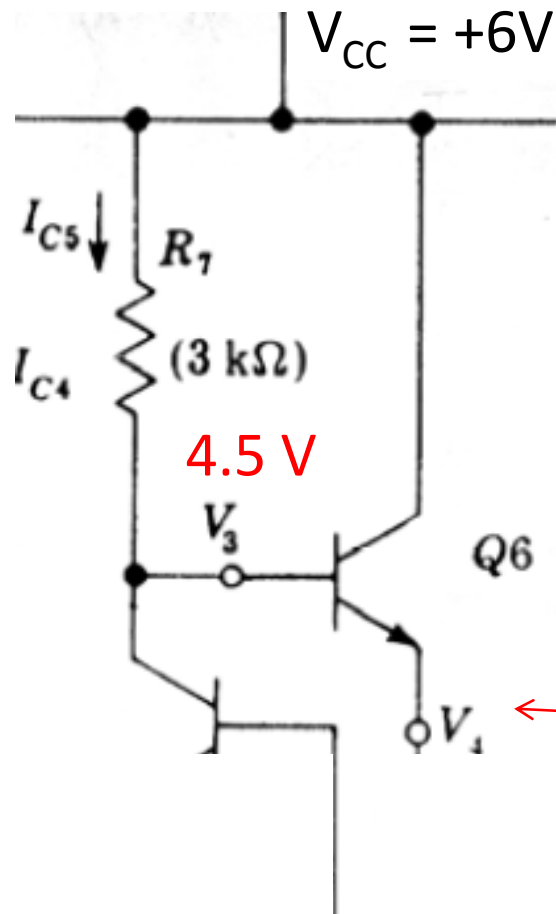


V_4 ?

$$4.5 - 0.6 = 3.9V$$

vi) I_8 hence I_{C7} ?

vii) Voltage at base of Q_8 ?

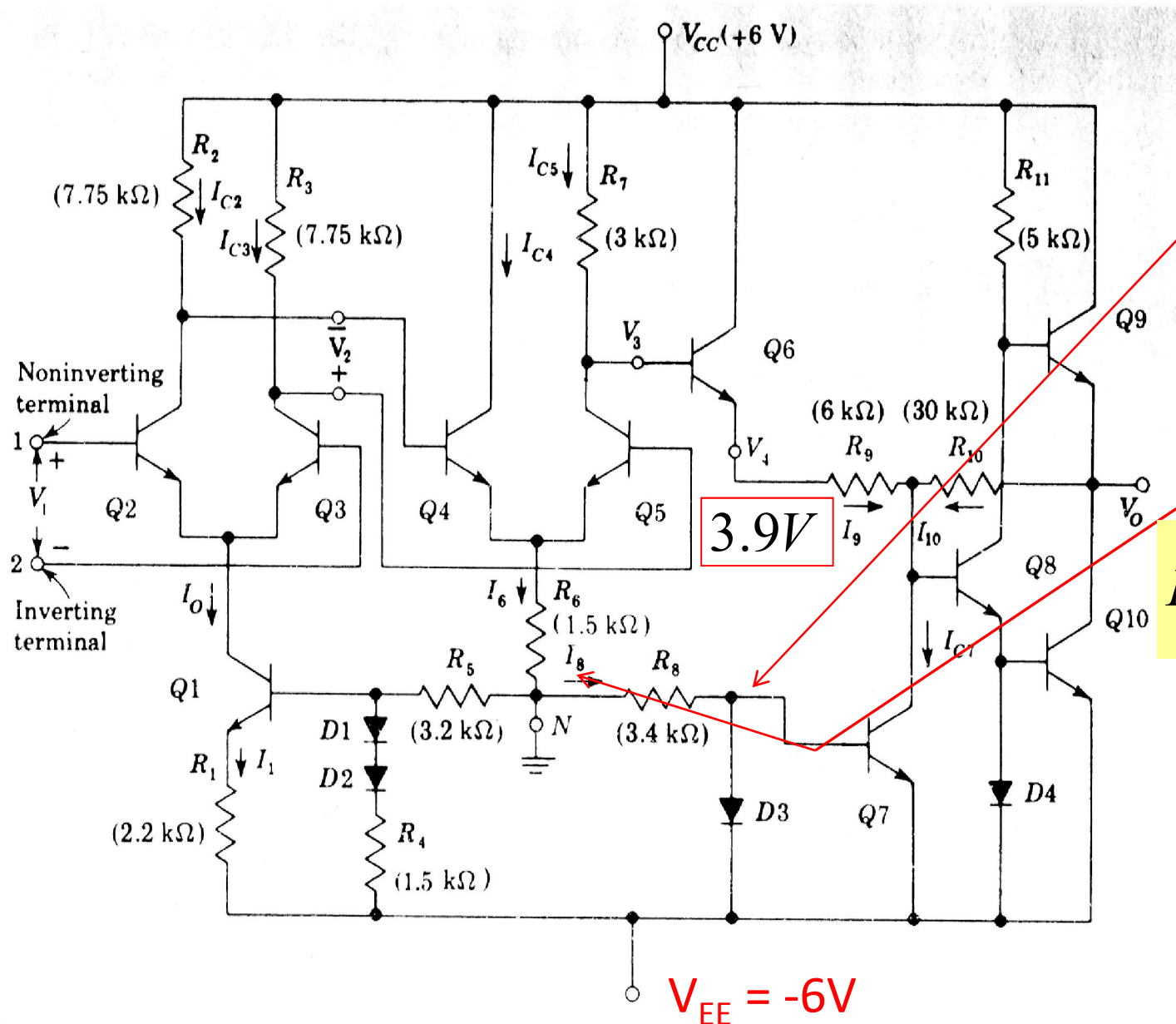

Voltage here?

$$-6 + 0.6 = -5.4V$$

I_8 ?


$$I_8 = \frac{5.4}{3.4k} = 1.6mA$$

I_{C7} ?

$$I_{C7} = I_8$$

By CM action

viii) I_9 ? ix) I_{10} ? x) V_O ?

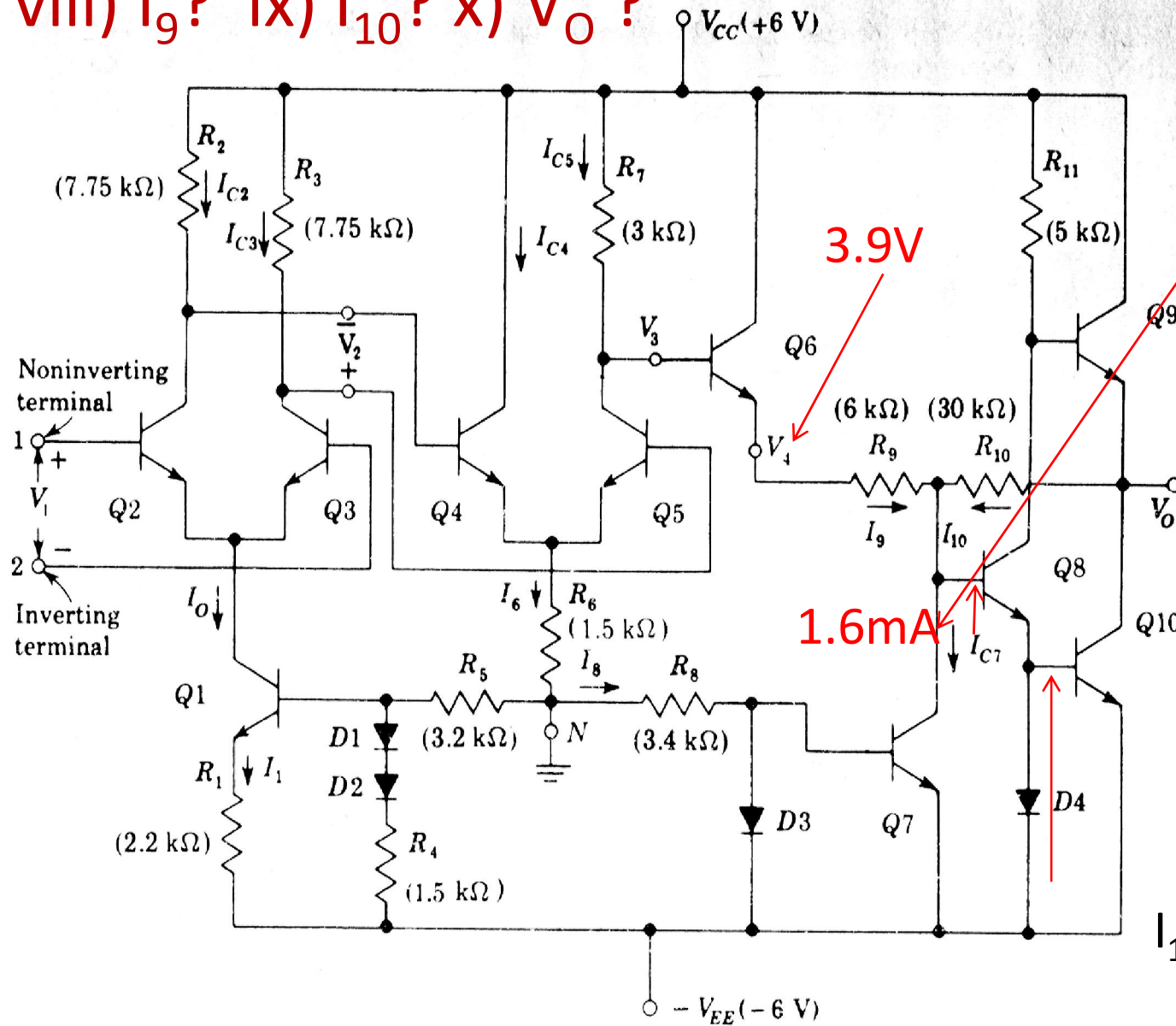

$$V_{EE} = -6V$$

Voltage here?

$$-6 + 0.6 + 0.6 = -4.8V$$

I_9 ?

$$I_9 = \frac{3.9 - (-4.8V)}{R_9} = 1.45mA$$

I_{10} ?

$$KCL: I_9 + I_{10} = I_{C7}$$

$$I_{10} = 1.6mA - 1.45mA = 0.15mA$$

V_O ?

Now calculate gain

Differential amplifier
Two outputs

Differential amplifier
single output

Emitter-follower to
'match' the stages

$$A_{Vd} = g_m (R_C \parallel R_{i2})$$

$$A_{Vd} = 40 \times \frac{1}{2} \text{mA} (R_C \parallel 2r_{be})$$

$$A_{Vd} = 20 \text{mA} \times (7.75 \text{k} \parallel 2 \times 10 \text{k})$$



$$A_{Vd} = 87$$

Ensures
a good
CMRR
- Rejects
the CM
signals

Temperature
compensated
current source

$$A_{Vd} = 87 \times 30 \times 1 \times 5 = 1,310$$

Simple current
mirror

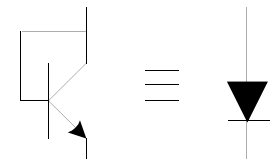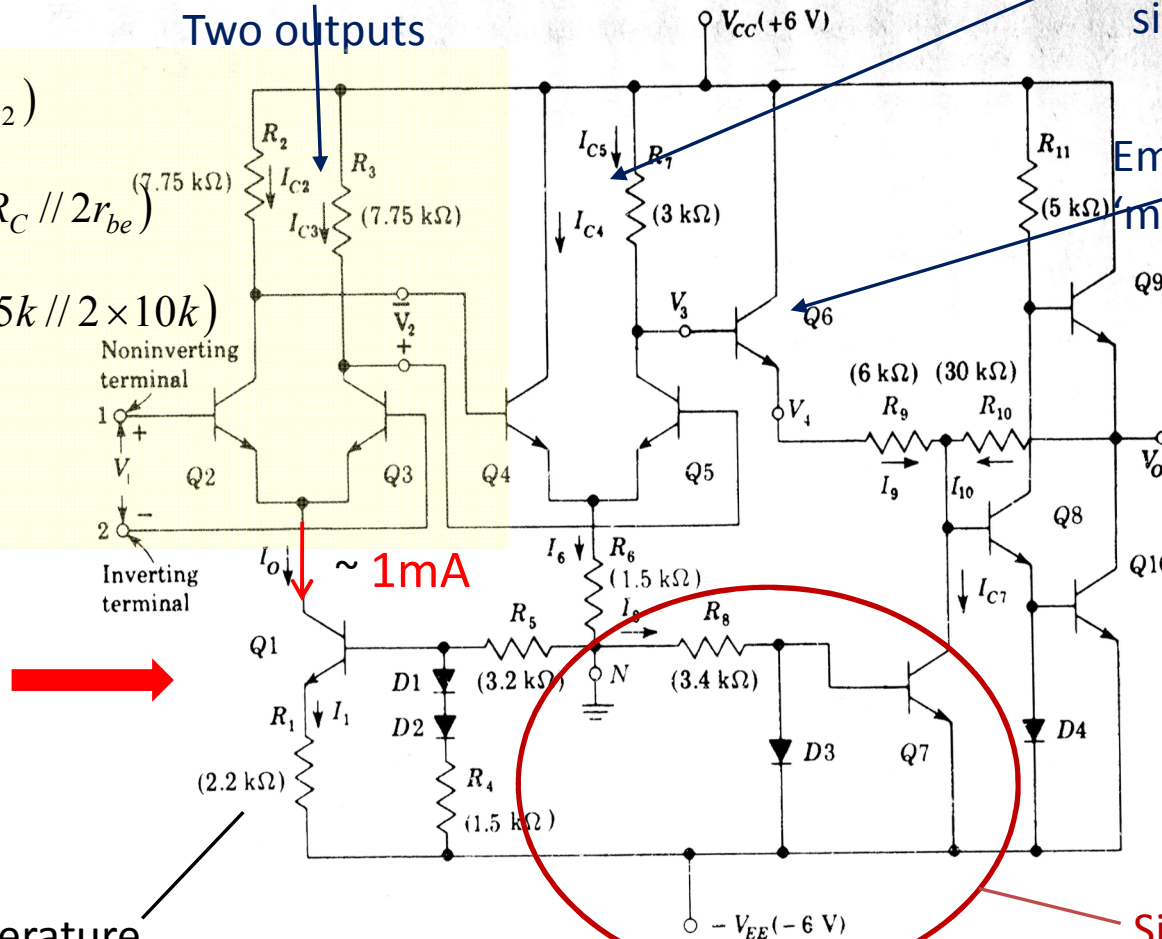

Tuesday 23rd Feb

- No lecture tomorrow
- See you on Wednesday