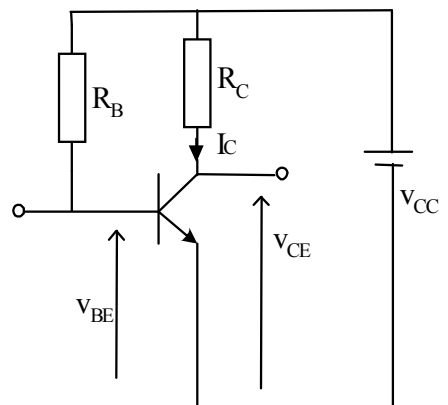


Exercises part 2

1. Consider the circuit shown opposite.

- a) What are the disadvantages of the biasing arrangement?
- b) The circuit is to be designed such that V_{CE} is fixed at $\sim V_{CC}/2$. Why would this be desirable?
- c) What is the voltage gain of the circuit?
- d) What is the effect on the voltage gain of increasing R_C subject to the constraint of b)?



Solution

- a) The resistor R_B is used to try to fix the DC base current hence the collector current. This does not provide for stability of the bias current (I_C) as I_B will drift with temperature. Four resistor biasing provides a far better solution; in particular, the emitter resistor provides DC feedback which helps to stabilise the collector current against temperature effects. (See the text books for more detail)
- b) Allows for a symmetrical swing for ac signals at the output.
- c)

$$A_V = g_m \times R_C = 40 \times I_C \times \frac{V_{CC} - V_{CE}/2}{I_C}$$
$$= 20 \times V_{CE}$$

- d) Increasing R_C with V_{BE} fixed would cause V_{CE} to decrease as I_C would be unchanged. To restore V_{CE} to $V_{CC}/2$, would be necessary to increase R_B so as to reduce I_B and hence I_C . Hence the gain would be unchanged (remember the ac input would be ac coupled via a coupling capacitor on the input).