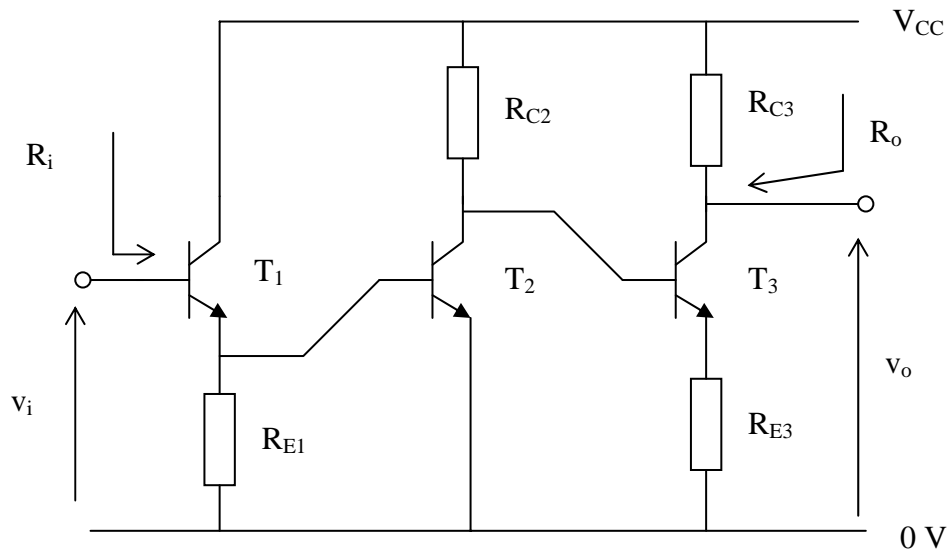


## Example: 3 stage Amplifier

(Using the details of amplifier properties provided)

### Question



In the circuit shown above, biasing components have been omitted. The collector currents in transistor  $T_1$ ,  $T_2$  and  $T_3$  are  $0.1\text{ mA}$ ,  $0.5\text{ mA}$  and  $2\text{ mA}$  respectively. Calculate the transistor transconductance ( $g_m$ ) and emitter-base resistance ( $r_{be}$ ) of each transistor. ( $\beta_o = 100$ ) Calculate the voltage gain  $v_o/v_i$ , the input resistance  $R_i$ , the output resistance,  $R_o$ .  $R_{E1} = 1\text{ k}\Omega$ ,  $R_{C2} = 10\text{ k}\Omega$ ,  $R_{C3} = 2\text{ k}\Omega$  and  $R_{E3} = 200\text{ }\Omega$ ; assume  $r_{ce}$  and  $r_{b'c}$  are infinite and  $r_{bb'} = 0$ .

## **Solution**

Relationship between  $I_C$  and  $V_{BE}$ :

$$I_C = I_S \exp\left(\frac{V_{BE}}{V_T}\right) \quad \text{where } V_T \text{ is 25 mV @ room. Temp}$$

$g_m$  transistor transconductance

$$g_m = \frac{\Delta I_C}{\Delta V_{BE}} = \frac{I_S}{V_T} \exp\left(\frac{V_{BE}}{V_T}\right) = \frac{I_C}{V_T}$$
$$\underline{g_m = 40 I_C}$$

$r_{b'e}$  dynamic resistance of the emitter-base junction

$$r_{b'e} = \frac{\Delta V_{BE}}{\Delta I_B} = \frac{\Delta V_{BE}}{\Delta I_C} \frac{\Delta I_C}{\Delta I_B} = \frac{\beta_o}{g_m}$$
$$\underline{r_{b'e} = \beta_o / (40 I_C) = \beta_o / g_m}$$

$\beta_o$  = common-emitter a.c. current gain  $\Delta I_C / \Delta I_B$

$$g_{m1} = 40 \times 0.1\text{m} = 4\text{mA/V}$$

$$g_{m2} = 40 \times 0.5\text{m} = 20\text{mA/V}$$

$$g_{m3} = 40 \times 2\text{m} = 80\text{mA/V}$$

$$r_{b'e1} = 100/g_{m1} = 25\text{k}\Omega$$

$$r_{b'e2} = 100/g_{m2} = 5\text{k}\Omega$$

$$r_{b'e3} = 100/g_{m3} = 1.25\text{k}\Omega$$

## **Voltage gain:**

$$v_o/v_i = v_o/v_{i3} \times v_{i3}/v_{i2} \times v_{i2}/v_i$$
$$= v_o/v_{i3} \times v_{o2}/v_{i2} \times v_{o1}/v_i = A_{v1} A_{v2} A_{v3}$$

*[BEST TO START FROM THE LAST STAGE AND WORK BACK]*

Third stage: common-emitter amplifier with emitter degradation

$$A_{v3} = - \frac{g_{m3} R_{C3}}{1 + g_{m3} R_{E3}}$$

$$= - 80\text{m} \times 2\text{k} / (1 + 80\text{m} \times 0.2\text{k}) = -9.4$$

$$\underline{A_{v3} = -9.4}$$

Also will need  $R_{i3}$  to work out loading on second stage:

$$R_{i3} = r_{be3} + (1 + \beta_o) R_{E3}$$
$$= 1.25\text{k} + 101 \times 0.2\text{k} = 21.5\text{k}$$

$$\underline{R_{i3} = 21.5\text{k}}$$

Second stage: Common emitter

$$\begin{aligned} A_{v2} &= -g_{m2} R_{C2} // R_{i3} \\ &= -20\text{m} \times 6.83\text{k} = -136.5 \end{aligned} \quad \underline{A_{v2} = -136.6}$$

Also need  $R_{i2}$  to work out loading on first stage

$$\underline{R_{i2} = r_{be2} = 5\text{ k}}$$

First stage: emitter follower

$$\begin{aligned} A_{v1} &= \frac{g_{m1} R_{E1} // R_{i2}}{1 + g_{m1} R_{E1} // R_{i2}} \\ (R_{E1} // R_{i2} &= 0.83\text{ k}) \\ A_{v1} &= 4\text{m} \times 0.83\text{k} / (1 + 4\text{m} \times 0.83\text{k}) = 0.77 \end{aligned} \quad \underline{A_{v1} = 0.77}$$

$$\text{Total gain is } 9.4 \times 136.5 \times 0.77 = 988$$

$$\underline{\text{Overall gain} = +988 \text{ (large)}}$$

Input resistance

is that of the first stage (emitter follower)

$$\begin{aligned} R_i = R_{i1} &= r_{be1} + (1 + \beta_o) R_{E1} // R_{i2} \\ &= 25\text{k} + 101 \times 0.83\text{k} = 109\text{k} \end{aligned} \quad \underline{R_i = 109\text{ k (high)}}$$

Output resistance

Is that looking into 3<sup>rd</sup> stage (CE-ED)

$$R_o = R_{C3} = 2\text{ k } \Omega \quad \underline{R_o = 2\text{ k}}$$