

# Electronic circuits and systems

## ELEC271

### Part 21

### Op-amp limitations

**So far have assumed an ideal op-amp:**

Input draws no current

Zero output voltage for zero input voltages

**Not in fact true!** Although OK for doing simple design

**Now the truth! .....** And what can be done

# Slew-rate limit to bandwidth

SR relates to the ability of the op-amp to respond to a signal; that is, it relates to the **transient response** of the op-amp.

**Part 9:** the response,  $t_{\text{rise}}$  of an ac coupled amplifier should be an **exponential rise** with a time constant related to the upper cut-off frequency,  $f_H$  of the amplifier:

$$f_H = \frac{1}{2\pi\tau_r}$$

## Op-amps also have a limit on how rapidly the output voltage can change



- Transient response of an **op-amp** is **linear** - gradient is referred to as the **slew rate**.
- such a response is obtained when a capacitor is charged by a constant current.
- The capacitor in this case is the large compensation one (C) – see the 741 schematic circuit - the constant current (I) is provided by the current mirror bias circuit at the saturated input stage. So....

$$SR \equiv \frac{dV_o}{dt} = \frac{I}{C}$$

For the op-amp

**If the applied signal amplitude exceeds the slew rate limit at some frequency below  $f_H$ , then an incorrect estimate of the true bandwidth will be obtained.**

# Charging of Compensation capacitor

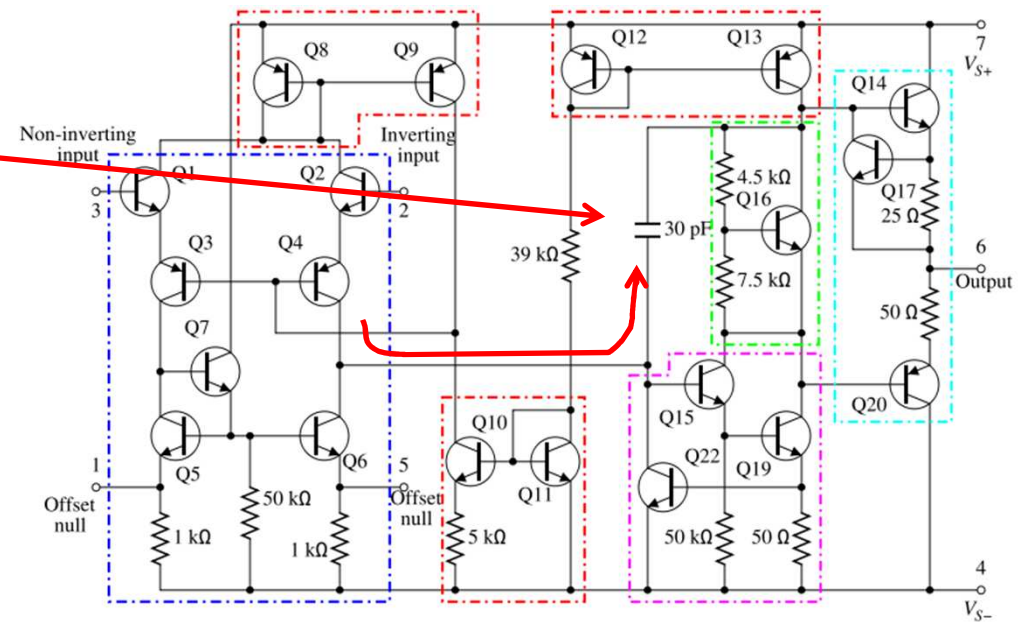 

30pF Compensation capacitor charges via a constant current source (current mirror)

## Slew rate (contd.)

$$SR \equiv \frac{dV_o}{dt} = \frac{I}{C}$$

For the 741 op-amp  $C = 30\text{pF}$  and  $I \sim 19\mu\text{A}$   
giving a SR value of about  $0.6\text{V}/\mu\text{s}$ .

---

**Consider a sine-wave input to an op-amp circuit:**  $V_i = V_m \sin(\omega t)$

$$\text{Then } \frac{dV_i}{dt} = \omega V_m \cos(\omega t) \quad \text{and} \quad \left. \frac{dV_i}{dt} \right|_{\max} = \omega V_m = 2\pi f V_m$$

If the value of  $(2\pi f V_m)$  is **less than** the **SR limit**, the output can follow the input!


**Example:** Assume input signal amplitude same as power supply value (10V say),

then  $V_m = 10\text{V}$ . Now  $SR = \omega V_m = 0.6\text{V} / \mu\text{s}$

that is,  $f = \frac{0.6}{2\pi \times 10^{-6}} \frac{1}{10} = 9.6\text{kHz}$  for the slew rate limited frequency of  
a 10 V amplitude signal

**Higher frequency signals would be limited and distorted.**

 **A slew rate limited output will be apparent from the shape of the output waveform**



**Unlike the upper bandwidth limit**, the frequency at which the slew rate limit is reached depends on the **amplitude of the output signal as well as its frequency**.

**Exercise:** An operation amplifier with a slew-rate limit of  $1\text{V}/\mu\text{s}$  is required to amplify a sinusoidal  $100\text{kHz}$  signal. Calculate the maximum amplitude of the output voltage that can be achieved without distortion.

**Solution**

$$\text{Slew rate} = dv_o/dt = 1\text{V}/\mu\text{s}$$

For a sinusoidal signal,  $v(t) = V_o \sin(\omega t)$ ;  $dv_o/dt = V_o \omega \cos(\omega t) = V_o \omega$  (maximum)

for a signal frequency of  $100\text{kHz}$ , then:  $10^6 = V_o 2\pi \times 10^5$

$$SR = V_o 2\pi \times f$$

So  $V_o$  (max) =  $1.6\text{ V}$  (so to avoid SR limiting, ensure  $V_o < 1.6\text{ V}$ )

# Part 21

## Op-amp limitations (contd.)


**So far have assumed an ideal op-amp:**

Input draws no current

Zero output voltage for zero input voltages


**Not in fact true!** Although OK for doing simple design

 **Last time: slew rate – need to consider dynamic response (time domain) – 741 –  $0.6\text{V}/\mu\text{s}$**



# The Voltage Offset

Consider an experiment:

 


Here  $V_p = V_n = 0$  (tied to ground)

So **ideally** we expect:

$$V_o = A_{ol} [V_p - V_n] \equiv 0$$

However, in **practice**, we usually find  $V_o \neq 0$

 This is due to **an imbalance** between input stages of the op-amp which process  $V_p$  and  $V_n$  resulting in the **VOLTAGE TRANSFER CURVE (VTC)** for a real op amp being displaced from the origin:




There is a **shift**

can be to the left OR right of the VTC away from the origin

– called the “**input offset voltage**”,
 
# How to model the offset

We can therefore **model** a real op-amp as



N.B.  $V_{OS}$  is a DC source **referenced to the input** – it is always connected to the positive (+ve) input **by convention**, with polarity shown.

But note that it is equally likely to be a positive or negative value!

It is the equivalent input voltage that would need to be applied (as shown) to make  $V_o = 0$

The manufacturer usually gives the **magnitude** of  $V_{OS}$  - eg for 741C,

$$V_{OS} = 2\text{mV typical, } 6\text{mV max.}$$


This means ~50% of 741C's tested have  $V_{OS}$  between -2mV to +2mV, but all have  $V_{OS}$  between -6mV and +6mV.


 
## What error is caused by $V_{OS}$ ?

e.g. For the non –inverting amp:

We first suppress  $V_g$  to allow us to concentrate on the effect of  $V_{OS}$  alone




Replacing real op-amp by its model gives

$$V_o = \left[ \frac{R_1 + R_2}{R_1} \right] \times V_{os}$$

So the offset voltage is amplified by the gain of the amplifier to produce a DC output offset voltage.


If the gain is small, so is the output offset ;

 but if, for example, the gain is  $\sim 1000$ , then  $V_{OS}$  becomes  $\pm 2V$  typical,  $\pm 6 V$  max for a 741C, **not a small error!**


 
# The Current Offset (1)


Suppose, we take an op-amp and build the following circuit:



Input transistors in the **op-amp MUST be provided with base current** in order to operate ( $I_{Bp}$  and  $I_{Bn}$ )

→ a voltage is generated across the 1MΩ resistor which acts as an input voltage to the op-amp, and so it is amplified to give a DC output  $V_o$ .

 
N.B. the input bias currents can be either into op-amp or out of op-amp depending on whether input stage is constructed with npn or pnp transistors:


 
## The Current Offset (2)

These currents are particularly troublesome because they are **strongly temperature dependent** – so ***the output voltage drifts***

The effect can be significantly reduced if the circuit is arranged to present the same resistance to both input terminals




So now we are only concerned with the **difference** between the two currents  $I_{Bp}$  and  $I_{Bn}$

$$v_o = A_{ol} [(-I_{Bp} \times 10^6) - (-I_{Bn} \times 10^6)]$$

$$V_O = A_V (I_{Bp} - I_{Bn}) \times 1M$$

 **For example**, in the inverting op-amp circuit, always make  $R_3 = R_1 // R_2$



**\* Practical tip**

# Data Sheets

The manufacturer, after measuring a **large number of samples**, gives us the average base current

$$I_B = \frac{I_{Bp} + I_{Bn}}{2}$$

which is called the **'input bias current'** on **data sheets**.

AND they give us the magnitude of the offset current difference

$$I_{os} = |I_{Bp} - I_{Bn}| = \text{'input offset current'}$$

**For a 741C:**

$$\begin{aligned} I_B &= 80\text{nA typical, } 500\text{nA max} \\ I_{os} &= 80\text{nA typical, } 200\text{nA max} \end{aligned}$$

$$\begin{cases} I_{Bn} = I_B - \frac{I_{os}}{2} \\ I_{Bp} = I_B + \frac{I_{os}}{2} \end{cases}$$

In the WORST possible case, this means either  $I_{Bp} = 600\text{nA}, I_{Bn} = 400\text{nA}$   
or  $I_{Bp} = 400\text{nA}, I_{Bn} = 600\text{nA}$

Summarise this by saying that in all cases


$$I_B - \frac{I_{os}}{2} < [I_{Bn}, I_{Bp}] < I_B + \frac{I_{os}}{2}$$

## Model of a Real Op-Amp including both Voltage and Current offsets

We model current offsets by CURRENT sources:

With current sources of polarity shown, model is of an op-amp with npn input transistors.

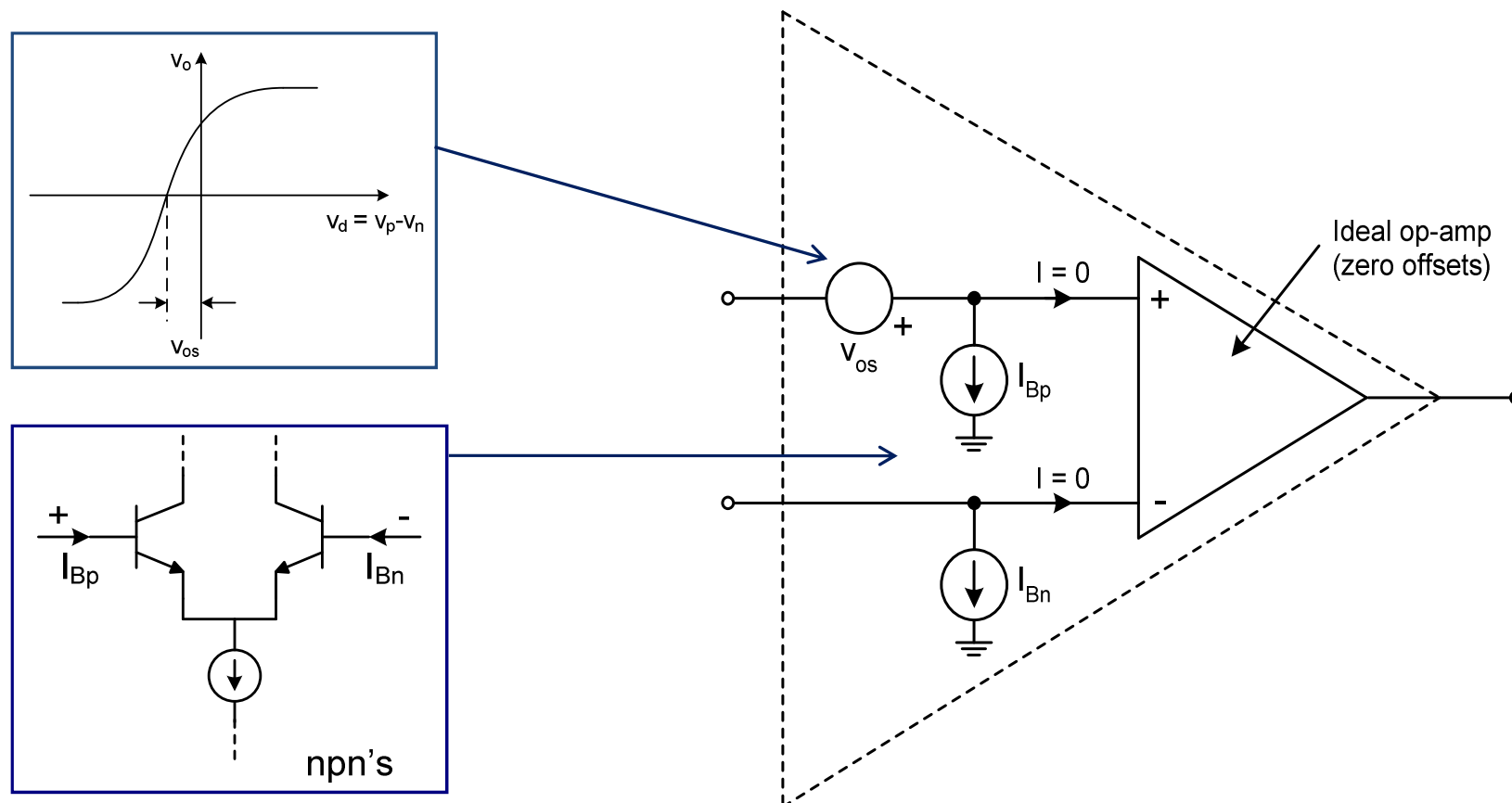Also, the voltage off-set voltage source is added to give the complete model



## Example: calculation of output offset in general case

Find  $V_o$  when


$$R_1 = 45k \quad R_2 = 90k \quad R_3 = 10k$$

Given that

$$V_{os} = 6mV; I_B = 500nA, I_{os} = 200nA$$

PREPARATION FOR CALCULATION

suppress  $V_g$  and insert model

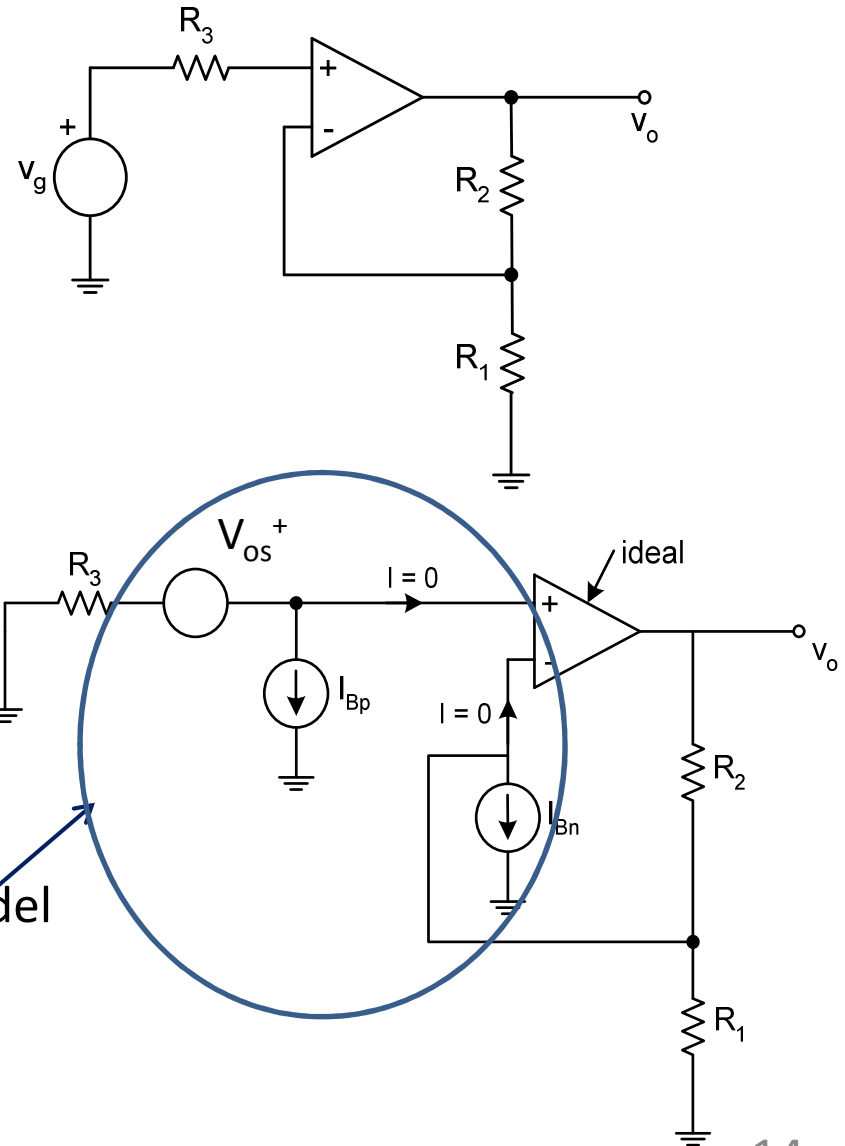


**Solution: find effect on output of all 'parasitic' sources**

**– use principle of superposition**

 **Effect of  $V_{os}$  alone is**

$$V_{o1} = \left[ \frac{R_1 + R_2}{R_1} \right] \times V_{os}$$




**Effect of  $I_{Bp}$  alone** is obtained by first replacing the current source with the equivalent voltage source =  $-I_{Bp}R_3$

(N.B. Note polarity !)

Then

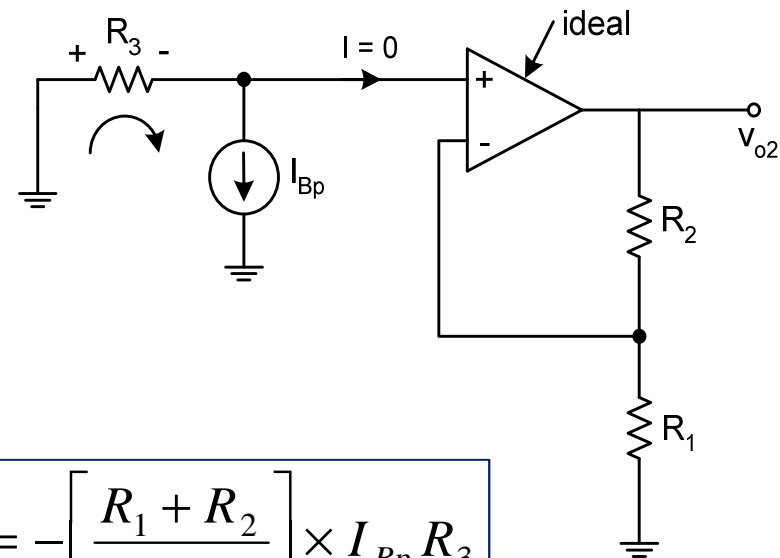
$$V_{o2} = \left[ \frac{R_1 + R_2}{R_1} \right] \times (-I_{Bp}R_3)$$



$$V_{o2} = - \left[ \frac{R_1 + R_2}{R_1} \right] \times I_{Bp}R_3$$

# Calculation of output offset in general case (contd.)


## Effect of $I_{Bn}$ alone

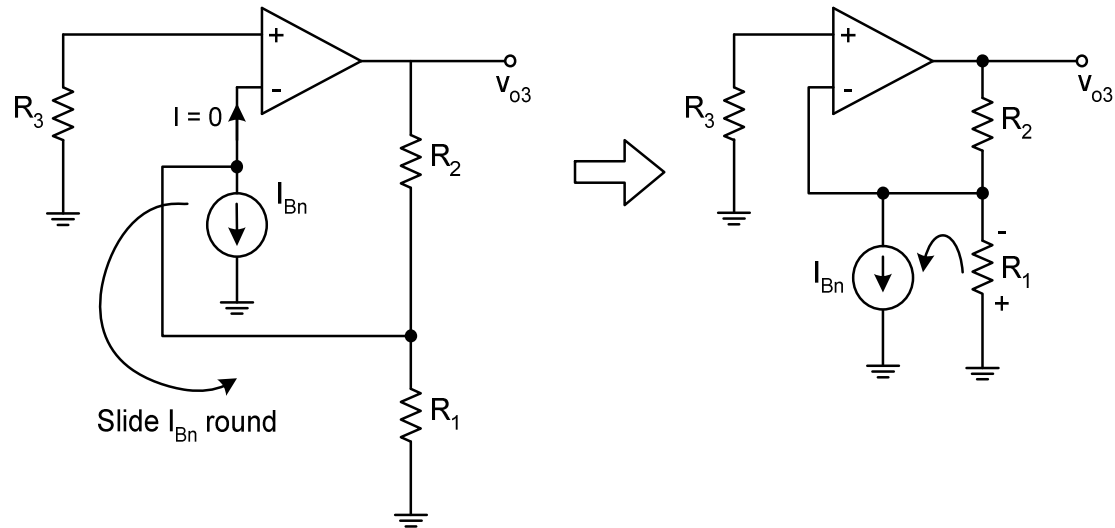

Now a source transformation:

$$V_{o3} = \left( -\frac{R_2}{R_1} \right) \times (-I_{Bn} R_1)$$

$$V_{o3} = I_{Bn} R_2$$

 


$$\text{So } v_{o3} = \left( -\frac{R_2}{R_1} \right) \times (-I_{Bn} R_1)$$


 
## COMBINING contributions gives

$$V_o = V_{o1} + V_{o2} + V_{o3}$$

$$\begin{aligned}
 V_o &= \left( \frac{R_1 + R_2}{R_1} \right) [V_{os} - I_{Bp} R_3] + \frac{R_2}{R_1} I_{Bn} R_1 \\
 &= \left( \frac{R_1 + R_2}{R_1} \right) [V_{os} - I_{Bp} R_3] + \underbrace{\left( \frac{R_1 + R_2}{R_1} \right) \left( \frac{R_1}{R_1 + R_2} \right)}_{=1!} R_2 I_{Bn} \\
 &= \left( \frac{R_1 + R_2}{R_1} \right) [V_{os} - I_{Bp} R_3] + \left( \frac{R_1 + R_2}{R_1} \right) R_1 \parallel R_2 I_{Bn} \\
 &= \left( \frac{R_1 + R_2}{R_1} \right) [V_{os} - I_{Bp} R_3 + R_1 \parallel R_2 I_{Bn}] \quad \left( \text{Take } \left( \frac{R_1 + R_2}{R_1} \right) \text{ outside the bracket} \right)
 \end{aligned}$$



$$V_o = \left( \frac{R_1 + R_2}{R_1} \right) V_{eff}$$

with

$$V_{eff} = [V_{os} - I_{Bp} R_3 + R_1 \parallel R_2 I_{Bn}]$$

where  $V_{eff}$  = effective input offset voltage – for this amplifier circuit

# Calculation of $V_O$ in worst case

$$Gain = \frac{R_1 + R_2}{R_1} = \frac{45k + 90k}{45k} = 3$$

$$R_1 \parallel R_2 = 45k \parallel 90k = 30k$$

Consider components of  $V_{eff} = [V_{os} - I_{Bp} R_3 + R_1 \parallel R_2 I_{Bn}]$

From data sheet:  $-6mV < V_{os} < 6mV$  and  $400nA < [I_{Bp}, I_{Bn}] < 600nA$

$$10k \times 400nA < R_3 I_{Bp} < 10k \times 600nA \Rightarrow 4mV < R_3 I_{Bp} < 6mV$$

$$30k \times 400nA < R_1 \parallel R_2 I_{Bn} < 30k \times 600nA \Rightarrow 12mV < R_1 \parallel R_2 I_{Bn} < 18mV$$


Combine graphically: Draw ranges of each component

MAX NEG value of  $V_{eff}$  when each component has max. neg. value

$$\therefore \text{Max.neg. } V_{eff} = -6mV + 12mV - 6mV = 0$$

MAX Pos value of  $V_{eff}$  when each component has max. pos. value
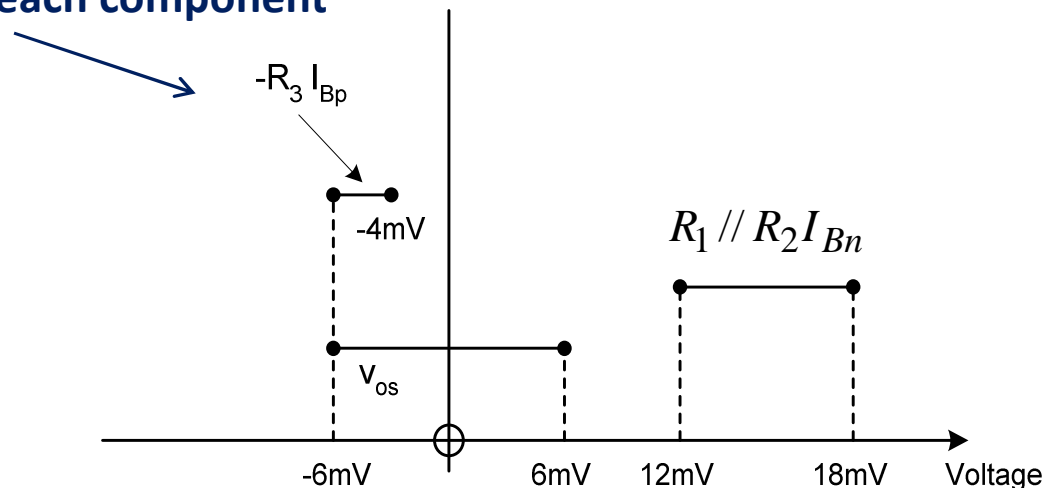
$$\therefore \text{Max.pos. } V_{eff} = -4mV + 6mV + 18mV = +20mV$$



Most probable value for  $V_O$  is half way through this range i.e.  $10mV \times \text{Gain} = 30mV$

## Calculation of $V_o$ in worst case (contd.)

So in worst case,  $V_o$  lies in the range

$$0 \leq V_o \leq 3 \times 20mV$$

$$0 \leq V_o \leq 60mV$$

MOST LIKELY value of  $V_o$   
is mid-way through this range;  
ie  $V_o$  (max probability) = **30mV**

NB We can adjust  **$R_3$**  then chose




$$R_3 = R_1 \parallel R_2$$

Since in this case, range pattern  
is symmetrical about zero voltage point!

$$\text{Min } V_{eff} = -18mV - 6mV + 12mV = -12mV$$

$$\text{Max } V_{eff} = -18mV + 6mV + 18mV = +12mV$$

   So that o/p offset voltage is  $-36mV < V_o < 36mV$




**Most probable value for  $V_o$  is zero!**

## Some PRACTICAL points


Important to remember that we are dealing here with **DC**  $V_{OS}$  and  $I_{Bp}$  and  $I_{Bn}$ .

**The analysis must consider only DC paths.** If capacitors are present then the analysis must treat them as OPEN CIRCUIT because they block DC.

 1) In this circuit we make  $R_3 = R_1 // R_2$  so that the DC paths resistances seen by the **bias currents  $I_{Bp}$  and  $I_{Bn}$**  are equal




 2) But in this circuit we make  $R_3 = R_2$  because the capacitor blocks the DC path through  $R_1$


 
## Some further PRACTICAL points

**Note that there will be a problem** if no DC paths are provided to one or other of the inputs to allow the bias currents to flow. e.g







The solution in both cases would be to place a resistor across at least one of the capacitors that is:

- large enough not to affect the expected response
- but small enough to allow the small bias currents to flow without creating a significant DC voltage offset

# These circuits are OK

## What do they do?

 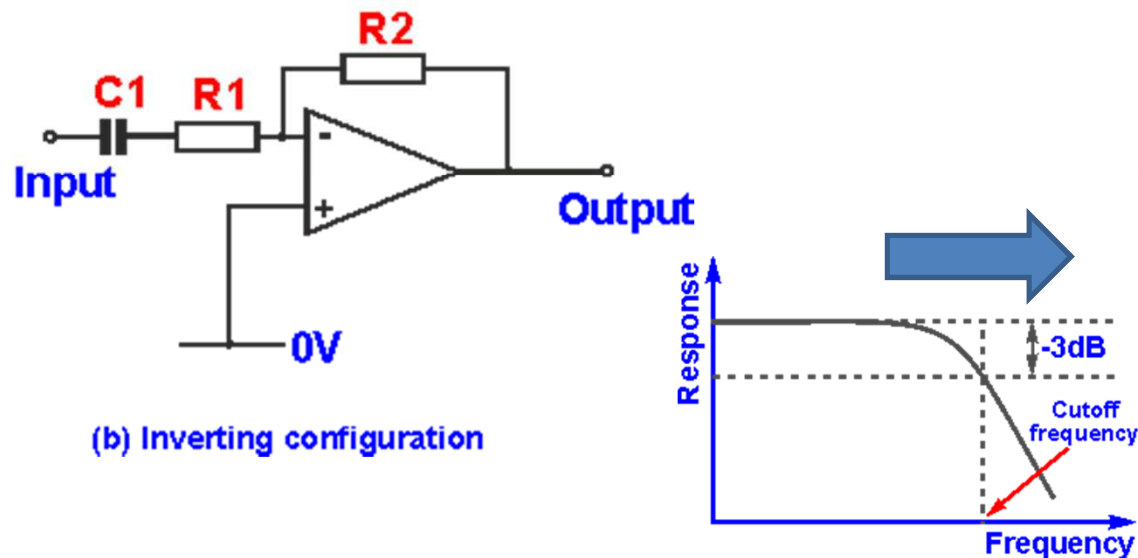  

**End of ....the lecture topics !!**

**Some revision classes will follow (3-4)**

**1<sup>st</sup> one on Monday after Easter**

**The slides can be found on VITAL  
First item in 'Sessions/resources**

# Self-assessment Test 2

- A self-assessment test will be available on VITAL on 1<sup>st</sup> Monday of next term at 9am (look in 'Assessment' section).
- 12 short questions
- It should take no more than 1 hour
- use your notes! – it's all there.