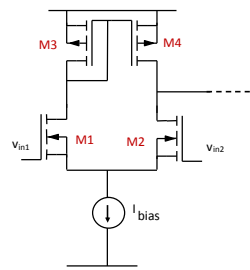


Solutions to Part 7 Exercises


1. Derive equations for the transconductance and output resistance of a MOSFET in the linear region of operation.

$$I_D = \beta \left[ (V_{GS} - V_T)V_{DS} - \frac{V_{DS}^2}{2} \right]$$
$$g_m = \left. \frac{\Delta I_D}{\Delta V_{GS}} \right|_{V_{DS} = \text{const.}} = \beta \times V_{DS}$$
$$g_{ds} = \left. \frac{\Delta I_D}{\Delta V_{DS}} \right|_{V_{GS} = \text{const.}} = \beta \times (V_{GS} - V_T - V_{DS})$$
$$r_{ds} = \frac{1}{g_{ds}}$$

2. The figure shows a differential amplifier. Assuming that the amplifier feeds into a very large load resistance, show that the differential gain is given by  $g_m \times r_{ds2} // r_{ds4}$  and the common mode is (ideally) zero. The technique is shown in part 5 – this derivation is much easier!



MOSFET Differential Amplifier

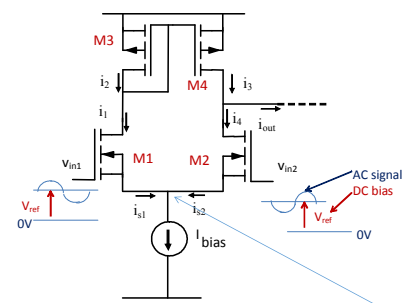


$I_D \sim V_{GS}^2$   
 $i_1 = i_2$   
 $i_2 = i_3$   
Over 1<sup>st</sup> half of sine wave,  $i_1$  increases, hence so does  $i_3$   
 $i_4$  reduces, hence  
 $i_{out} = i_4 - i_3$   
 $i_{s1} = -i_{s2}$   
So forms an ac ground

voltage gain?

a.c. analysis: simpler than for BJTs!

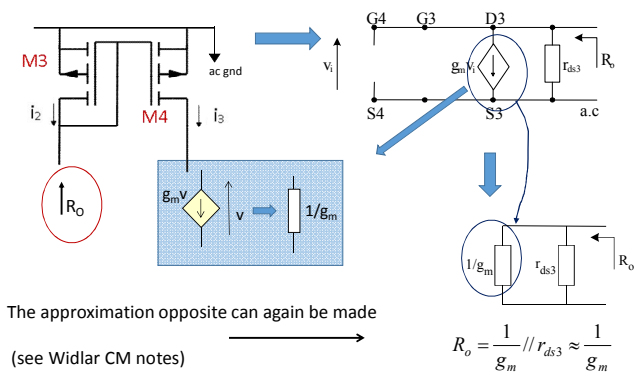Need an equivalent circuit for the current mirror load:  
what 'resistance' is seen looking up into the current mirror?



Ac equivalent circuit for  $A_{vd}$  (ignore  $r_{ds}$ )

Note that the voltage drop across the  $1/g_m$  load is

$$v_4 = (g_m v_1) \times 1/g_m = v_1$$


Then write:

$$\begin{aligned} i_o &= g_m (v_4 - v_2) \quad (\text{KCL}) \\ &= g_m (v_1 - v_2) \\ &= g_m v_{id} \end{aligned}$$

That is,  $i_o = g_m v_{id}$

$$\text{So } v_o = g_m v_{id} R_L$$

$$\text{So } v_4 = v_1$$

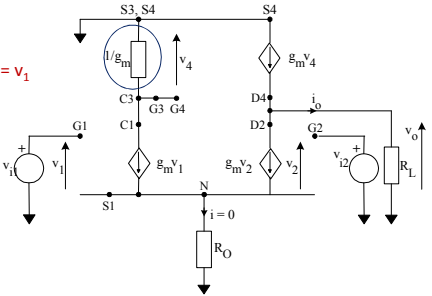

$$\therefore A_{vd} = g_m R_L \text{ (single ended voltage gain)}$$

Include the effect of  $r_{ds}$ 's


$v_2$  and  $v_4$  are set to zero  
(by convention) for finding  
output resistance,  
the a.c. load is by inspection,

$$R_o' = r_{ds4} \parallel r_{ds2} \text{ and } R_o = r_{ds4} \parallel r_{ds2} \parallel R_L$$

So **without**  $R_L$   $A_{vd} = g_m (r_{ds4} \parallel r_{ds2})$  - VERY HIGH  
But **with**  $R_L$ ,  $A_{vd} = g_m (r_{ds4} \parallel r_{ds2} \parallel R_L)$

if  $R_L \ll r_{ds4} \parallel r_{ds2}$ , then  $A_{vd} \sim g_m R_L$  - VOLTAGE GAIN MUCH REDUCED if  $R_L$  small!!

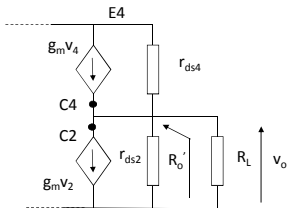→ ensure that the diff. amp. is not fed into a low impedance stage!




Common Mode Gain

Currents in left and right-hand sides of the circuit are the same (by CM action), so

$$i_o = 0$$

$$v_o = 0$$

$$A_{vc} = 0$$

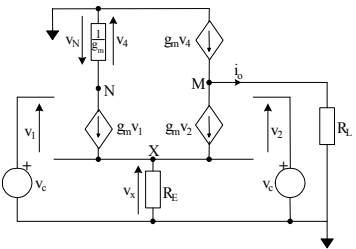

Ideally, the common-mode gain is zero! (In reality, very small)