

Electronic circuits and systems

ELEC271

Part 3

The Differential amplifier – I

Another important circuit building block

How does it work and what does it do?


How to analyse?

How to design it?

A target for week 4...

By about week 4 we will be able to:

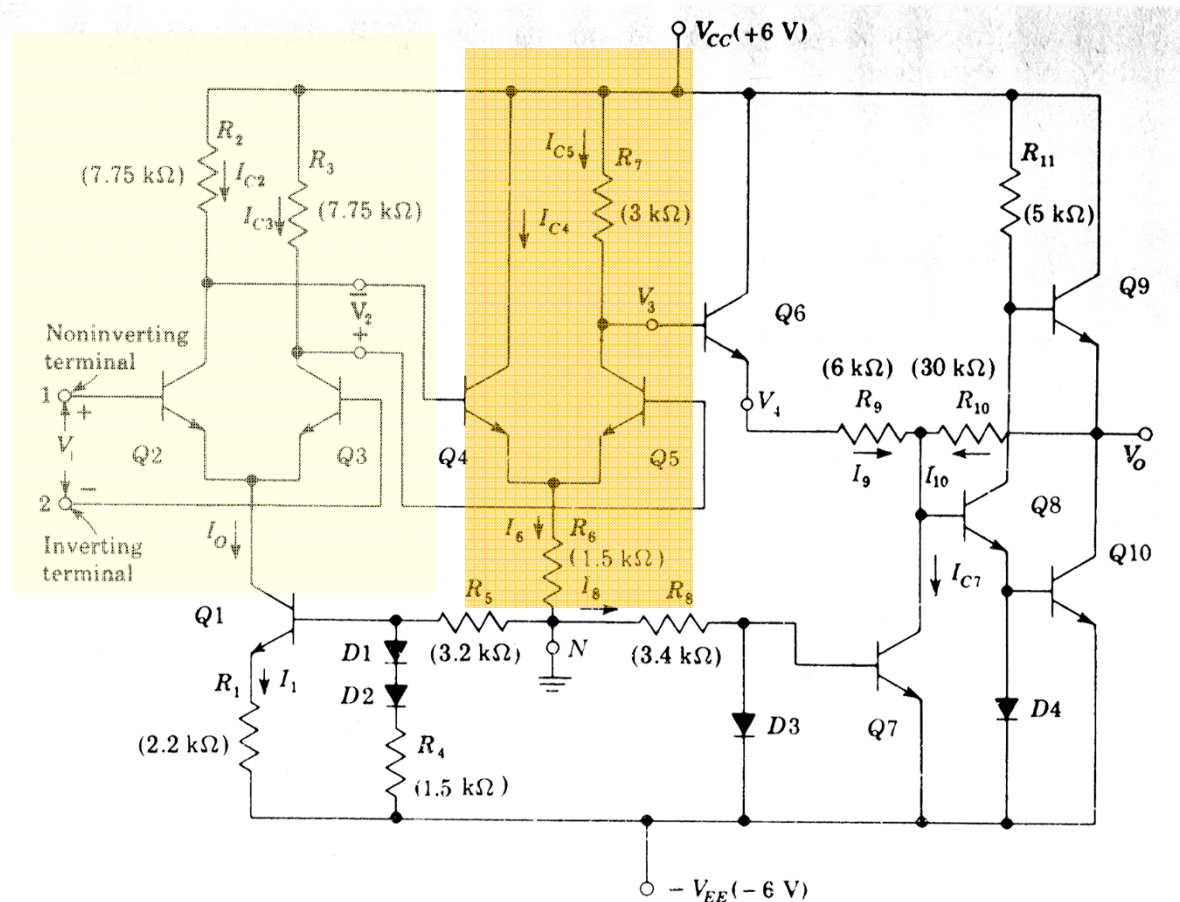- Identify circuit 'building blocks'
- Perform a dc analysis to estimate all currents and voltages
- Perform an ac analysis to estimate gain of amplifier



Motorola MC1350 operational amplifier


Differential amplifier principles

- amplifies the difference between two signals.

Ideally:-

$$v_o = A_d(v_{i1} - v_{i2})$$

 Note that signals that are common mode (CM), that is same phase, will not affect v_o .



Reality:-

Amplifier **will** amplify CM signals. We define:

Differential mode $v_{id} \equiv (v_{i1} - v_{i2})$ (1)

Common mode $v_{ic} \equiv \frac{1}{2}(v_{i1} + v_{i2})$ (2)

Why the factor ½?

Principles (contd)

$$v_{id} \equiv (v_{i1} - v_{i2})$$
$$v_{ic} \equiv \frac{1}{2}(v_{i1} + v_{i2})$$

Why the factor $\frac{1}{2}$?

No CM
signal

Consider:-

$$v_{i1} = + 50 \mu\text{V}$$
$$v_{i2} = - 50 \mu\text{V}$$

compared to

$$v_{i1} = 1050 \mu\text{V}$$
$$v_{i2} = 950 \mu\text{V}$$

**CM signal of
1000 μV**

Corresponding DM and CM inputs are

$$v_{id} = + 100 \mu\text{V}$$
$$v_{ic} = 0 \text{ V}$$

and

$$v_{id} = + 100 \mu\text{V}$$
$$v_{ic} = 1000 \mu\text{V}$$

without the factor $\frac{1}{2}$, the common mode for the second case would be considered incorrectly as 2000 μV : the average value of CM input must be used.

What is this 'common mode' signal? It is unwanted noise and interference that will be picked up on the two input pins of the amplifier - usually same in phase and magnitude.

Common-mode rejection ratio

This is a figure of merit for the amplifier which tells us how good it is at rejecting the unwanted signal (CM) relative to the one we want to amplify (DM).

First express output as a linear combination of the two inputs:

$$v_o = A_1 v_{i1} + A_2 v_{i2} \quad (3)$$

Voltage amplification factor of input 1 with input 2 grounded

Voltage amplification factor of input 2 with input 1 grounded

Then, from Eqn.s 1,2:

$$[(1) + (2)] \rightarrow v_{i1} = \frac{1}{2} v_{id} + v_{ic}$$

$$[(1) - (2)] \rightarrow v_{i2} = -\frac{1}{2} v_{id} + v_{ic}$$

Substitute in Eqn.3 to get

$$v_o = A_d v_{id} + A_c v_{ic}$$


where $A_d \equiv \frac{1}{2}(A_1 - A_2)$

$$A_c \equiv (A_1 + A_2)$$

$$(4) \quad \begin{aligned} v_{id} &\equiv (v_{i1} - v_{i2}) \\ v_{ic} &\equiv \frac{1}{2}(v_{i1} + v_{i2}) \end{aligned}$$

Interpretation

$$v_o = A_d v_{id} + A_c v_{ic}$$

 

Want $A_d \gg 1$, $A_c \rightarrow 0$ for a good diff. amp. Define:

$$CMRR = \rho = \left| \frac{A_d}{A_c} \right|$$

so Eqn.4 becomes

$$v_o = A_d v_{id} \left(1 + \frac{1}{\rho} \frac{v_{ic}}{v_{id}} \right) \quad v_o \sim A_d v_{id}$$

want ρ large. Examples of commercial op-amps:

741	$\rho = 70 - 90 \text{ dB}$	(3,000 to 30,000)
OP07	$\rho = 94 - 106 \text{ dB}$	(50,000 to 200,000)


Sometimes there are two outputs

Convention is therefore

Inputs

$$v_{i1} = \frac{v_{id}}{2} + v_{ic}$$

$$v_{i2} = -\frac{v_{id}}{2} + v_{ic}$$

 

Outputs

$$v_{o1} = \frac{v_{od}}{2} + v_{oc}$$

$$(\quad = A_d \frac{v_{id}}{2} + A_c v_{ic} \quad)$$

$$v_{o2} = -\frac{v_{od}}{2} + v_{oc}$$

$$(\quad = -A_d \frac{v_{id}}{2} + A_c v_{ic} \quad)$$


Diff. mode gain:
$$A_d = \frac{v_{o1} - v_{o2}}{v_{i1} - v_{i2}} = \frac{v_{od}}{v_{id}}$$

Common mode gain
$$A_c = \frac{v_{o1} + v_{o2}}{v_{i1} + v_{i2}} = \frac{v_{oc}}{v_{ic}}$$

$$CMRR = \rho = \left| \frac{A_d}{A_c} \right|$$

We now consider a real circuit.

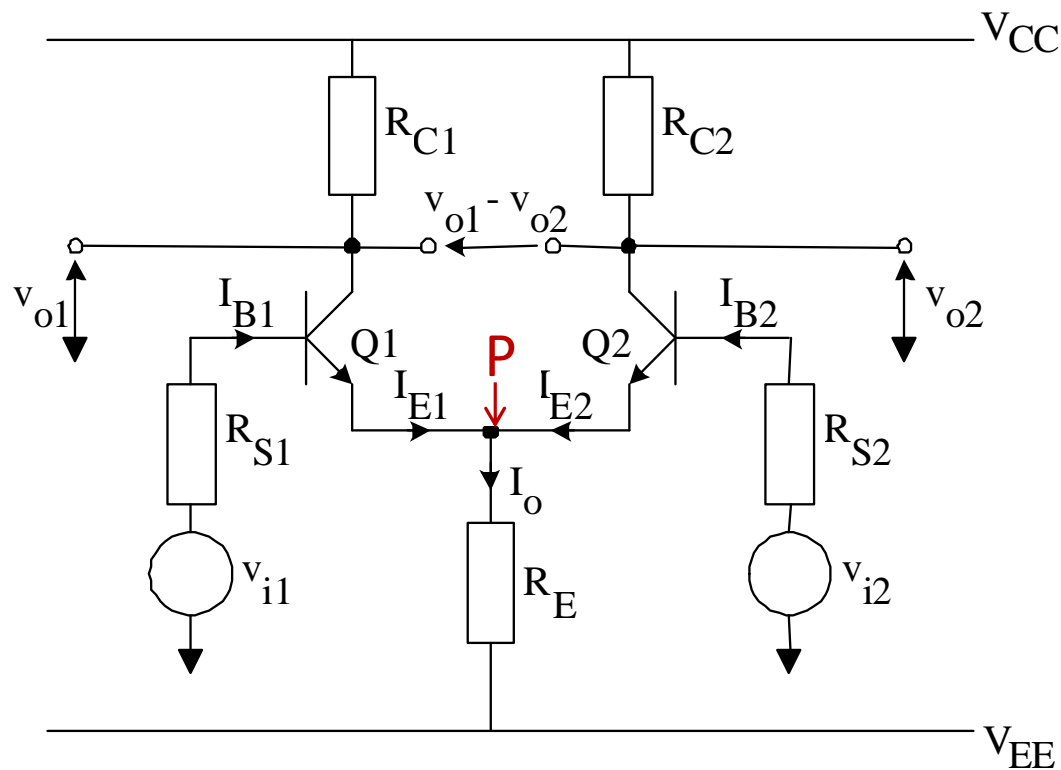The differential amplifier (or 'long-tail pair', or emitter-coupled amplifier)



d.c. conditions

($v_{i1} = v_{i2} = 0$).

Neg. supply rail biases

Q1,2 on

- R_E sets the current.
- Assume that the transistors do not saturate
- small I_B causes little voltage drop so that the base of Q1, 2 ~ 0 V.
- = Point P will be at ~ -0.7 V due to the forward biased B/E

$$I_o \approx \frac{|V_{EE}| - 0.7}{R_E}$$

Question:

Why are split supply rails used?


R_E and V_{EE} constitute a simple current source

Response to ac signals: Diff. mode

Consider the application of test sine waves to the inputs,


RECALL:
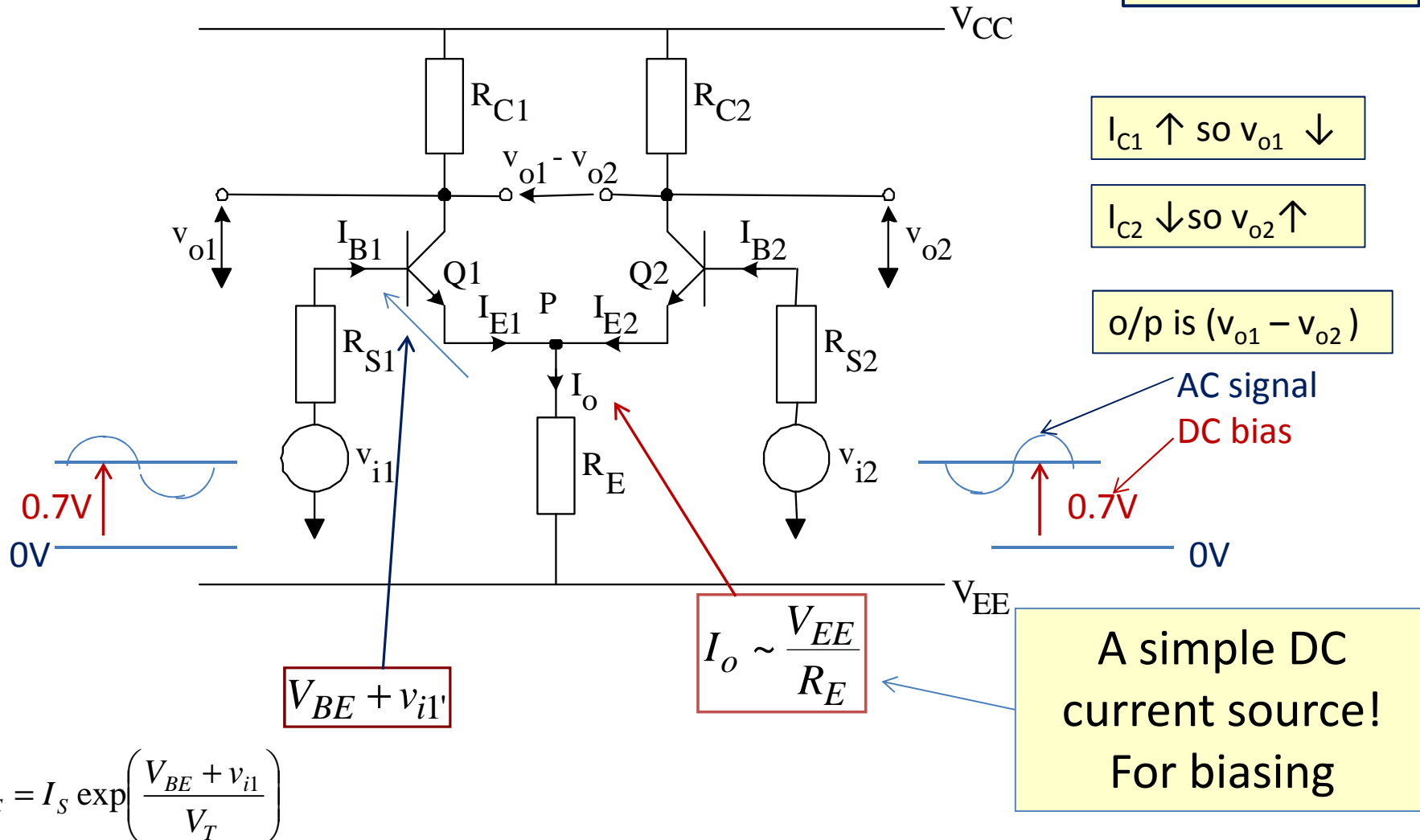
$$I_C = I_S \exp\left(\frac{V_{BE}}{V_T}\right)$$




Response to ac signals: Common mode

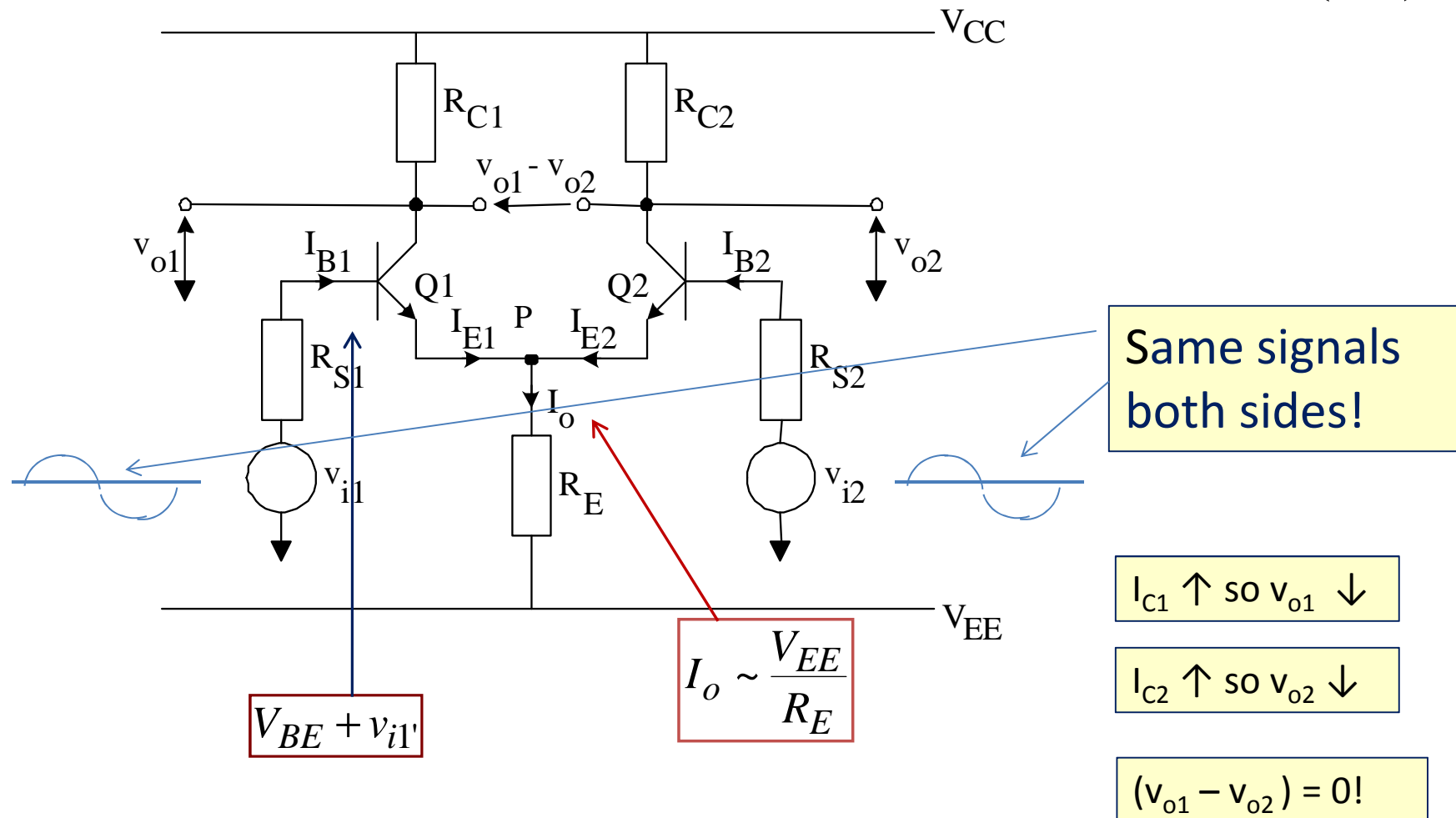Consider the application of test sine waves to the inputs, RECALL: $I_C = I_S \exp\left(\frac{V_{BE}}{V_T}\right)$




Small-signal analysis


Differential inputs

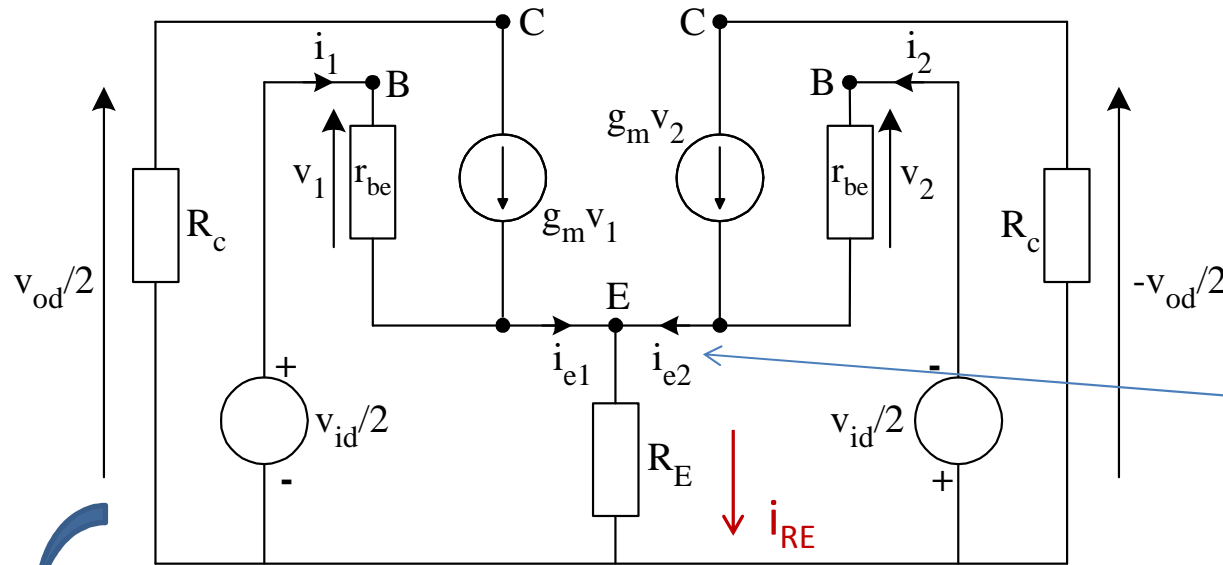

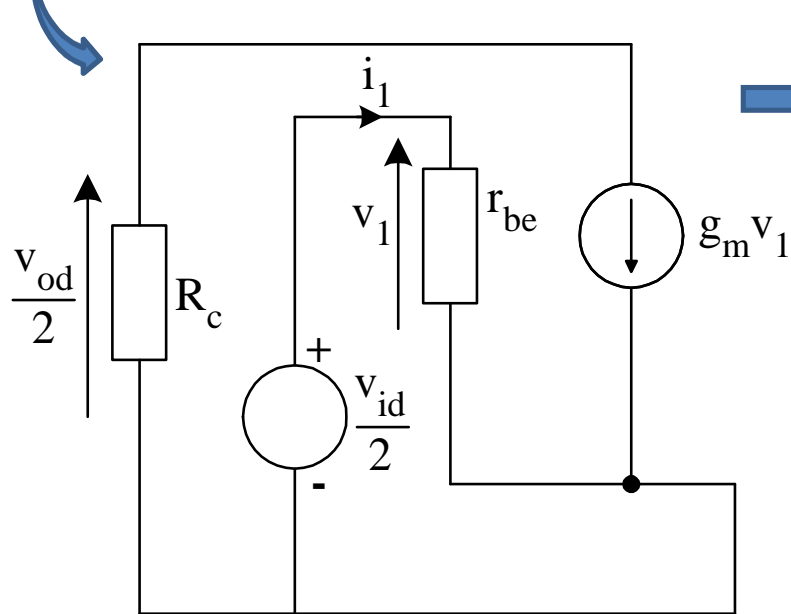Assuming identical Q's
 $i_{e1} = -i_{e2}$!
 So i_{RE} = doesn't change!
 It's an 'ac ground'



Just consider one side of the circuit

 

$$i(R_C) = -g_m v_1$$

$$\frac{v_{od}}{2R_C} = -g_m \frac{v_{id}}{2}$$

$$A_d \equiv \frac{v_{od}}{v_{id}} = -g_m R_C$$

$$A_d = -40 \left(\frac{I_o}{2} \right) R_C$$

Interpretation

$$A_d = -20I_o R_C$$


- we have assumed $R_{C1} = R_{C2} = R_C$ (see exercise 1.b at the end of the handout for another case).
- **Thus a higher bias current leads to a higher voltage gain.**
- **Taking the output single ended gives:**
$$\left\{ \begin{array}{l} A_{d1} = \frac{v_{o1}}{v_{i1} - v_{i2}} = -g_m \frac{R_{C1}}{2} \\ A_{d2} = \frac{v_{o2}}{v_{i1} - v_{i2}} = +g_m \frac{R_{C2}}{2} \end{array} \right.$$
- Note for single ended output, the gains are exactly half the voltage gain of double ended output or simple common emitter amplifier (why?).
- **Thus the voltage gain can be increased by increasing the value of collector resistor.**
- However, there is considerable constraint because of the need to avoid saturation in the transistors. This will lead us to use an 'active load' (see later lecture).

Design issues

The 'differential' input resistance of the D-M configuration is given approximately by:

$$R_{id} = \frac{v_{id}}{i_i} = \frac{2v_1}{i_i} = 2r_{be}$$
 
$$R_{id} = 2r_{be} = 2 \frac{\beta_o}{g_m} = 2 \frac{\beta_o}{40I_C} = \frac{\beta_o}{10I_o}$$



thus the operating current must be chosen small to increase the input resistance.

$$R_{id} = \frac{\beta_o}{10I_o} \quad \text{(Eqn. 1)}$$

BUT want bias, I_c large for high gain!!

$$A_d = -20I_o R_C \quad \text{(Eqn.2)}$$

⇒ We have an engineering trade-off as I_o must be large for high voltage gain (Eqn.2) and small for large input resistance (Eqn. 1).


Alternatively, R_{id} can be increased by the following methods

1. Use Darlington transistors on the input

Effectively: $\beta_o \rightarrow \beta_o^2$

$$r_{be} \rightarrow \beta_o^2 / g_m$$

Large increase in input resistance

 

2. Use super gain transistors

Very narrow base transistors – enhances collector current
typically $\beta_o \sim 5,000$

$$\text{For } I_C = 1\mu\text{A}, r_{be} = \beta_o / g_m = 5,000 / 40 \times 1\mu\text{A} = \mathbf{125\text{ M}\Omega}$$

3. Use FET input transistors

JFET


$$R_{id} \sim 10^8 \Omega$$

MOSFET

$$R_{id} \sim 10^{10} - 10^{15} \Omega$$




Response to ac signals: Common mode

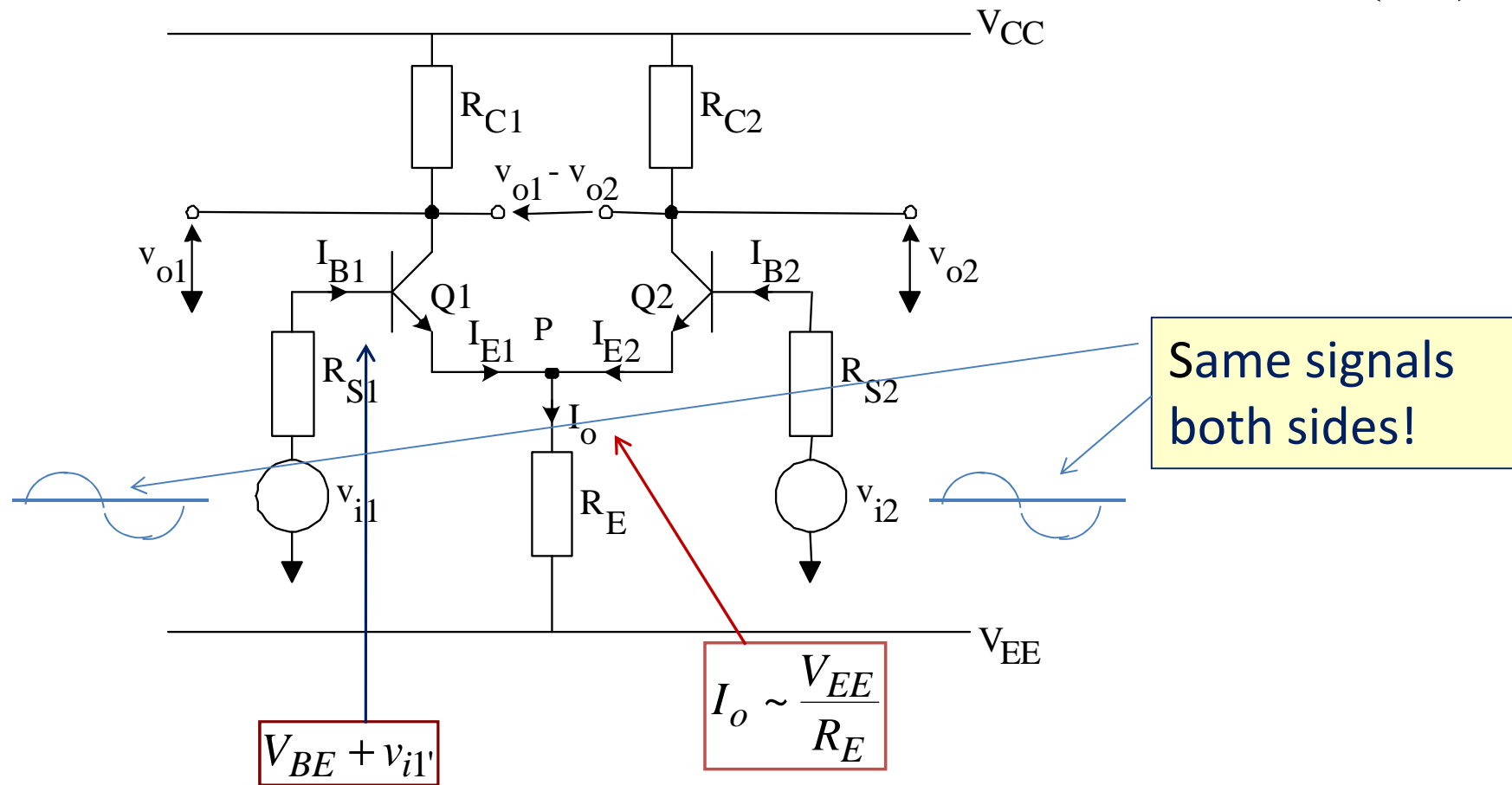Consider the application of test sine waves to the inputs, RECALL: $I_C = I_S \exp\left(\frac{V_{BE}}{V_T}\right)$




Small-signal analysis

Common-mode inputs

 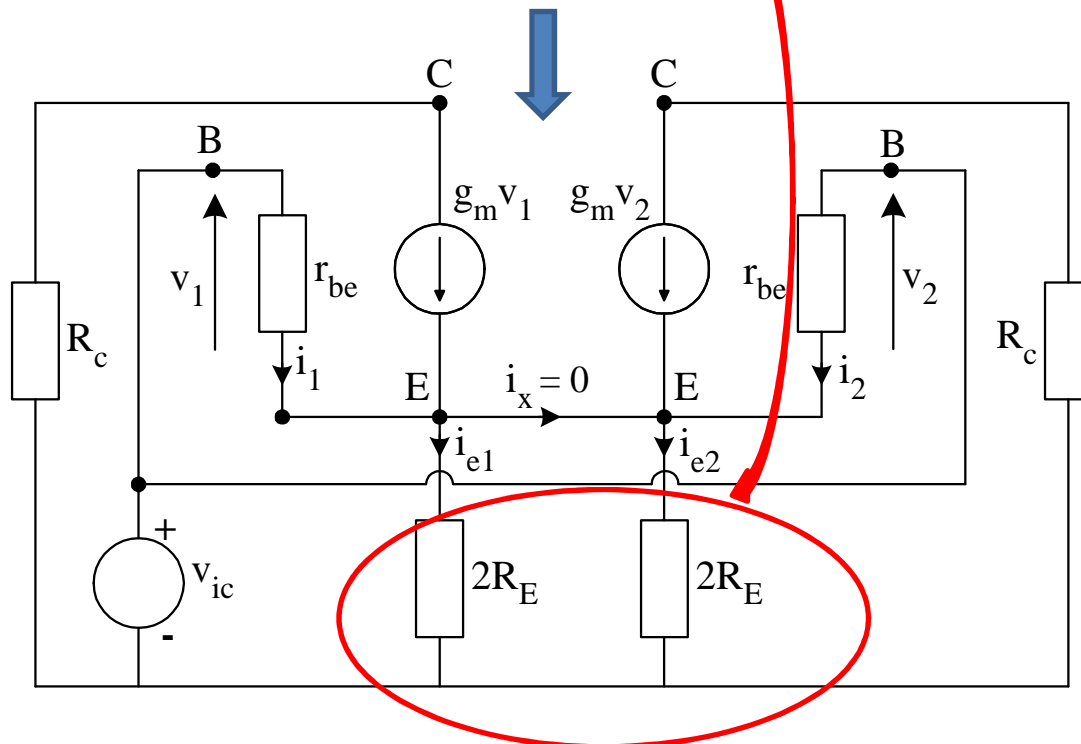 

CM - analysis

 

recognise this as the **CE-ED** configuration (see Part 2 notes).

Common mode signals therefore "see" the emitter resistor which thus severely degrades the common-mode gain.

Following the earlier analysis for CE-ED:

common mode input resistance can be shown to be

$$R_{ic} = \frac{v_{ic}}{i_i}$$

$$= r_{be} + 2(1 + \beta_o)R_E$$

$$A_{Vc} = -\frac{R_C g_m}{1 + 2(g_m + r_{be}^{-1})R_E}$$

$$= -\frac{R_C \beta_o}{r_{be} + 2(1 + \beta_o)R_E}$$

$g_m = \frac{\beta_o}{r_{be}}$

\Rightarrow Thus R_E must be large to make A_{Vc} small. However, R_E is also responsible for setting the d-c. bias condition !?

Design Example 3


Work out values for R_E and R_C to give a bias current of 0.1 mA with $V_o = 0$ V (DC), $\beta_o = 100$

Voltage drop across R_E ?

$$R_E = \frac{V_{EE} - |-0.6|}{0.1\text{mA}} = \frac{4.4}{0.1} \text{ k}\Omega \quad \mathbf{44 \text{ k}\Omega}$$

Voltage drop across R_C ?
 
$$R_C = \frac{V_{CC} - 0}{50 \mu\text{A}} = \frac{5}{50} \text{ M}\Omega \quad \mathbf{100 \text{ k}\Omega}$$



Now work out the differential input resistance and voltage gain ($\beta_o = 100$)

$$R_{id} = 2 \times r_{be} = 2\beta_o / g_m \quad g_m = 40 \times 50 \mu\text{A} = 2 \text{ mA/V} \quad R_{id} = 200/2 \text{ k} = \mathbf{100 \text{ k}\Omega}$$

$$A_{vd} = g_m \times \text{ac load}/2 \quad A_{vd} = g_m \times R_C / 2 \quad A_{vd} = 2\text{m} \times 100\text{k}/2 = \mathbf{100}$$

Now work out the common-mode voltage gain


$$A_{VC} = \frac{100\text{k} \times 100}{50\text{k} + 2(1 + 100)44\text{k}} \quad \mathbf{\sim 1}$$

$$A_{VC} = \frac{R_C \times \beta_o}{r_{be} + 2(1 + \beta_o)R_E}$$

CMRR?

Single-ended output

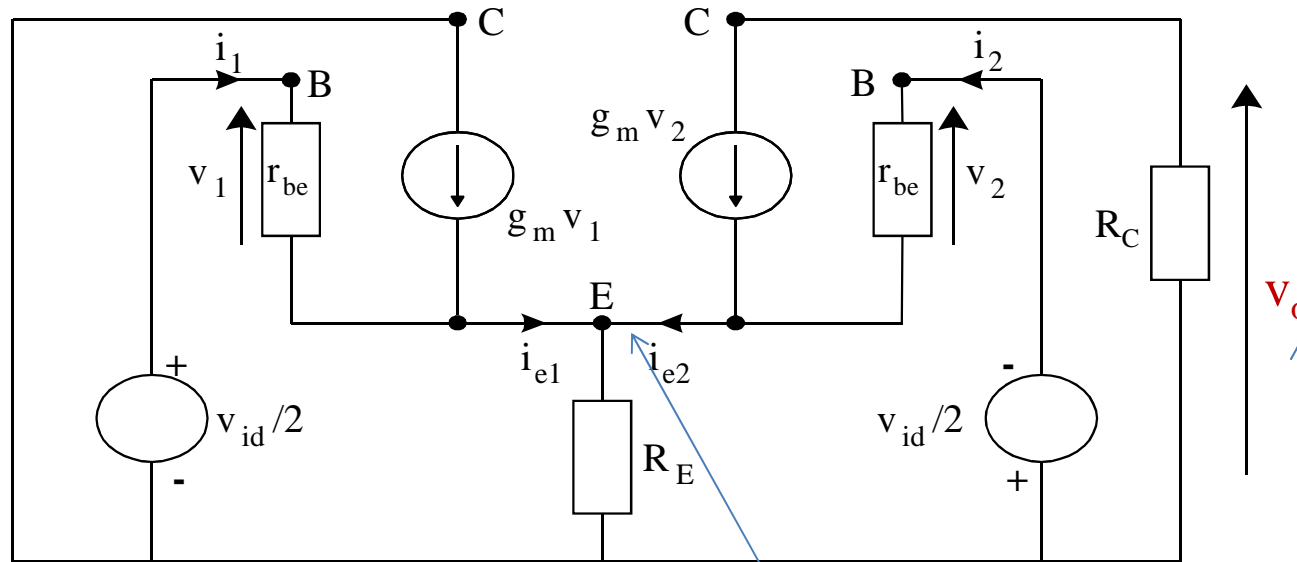Show that the voltage gain is $\frac{v_o}{v_{id}} = \frac{g_m R_C}{2}$



ac ground

So

$$v_2 = \frac{v_{id}}{2}$$

$$v_o = -g_m v_2 \times R_C$$

$$v_o = -g_m R_C \times \frac{-v_{id}}{2}$$

$$\frac{v_o}{v_{id}} = \frac{g_m R_C}{2}$$

Schematic entry in PSPICE

DC Analysis:


Bias current is 0.1 mA

Collector currents of Q1,2 a bit different


$$I_{C1} > I_{C2}$$

- Early Effect! (see Part 1)
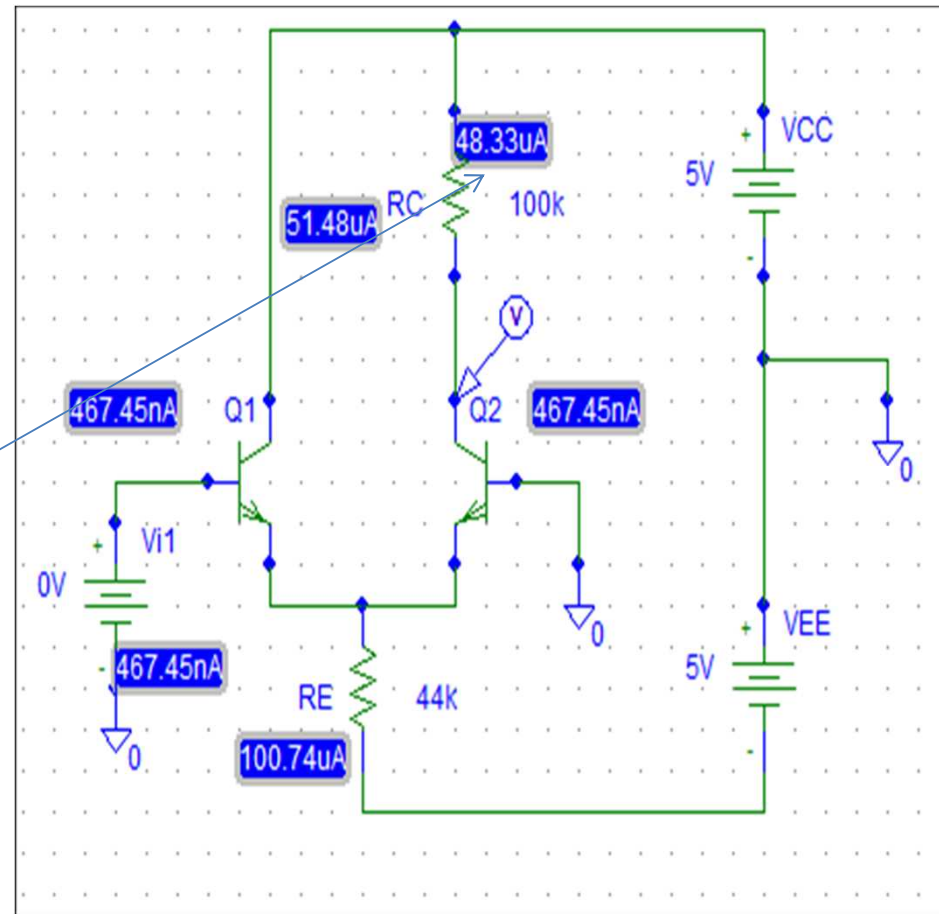
$$I_{C2} = 48 \mu A \text{ (not } 50 \mu A)$$




Output characteristics

 

IDEAL - FLAT

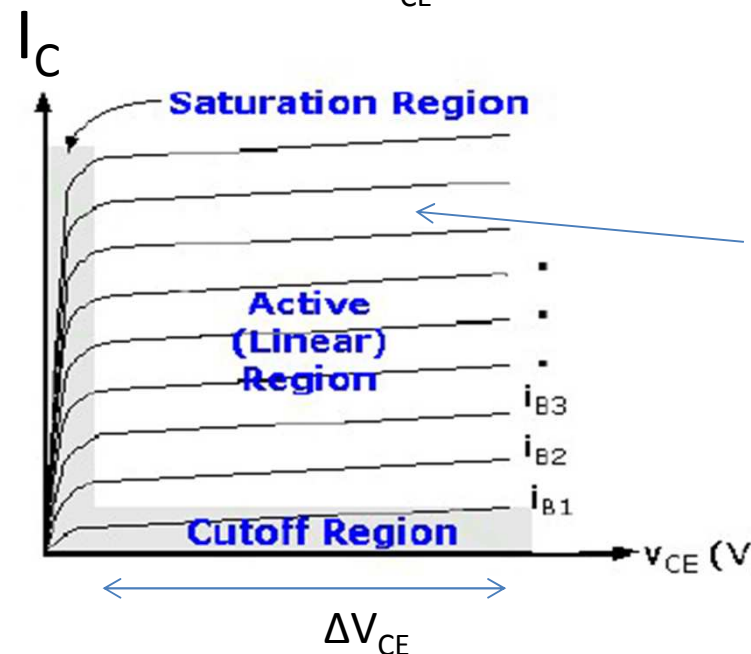Collector current is independent of V_{CE}




REAL – NOT FLAT

Due to the Early Effect

Collector current is weakly dependent on V_{CE}
 I_C increases with increasing V_{CE}

DC Voltage levels

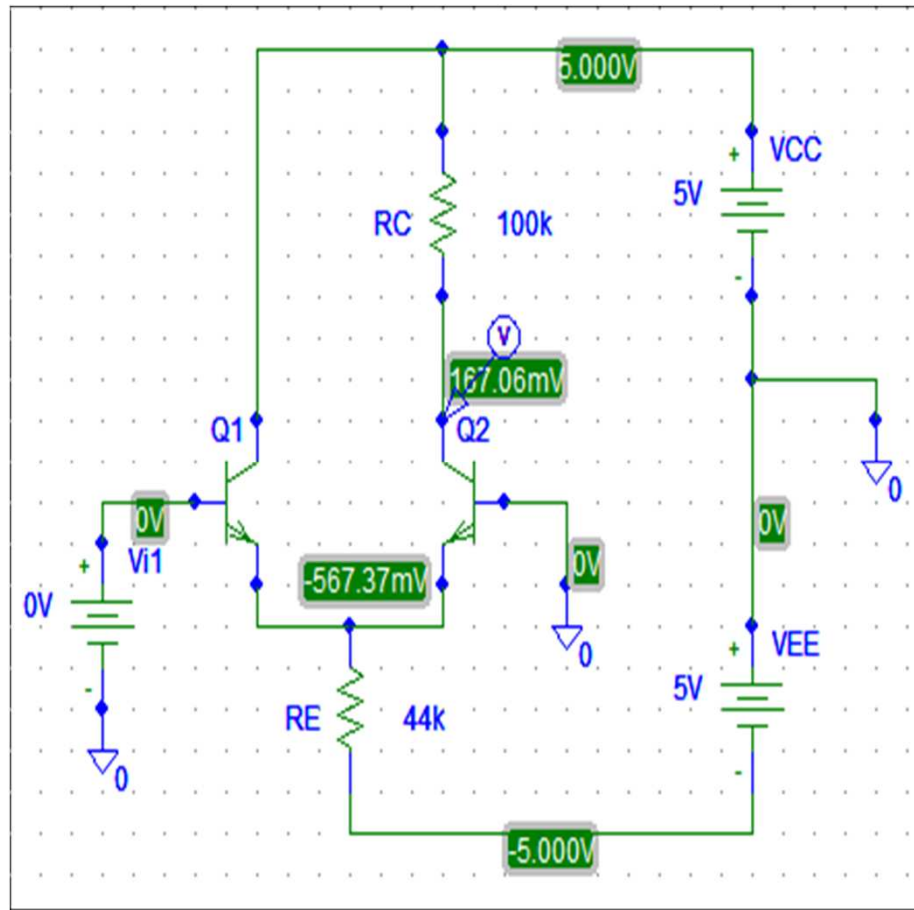

Output voltage ~ 170 mV (not 0 V)

$$V_{BE} (Q1, 2) = 0.567 \text{ V} \sim 0.6 \text{ V}$$

$$V_{CE} (Q1) = 5 - (-0.6) = 5.6 \text{ V}$$

$$V_{CE} (Q2) = 0.17 - (-0.6) = 0.77 \text{ V}$$

$$V_{CE} (Q1) \gg V_{CE} (Q2)$$



ideal transistors were assumed.

Flat output characteristic

Assume equal collector currents

Early Effect is modelled in SPICE

  Transfer characteristic: Apply a voltage sweep to V_{i1}



Check

- Gain is 87 but we predicted 100
- Reason for poor agreement?
- We estimated $I_C = 50 \mu\text{A}$ but Early Effect results in $48 \mu\text{A}$
- Re-calculate $g_m = 40 \times 48 \mu\text{A} = 1.92 \text{ mA/V}$ (not 2 mA/V !)
- Re-calculate Diff. Gain = $g_m \times R_C / 2 = 1.92 \times 50 = \mathbf{96}$

Simple theory predicts gain to circa 4%

Conclusions

We require

- a better bias circuit to replace R_E , which will allow us to set the current I_o , independently of the resistance in the 'tail'.
- We would also like such a bias circuit to exhibit a very large dynamic resistance to give high common mode rejection ratio (CMRR).
- a circuit to replace the collector resistors, which will present a high resistance (for high gain) without creating a large voltage drop which causes the transistors to saturate and upsets the symmetry of the voltage swing.

MCQ

The main function of the differential amplifier can be best described as:

- a) Provide more gain
- b) Increase input resistance
- c) Reject unwanted interference signals
- d) Make life more complicated for us

MCQ

The main function of the differential amplifier can be best described as:

- a) Provide more gain
- b) Increase input resistance
- c) Reject unwanted interference signals
- d) Make life more complicated for us

End of Part 3

- Next time
 - Look at better ways of biasing the diff.amp to give high CMRR
 - Decouple ac and dc design aspects