

Digital Electronics and Microprocessor Systems (ELEC211)

Dave McIntosh and Valerio Selis

dmc@liv.ac.uk

v.selis@liv.ac.uk

Digital 5: CPLDs and FPGAs
Shannon's expansion

Outline

- Complex Programmable Logic Devices (CPLDs)
- Field Programmable Gate Arrays (FPGAs)
- Shannon's expansion

Previous material

MUX ✓

PLA, PAL ✓


Flip-flops ✓

Karnaugh maps ✓


Use VITAL!:

- Stream lectures
- Handouts
- Notes and Q&A each week
- Discussion Board
- Exam resources

www.liv.ac.uk/vital

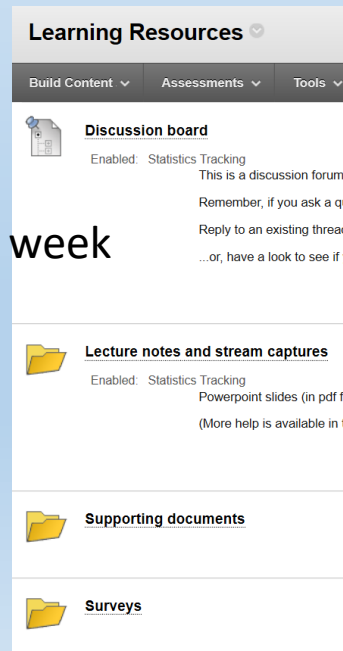

 Course textbook – please borrow and use it! ➡




Complex Programmable Logic Devices (CPLD)



Xilinx XCR3064XL

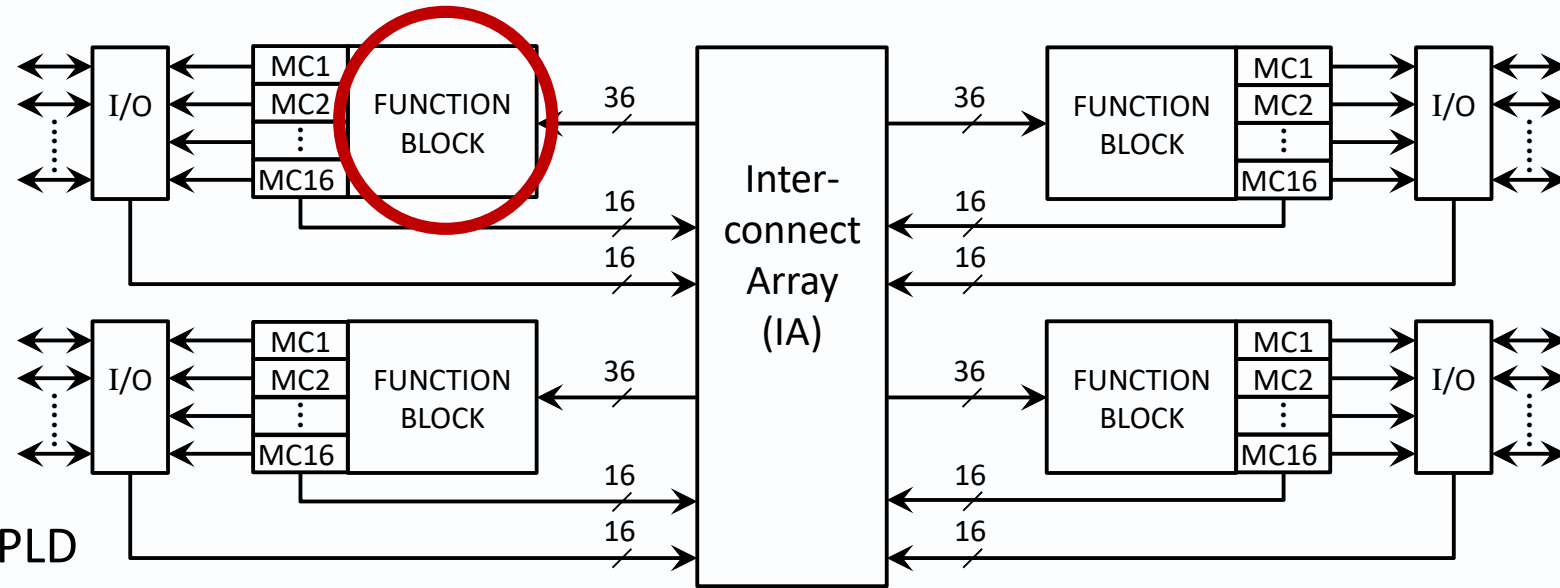
Complex Programmable Logic Devices (CPLDs)



Xilinx XCR3064XL CPLD

Each Function Block is a programmable AND-OR array, configured as a PLA.

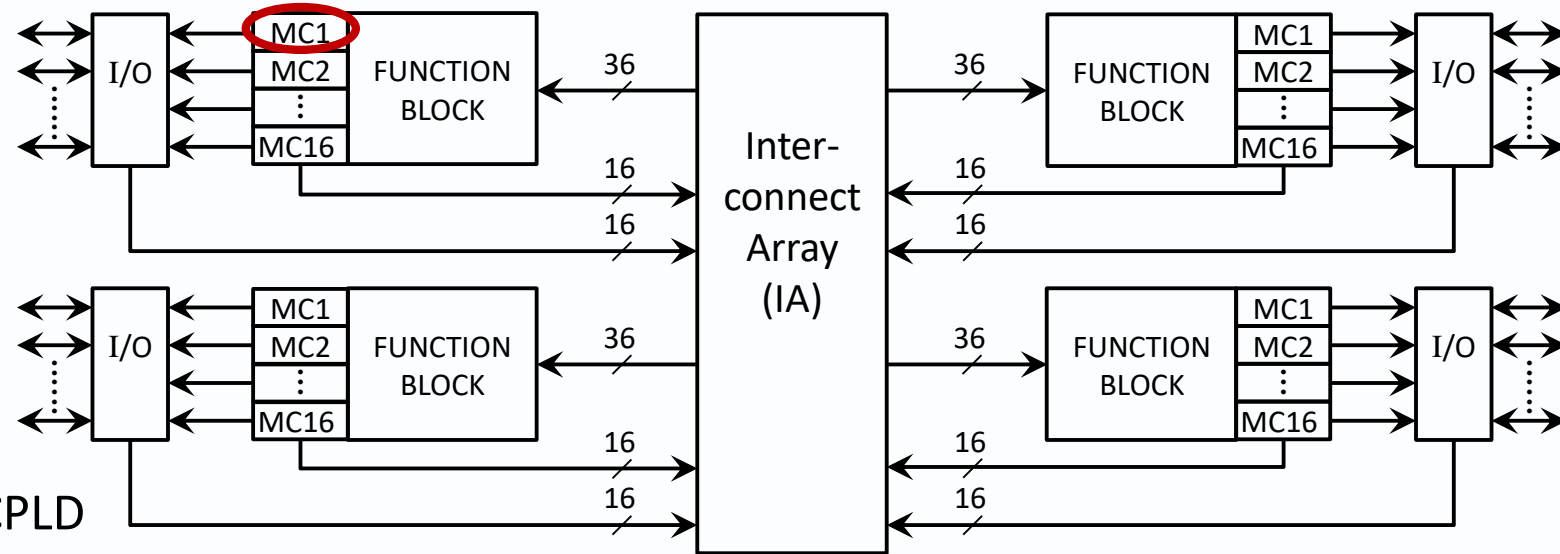Complex Programmable Logic Devices (CPLDs)




Xilinx XCR3064XL CPLD

Each **Macrocell (MC)** contains a:

- **Flip-Flop** and
- **multiplexers**

...that route signals from the function block to the **Input/Output (I/O)** block or to the **interconnect array (IA)**

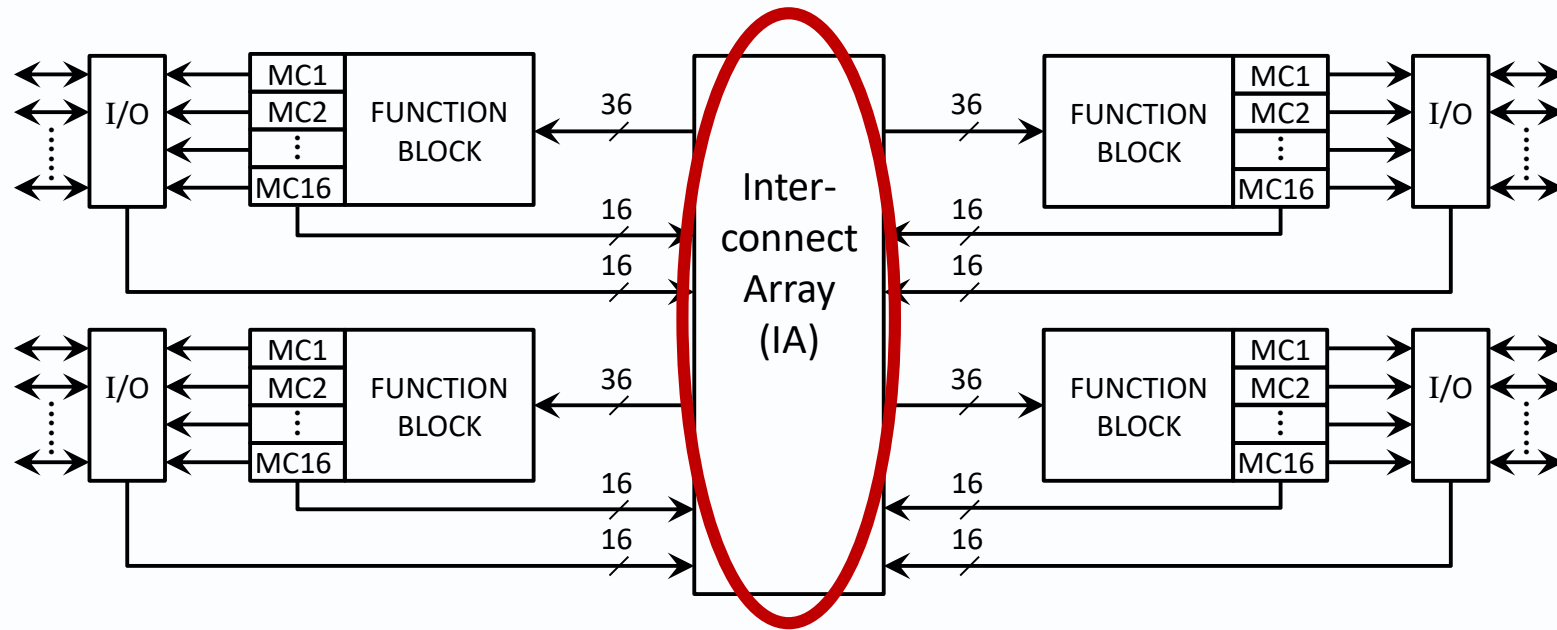Complex Programmable Logic Devices (CPLDs)




The **IA** selects signals from the **Macrocell outputs** or **I/O blocks** and connects them back to **function block inputs**.

Signal generated in one function block → can input to any other function block

The I/O blocks provide an interface between the bi-directional I/O pins and the interior of the CPLD

Clock enable (side-note)

 


Clock enable (CE):

- When $CE=1$, normal flip-flop operation on active edge
- When $CE = 0$, clock disabled, no state change ($Q^+=Q$)


CPLD Function Block & Macrocell

36 inputs from IA

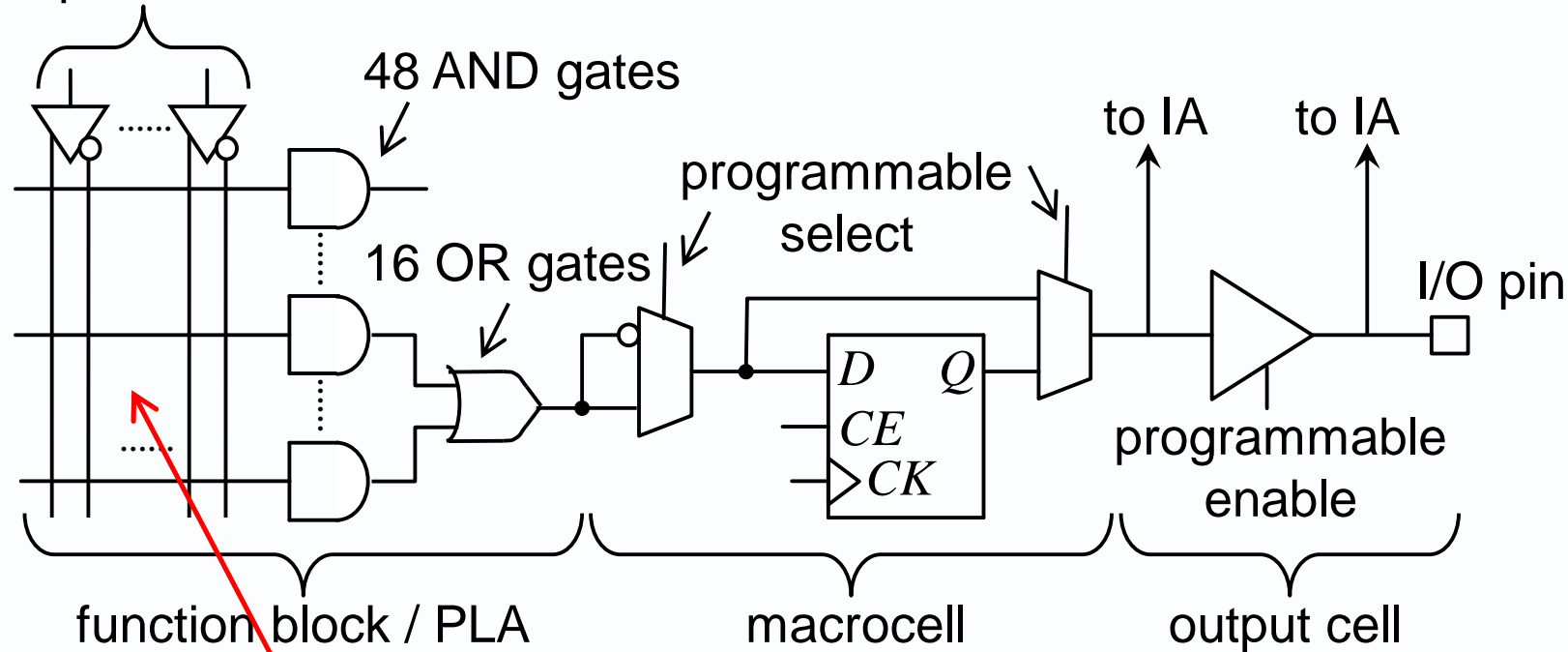


How is a signal (generated in the PLA) routed to an I/O pin via a macrocell?

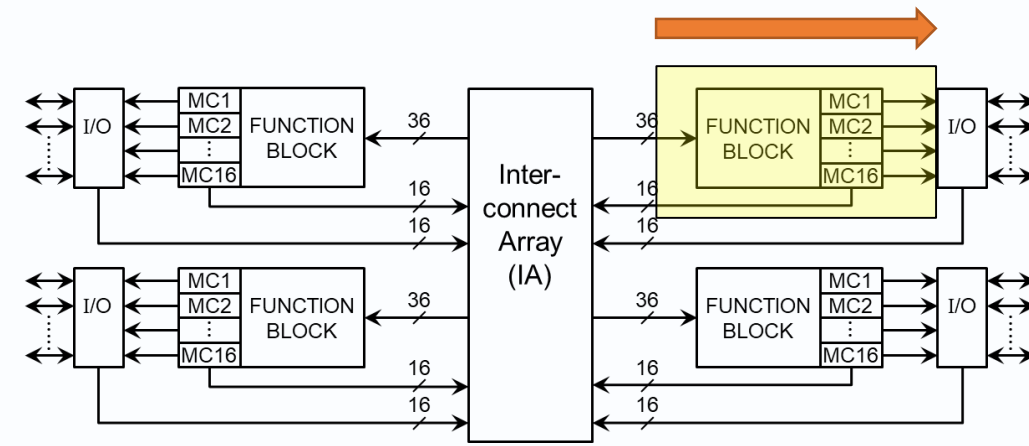- Any of the 36 inputs from the IA can be connected to any of the 48 AND gates.




CPLD Function Block & Macrocell

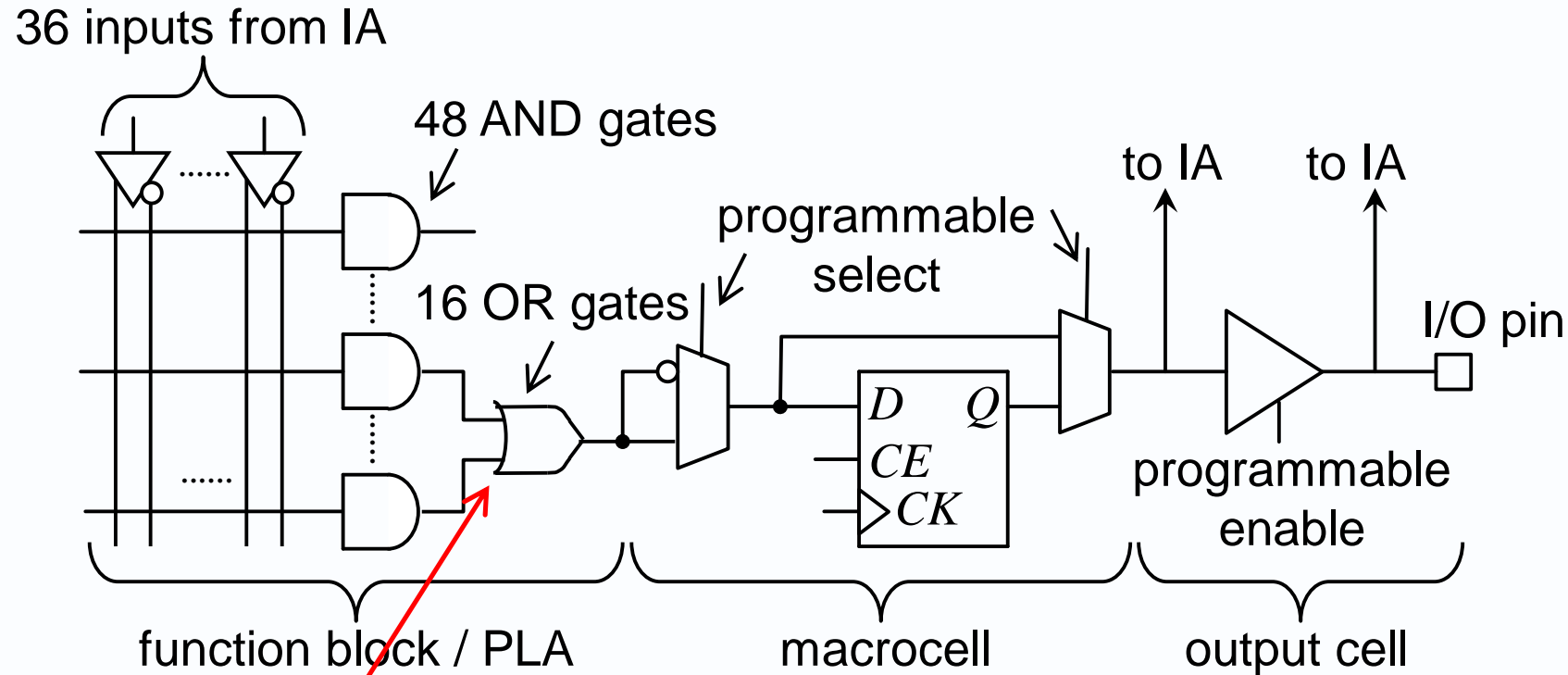


How is a signal generated in the PLA routed to an I/O pin via a macrocell?

 - Each OR gate can accept up to 48 product terms from the AND array.




CPLD Function Block & Macrocell

36 inputs from IA

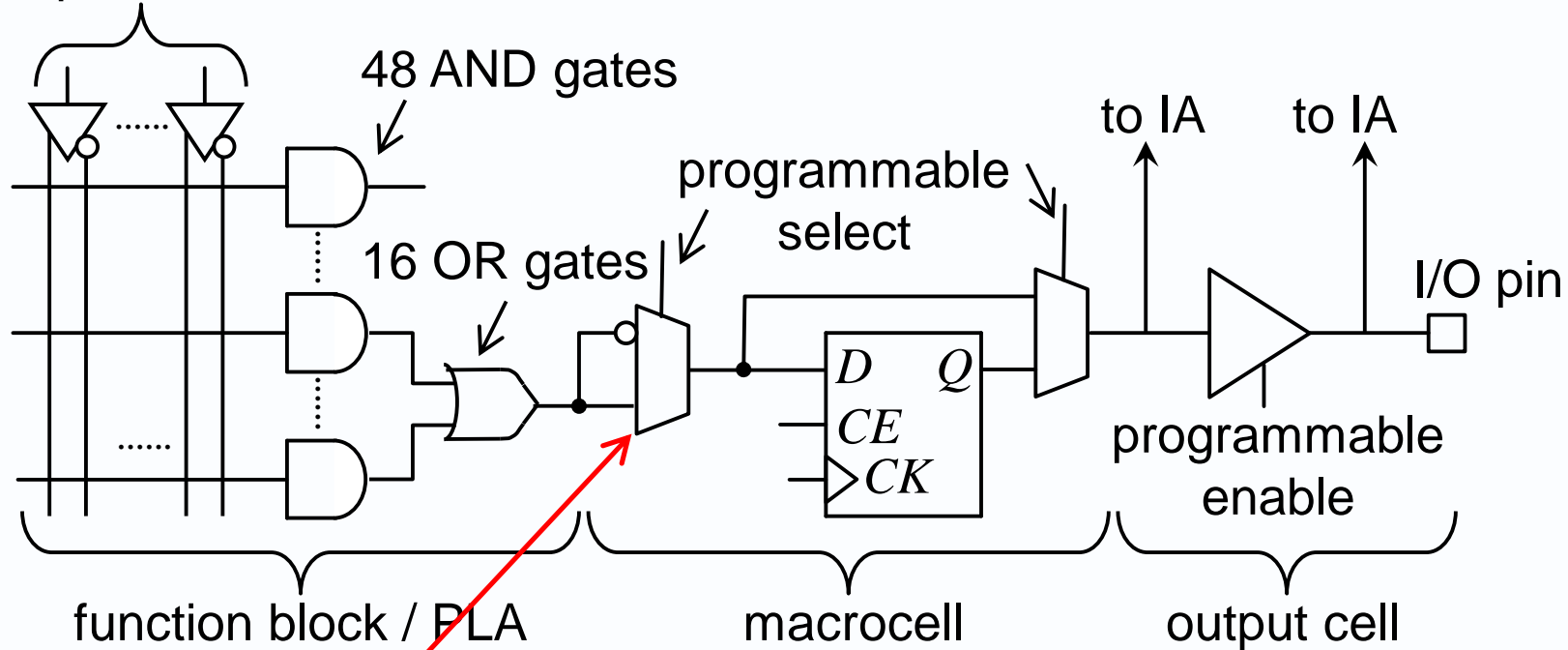


How is a signal generated in the PLA routed to an I/O pin via a macrocell?

 - The first Mux can be programmed to select the output of the OR gate or its inverse.




CPLD Function Block & Macrocell

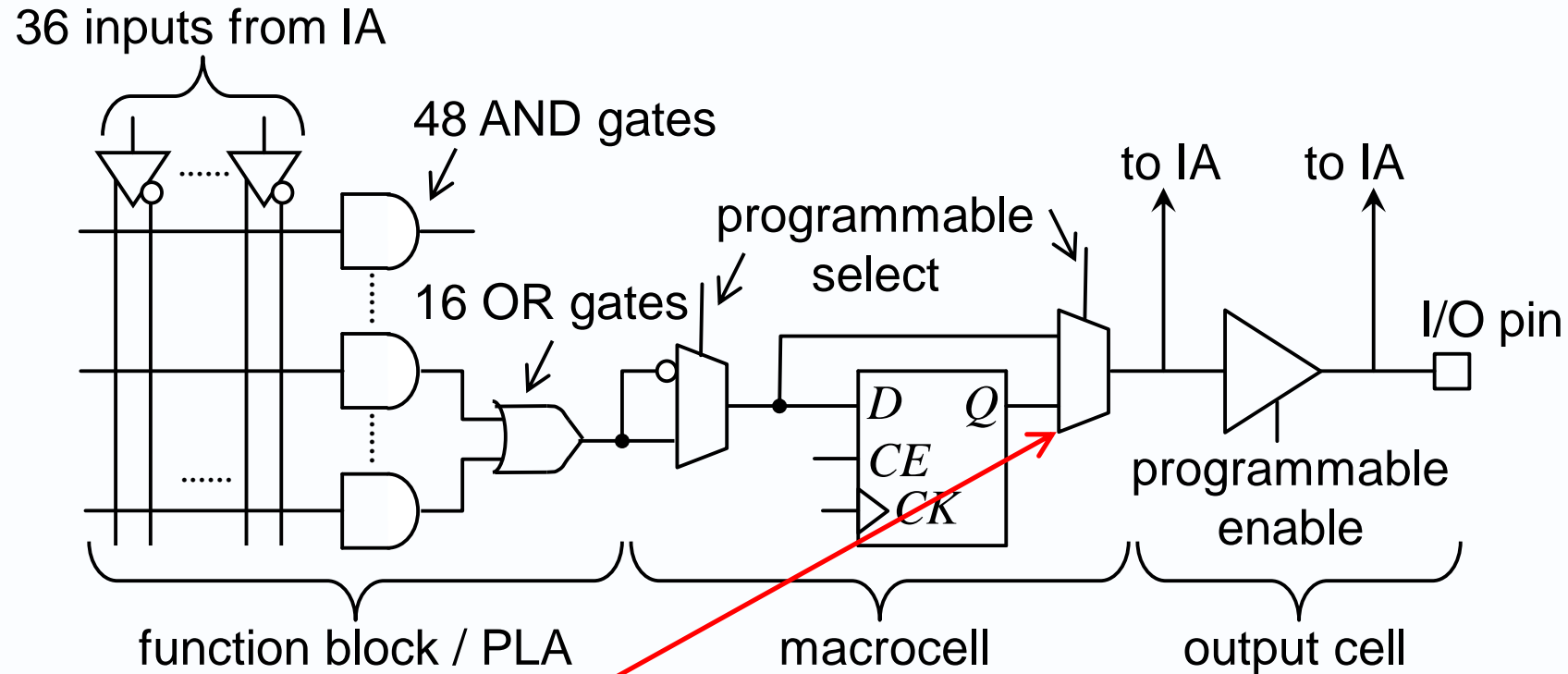


How is a signal generated in the PLA routed to an I/O pin via a macrocell?

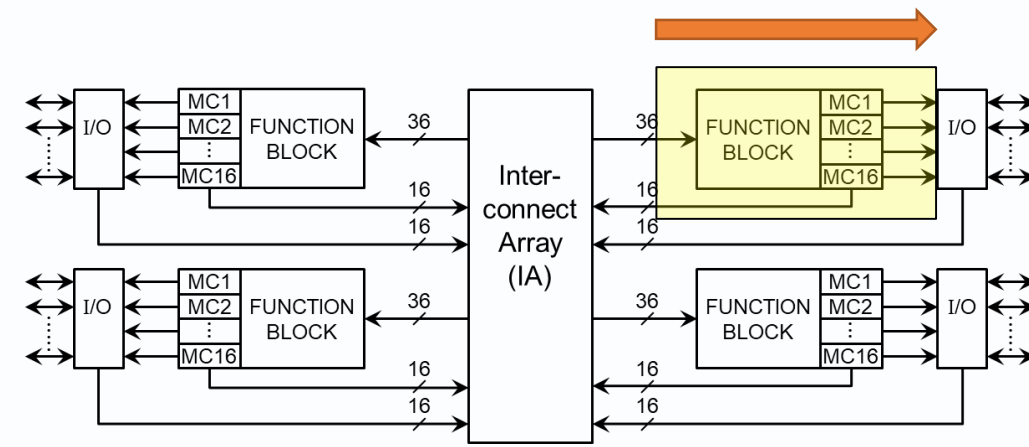- The second Mux can be programmed to select either the combinational output or the flip-flop output (Q).




CPLD Function Block & Macrocell

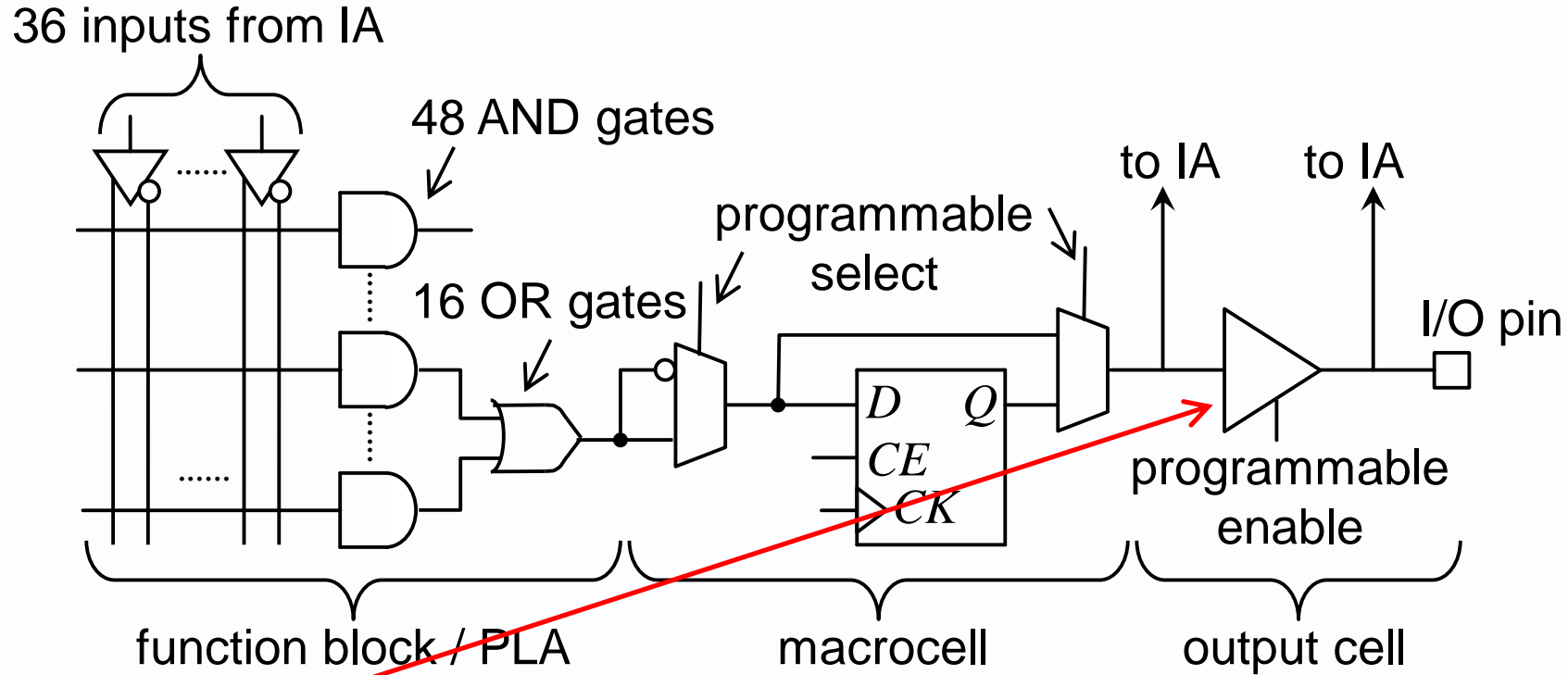

How is a signal generated in the PLA routed to an I/O pin via a macrocell?

 - The tri-state buffer defines the I/O pin as input (buffer disabled) or output
- Sophisticated CAD software is available for fitting logic circuits into a CPLD



Field Programmable Gate Arrays (FPGA)

This material will take you through a Altera® DE1 Development and Education board (Figure 1). Featuring an Altera Cyclone® II 2C20 FPGA, the DE1 board is designed for university and college laboratory use. It is suitable for a wide range of exercises in courses on digital logic and computer organization, from simple tasks that illustrate fundamental concepts to advanced designs.

 


Figure 1 Altera DE1 Board

The following hardware is provided on the DE1 board:

- Altera Cyclone® II 2C20 FPGA device
- Altera Serial Configuration device – EPCS4
- USB Blaster (on board) for programming and user API control; both JTAG and Active Serial (AS) programming modes are supported
- 512-Kbyte SRAM
- 8-Mbyte SDRAM
- 4-Mbyte Flash memory

Altera DE1 board

Cyclone II 2C20 FPGA


From supporting material for
Experiment 28, 2018/19

Field Programmable Gate Arrays (FPGA)

An FPGA is an IC that contains an array of identical logic cells.

The I/O blocks connect the Configurable Logic Blocks (CLBs) to IC pins

 The I/O blocks, the CLBs and the interconnection between CLBs are programmable



Simplified CLB (Configurable Logic Block)


This (simplified) CLB contains 2 function generators, 2 flip-flops, and multiplexers for routing signals within the CLB

The function generators are implemented as **lookup tables (LUT)**.

A 4-input LUT is essentially a reprogrammable ROM with 16 1-bit words.

The CLB has two combinational outputs (X, Y) & two flip-flop outputs (XQ, YQ).

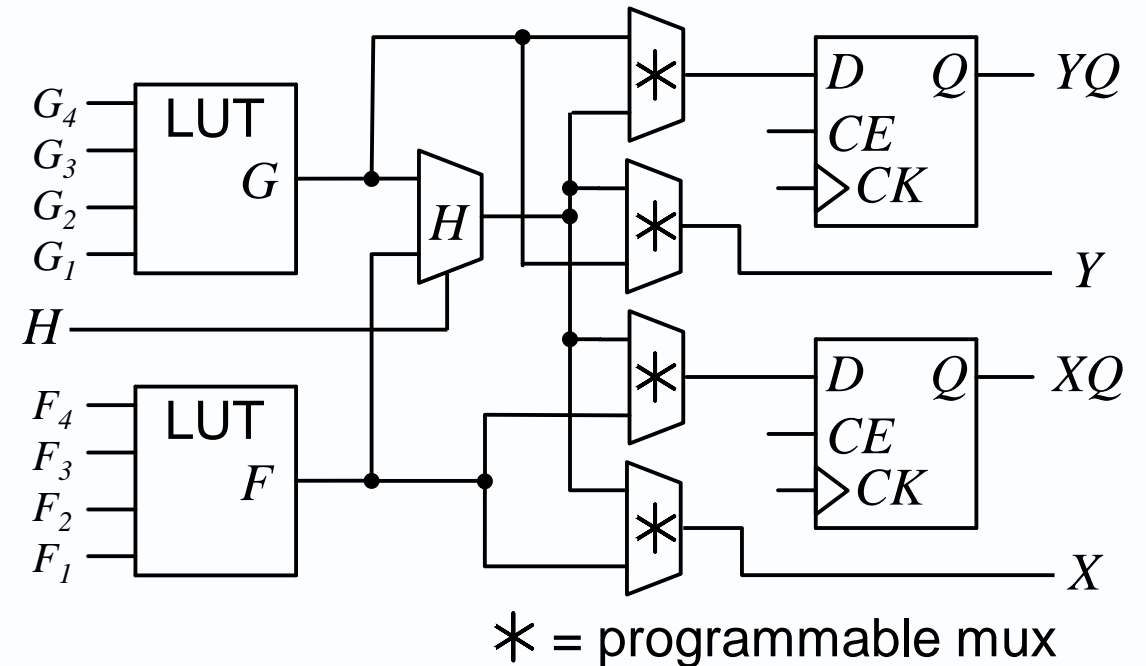X and Y outputs & the flip-flop inputs are selected by the programmable Multiplexers (the control inputs are programmed when the FPGA is configured)




Implementing a (LUT) function generator

0 or 1 in the squares represents the bits stored in the LUT. These bits enable particular minterms.

A function with only one minterm or with as many as 15 minterms requires a single function generator

e.g.

 

$$F = abcd \quad \text{or}$$

$$F = \bar{a}\bar{b}\bar{c}\bar{d} + \bar{a}b\bar{c}d + a\bar{b}\bar{c}d + \bar{a}bcd + a\bar{b}c + abc + ab\bar{c} + \bar{a}\bar{b}cd$$

Claude E. Shannon

C. Shannon, 1916 -2001,
American mathematician &
electronic engineer, known as
the 'Father of Information
Theory'.

Also, in 1937 he developed
digital circuit design theory as
an MSc student at MIT;
described as "possibly the
most important, & also the
most famous, MSc of the
century."



Shannon's theorem

$$\begin{aligned} f(a, b, c, d) &= c'd' + a'b'c + bcd + ac' \\ &= a'f_0 + af_1 \text{ (our goal)} \end{aligned}$$

Here's how
we do it:

		<i>ab</i>			
		00	01	11	10
<i>cd</i>	00	1	1	1	1
	01	0	0	1	1
	11	1	1	1	0
	10	1	0	0	0

f

		<i>a=0</i>		<i>a=1</i>	
		00	01	11	10
<i>cd</i>	00	1	1	1	1
	01	0	0	1	1
	11	1	1	1	0
	10	1	0	0	0

f_0 f_1

$$f = a'(c'd' + b'c + cd) + a(c' + bd)$$

Example: Shannon's expansion (decomposition)

Decompose the following function into 2 functions, one for a' and the other for a .

$$\begin{aligned} f(a, b, c, d) &= a'c'd' + abd + bcd + b'cd' + acd' \\ &= a'f_0 + af_1 \end{aligned}$$

Method

$$\begin{aligned} f(a,b,c,d) &= a'c'd' + abd + bcd + b'cd' + acd' \\ &= a'(\dots) + a(\dots) \end{aligned}$$

$ab \backslash cd$					
		00	01	11	10
00					
01					
11					
10					

f

$ab \backslash cd$		$a=0$		$a=1$	
		00	01	11	10
00					
01					
11					
10					

$f_0 \quad f_1$

Answer

$$\begin{aligned} f(a,b,c,d) &= a'c'd' + abd + bcd + b'cd' + acd' \\ &= a'(c'd' + b'd' + bcd) + a(cd' + bd) \end{aligned}$$


$ab \backslash cd$					
		00	01	11	10
00	1	1	0	0	
01	0	0	1	0	
11	0	1	1	0	
10	1	0	1	1	

f

$ab \backslash cd$		$a=0$		$a=1$	
		00	01	11	10
00	1	1	0	0	
01	0	0	1	0	
11	0	1	1	0	
10	1	0	1	1	

$f_0 \quad f_1$

 Realization of 5-variable functions with Function Generators



- Any 5-variable function can be realized using two 4-variable function generators and a 2-to-1 mux.

$$\begin{aligned} f(a, b, c, d, e) &= a'f(0, b, c, d, e) + af(1, b, c, d, e) \\ &= a'f_0 + af_1 \end{aligned}$$

Example

Decompose the following function into 2 functions, one for a' and the other for a .

$$\begin{aligned} f(a, b, c, d, e) &= b'c'd' + a'be + b'cde' + ab'd' + bcde \\ &= a'f_0 + af_1 \end{aligned}$$

Answer

$$f = (a + a')b'c'd' + a'be' + (a + a')cde' + ab'd' + (a + a')bcde$$

$$\begin{aligned} f(a,b,c,d,e) &= b'c'd' + a'be + b'cde' + ab'd' + bcde \\ &= a'(b'c'd' + be + b'cde') + a(b'd' + b'ce' + bcde) \end{aligned}$$

$bc \backslash de$					
		00	01	11	10
00	1	0	0	0	
01	1	0	1	1	
11	0	0	1	1	
10	0	1	0	0	


$a=0$

bc de		00	01	11	10
		00	01	11	10
00	1	1	0	0	
01	1	1	0	0	
11	0	0	1	0	
10	0	1	0	0	

$a=1$

Realization of 6-variable functions with Function Generators

 Any 6-variable function can be realized using four 4-variable function generators and three 2-to-1 mux.



$$g(a, b, c, d, e, f) = a'b'g(0, 0, c, d, e, f) + a'bg(0, 1, c, d, e, f) \\ + ab'g(1, 0, c, d, e, f) + abg(1, 1, c, d, e, f)$$

Summary and suggested reading

- CPLDs (Section 9.7)
- FPGAs (Section 9.8)
- Shannon's expansion

Roth and Kinney *Fundamentals of Logic Design*

