
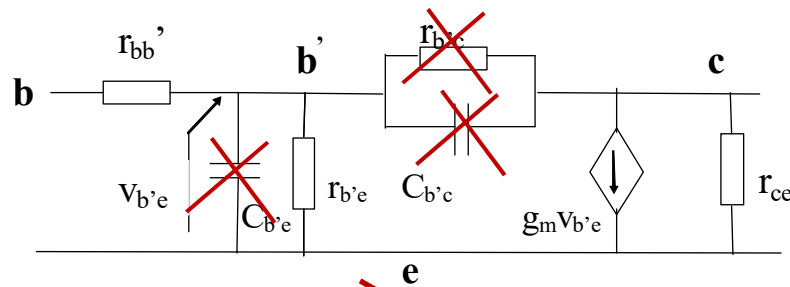


# Last time: a linear, small-signal BJT model


## Mid-frequency model

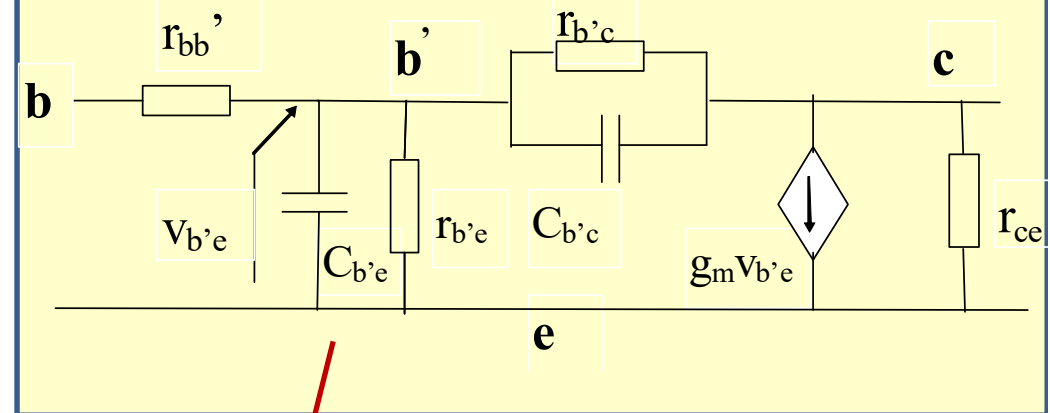

## High frequency model



Limited by circuit capacitors

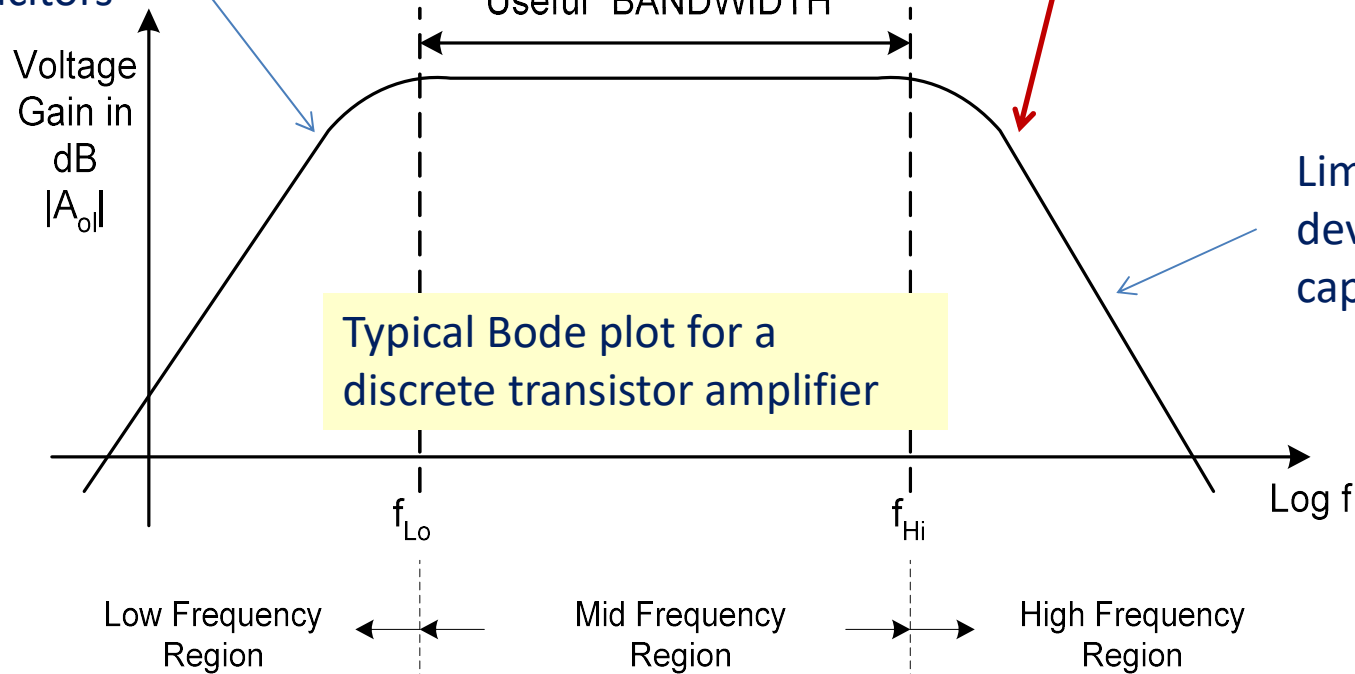

Limited by device/parasitic capacitance

## Part 2: Bipolar transistor amplifier configurations


- established an ac model for the bipolar transistor,
- now analyse the basic amplifier configurations.

1. **Common emitter (CE)**
2. **Common emitter with emitter degradation (CE-ED)**
3. **Common collector (CC) also known as emitter follower (EF)**
4. **Common base (CB)**

- voltage and current gains, input and output resistance etc.
- each configuration has **particular properties** that we can usefully employ when building up complex electronic circuits....

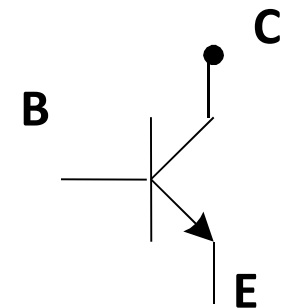
**.. by cascading stages!**

So look at examples of two and three stage amplifiers



# Golden Rules for drawing equivalent circuits

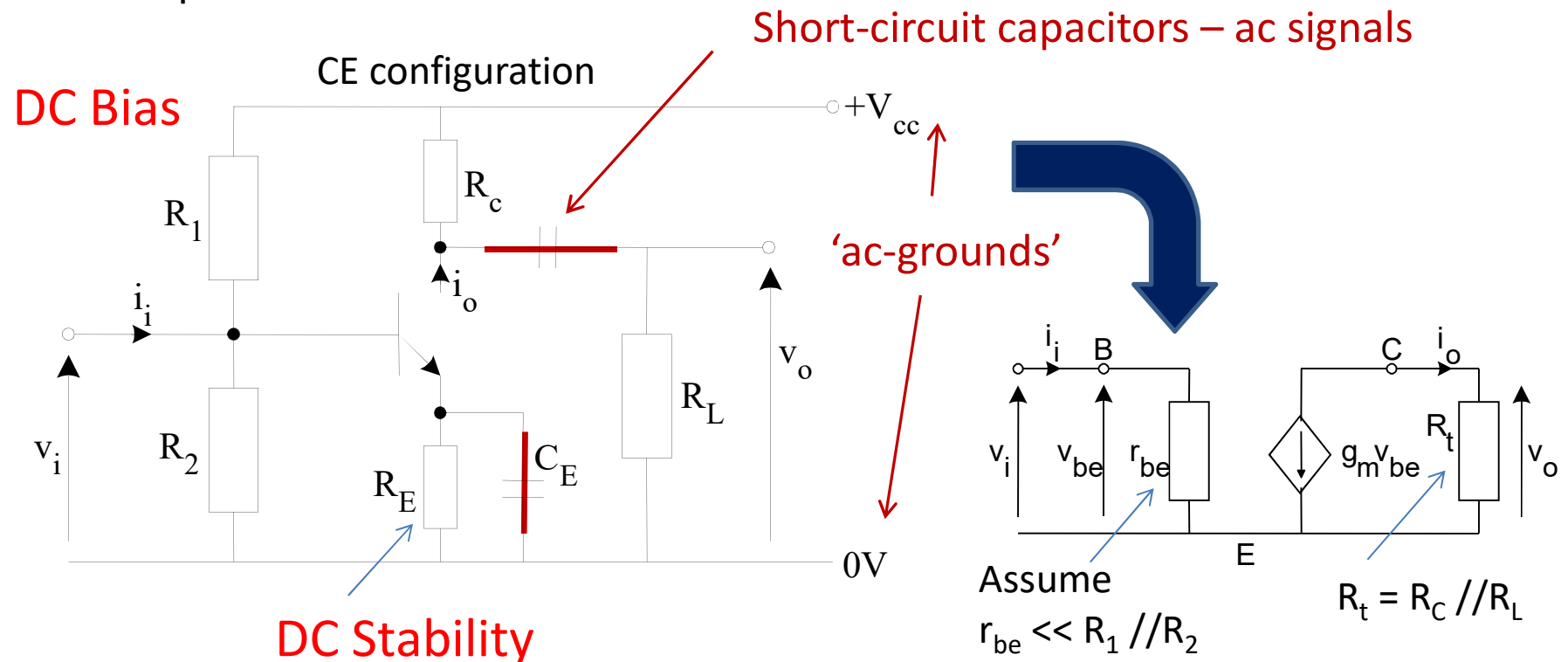1. Draw the equivalent circuit of the transistor first
2. Identify the a.c. grounds (voltage sources look like short circuits for a.c. currents!)
3. Convert capacitors to short circuits (we are interested in 'mid-frequency' regimes where the impedance of coupling/de-coupling capacitors is zero)
4. Add the other circuit components (resistors) to obtain the complete equivalent circuit.




# The common emitter amplifier

Voltage Gain,  $A_V$ :

so 
$$A_V \equiv \frac{v_o}{v_i} = \frac{v_o}{v_{be}}$$

$$v_o = i_o R_t = -g_m v_{be} R_t$$
 Ohm's Law

$$A_V = -g_m R_t$$

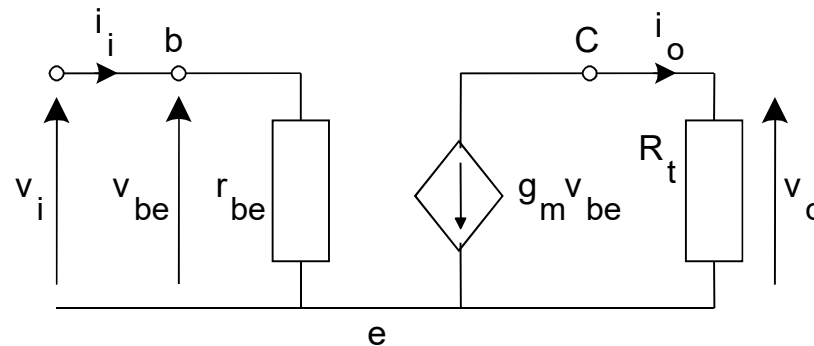

Use the simplest model!  
Even omit  $r_{bb'}$  and  $r_{ce}$


Assume  
 $r_{be} \ll R_1 // R_2$

**Include effect of  $r_{bb'}$  and  $R_s$  :**

$$A_V = \frac{v_o}{v_i'} = \frac{v_o}{v_{b'e}} \frac{v_{b'e}}{v_i'}$$
 Chain rule


$$v_{b'e} = v_i' \frac{r_{b'e}}{r_{b'e} + r_{bb'} + R_s}$$
 Potential division
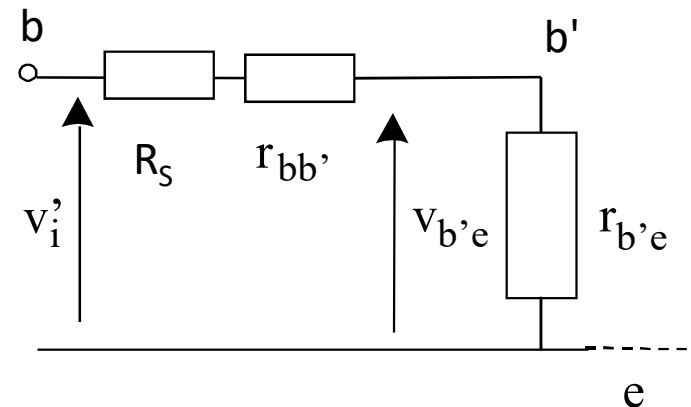
$$A_V' = -g_m R_t \frac{r_{b'e}}{r_{b'e} + r_{bb'} + R_s}$$



**Note the degradation of voltage gain by 'coupling term'**
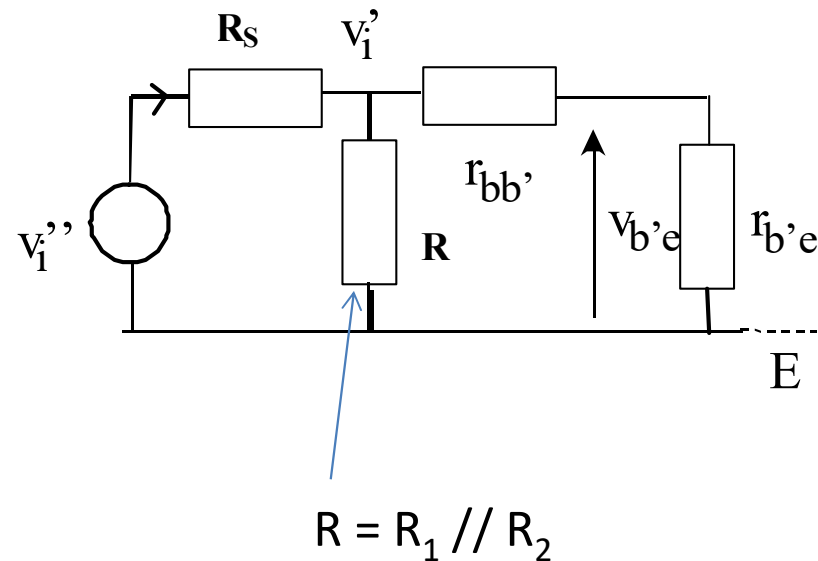
## Full treatment – include effect of bias resistors



$R$  and  $R_s$  'load' the front end of the amplifier – reduce the gain


$$A_v'' = -g_m R_t \frac{r_{b'e}}{r_{b'e} + r_{bb'}} \frac{R // (r_{bb'} + r_{b'e})}{R_s + R // (r_{b'e} + r_{bb'})}$$

Ex: Prove this equation....

# Input resistance

Ohm's Law gives

$$R_i = \frac{v_i}{i_i} = r_{be}$$

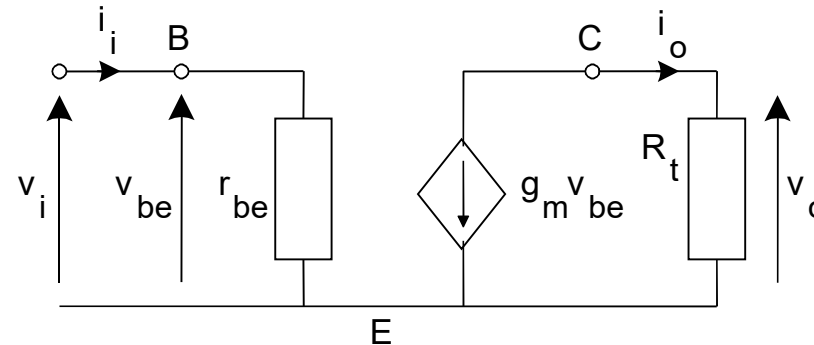


include  $r_{bb}'$ :  $R_i = r_{b'e} + r_{bb}'$

$r_{bb}'$  small; typically 50-100 (see data sheets)

easy to include the effect of R (bias resistors)

$$R_i' = \frac{v_i'}{i_i'} = R // (r_{b'e} + r_{bb}')$$

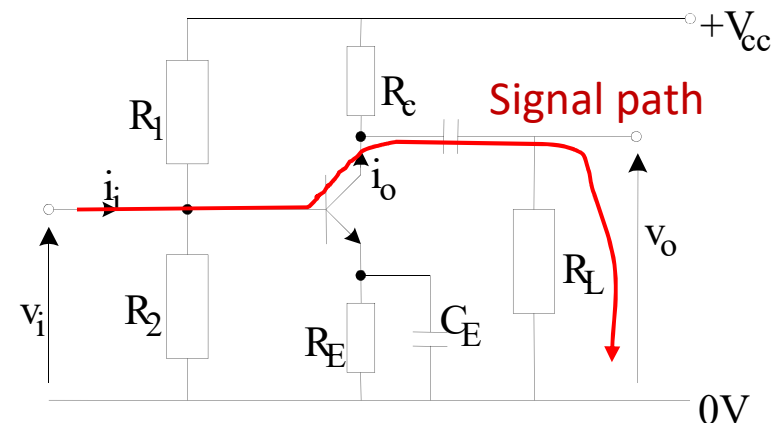usually make  $R \gg (r_{b'e} + r_{bb}')$



- so signal goes into the transistor not through the bias resistors!!


# Current Gain

$$A_i \equiv \frac{i_o}{i_i}$$

We can write:  $i_o = -g_m v_{be}$

$$v_{be} = i_i r_{be}$$

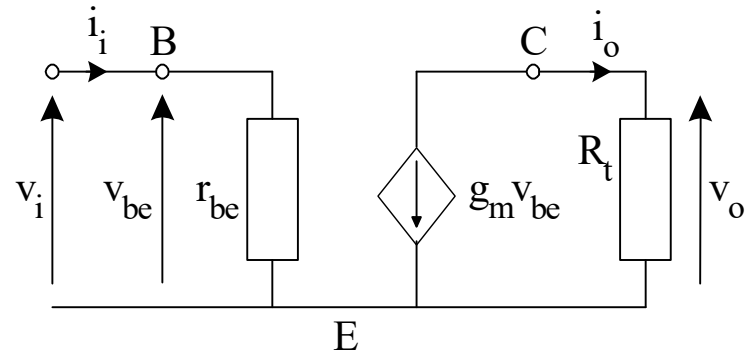so 
$$A_i = \frac{i_o}{i_i} = -g_m r_{be} = -\beta_o$$



(Q: what is the effect of including  $r_{bb}'$ ??)

# Output resistance


## Technique:

1. Set i/p voltage = 0
2. Let  $R_L \rightarrow \text{infinity}$
3. Drive o/p terminal by a volt source,  $v$

Then output resistance,

$$R_o \equiv \frac{v}{i} = R_C$$


So here,  $R_o = R_C$

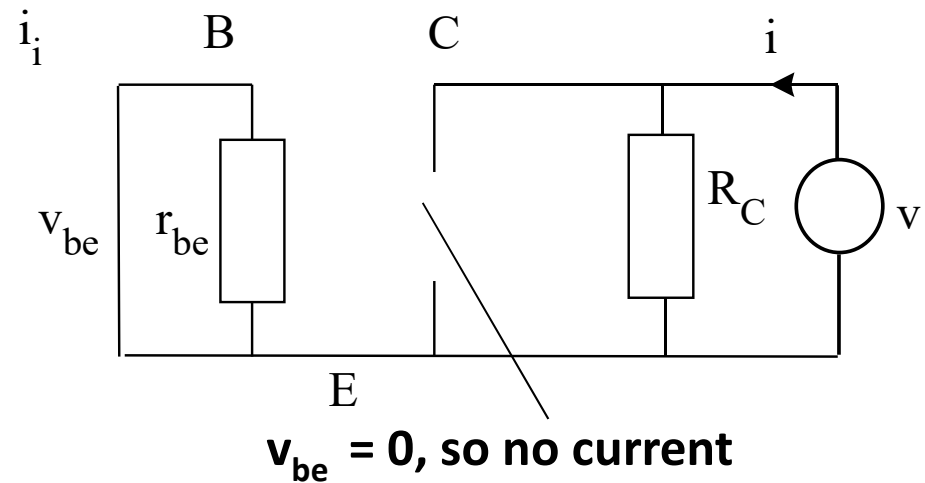

If we include effect of  $r_{ce}$ :  $R_o = R_C // r_{ce}$



# PSPICE simulation(DC voltages)

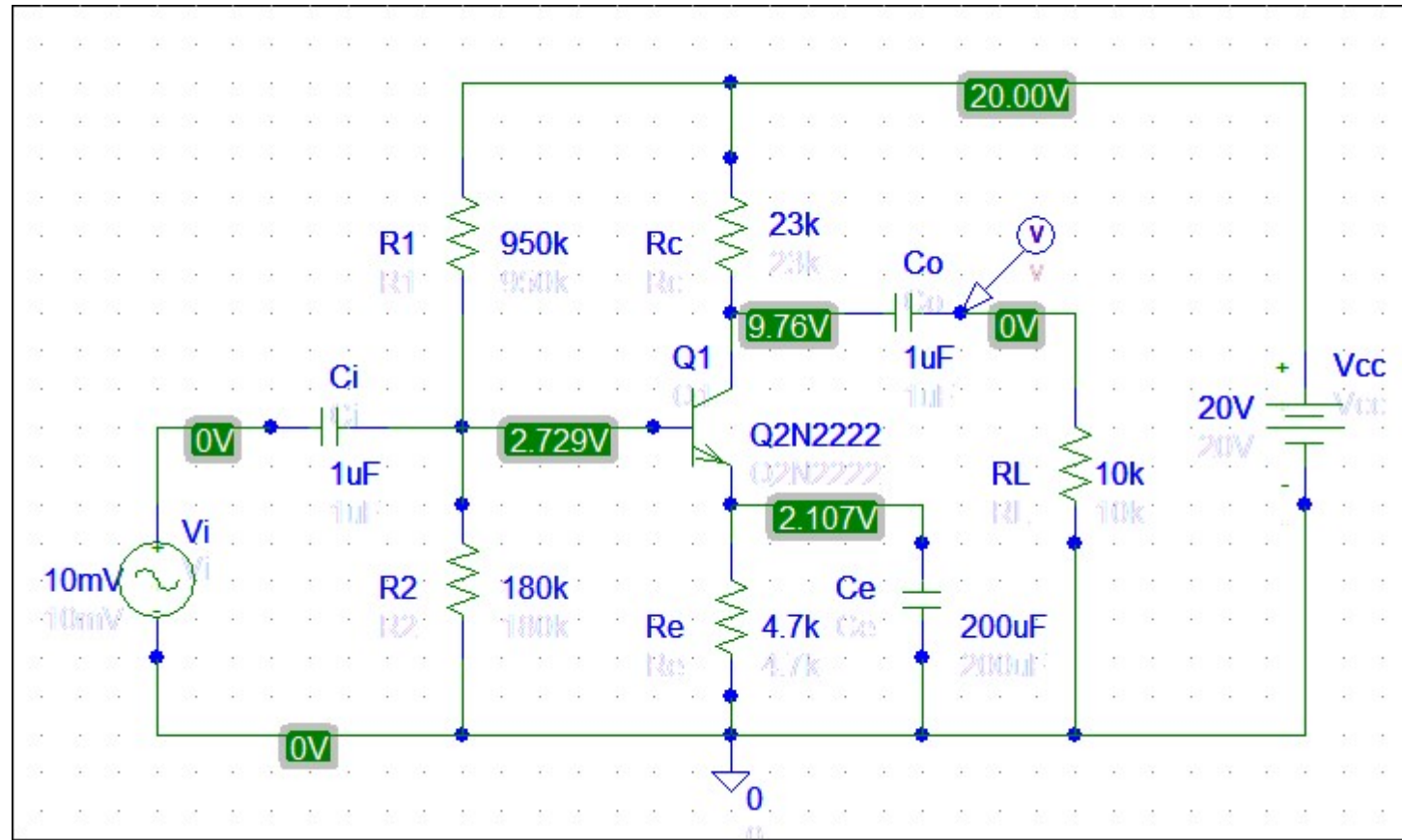

$$V_{BE} = 2.73 - 2.11 = 0.62 \text{ V} \quad V_{CE} = 9.76 - 2.11 = 7.65 \text{ V}$$

# PSPICE simulation(DC currents)


$$I_C = 0.45 \text{ mA}$$

$$g_m = 40I_C = 40 \times 0.45 \text{ mA/V} = 18 \text{ mA/V}$$

$$r_{be} = \frac{\beta_o}{g_m} = \frac{104}{18} \text{ k} = 13 \text{ k}\Omega$$

$$A_V = g_m \times ac \text{ load}$$
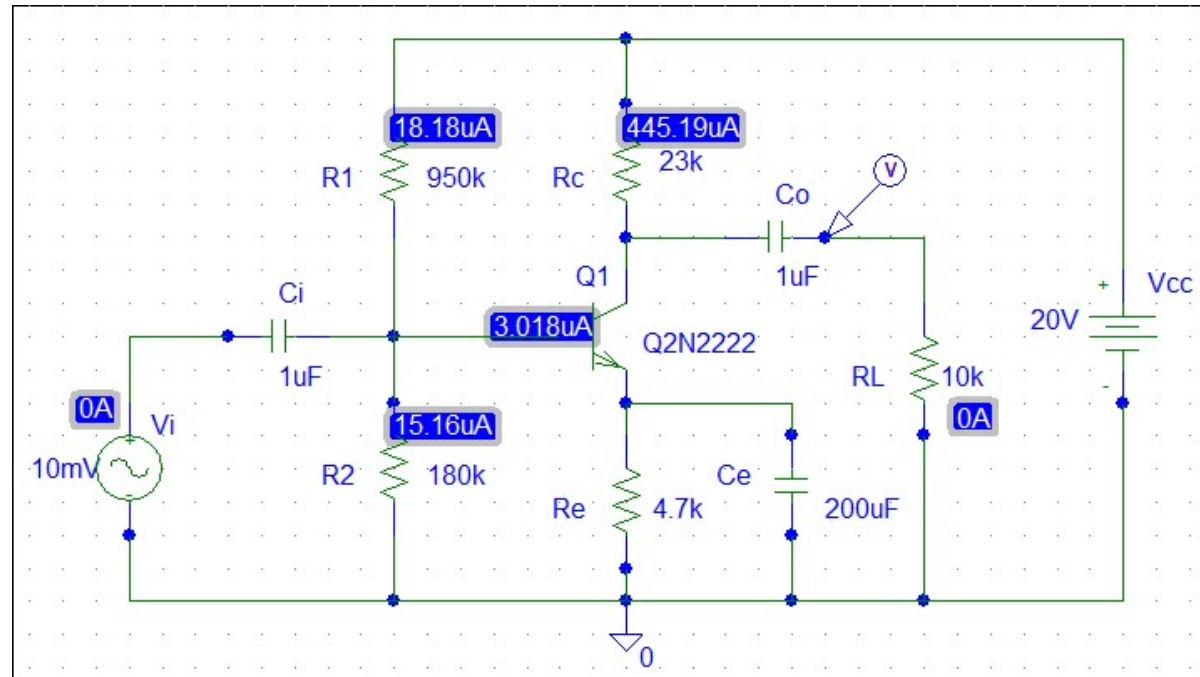
$$ac \text{ load} = \frac{R_C \times R_L}{R_C + R_L} = 7 \text{ k}\Omega$$



Small-signal values:  $A_V = 126$ ,  $R_{in} = r_{be} = 13 \text{ k}\Omega$ ,  $R_o \sim R_C = 23 \text{ k}\Omega$


# PSPICE simulation: $R_{in}$ , $A_v$ , $A_i$

Apply ac sweep ( $v_{in} = 10 \text{ mV}$ )

$$R_{in} = \frac{v_i}{i_i}$$


$$A_v = \frac{v_o}{v_i}$$

$$A_i = \frac{i_o}{i_i}$$

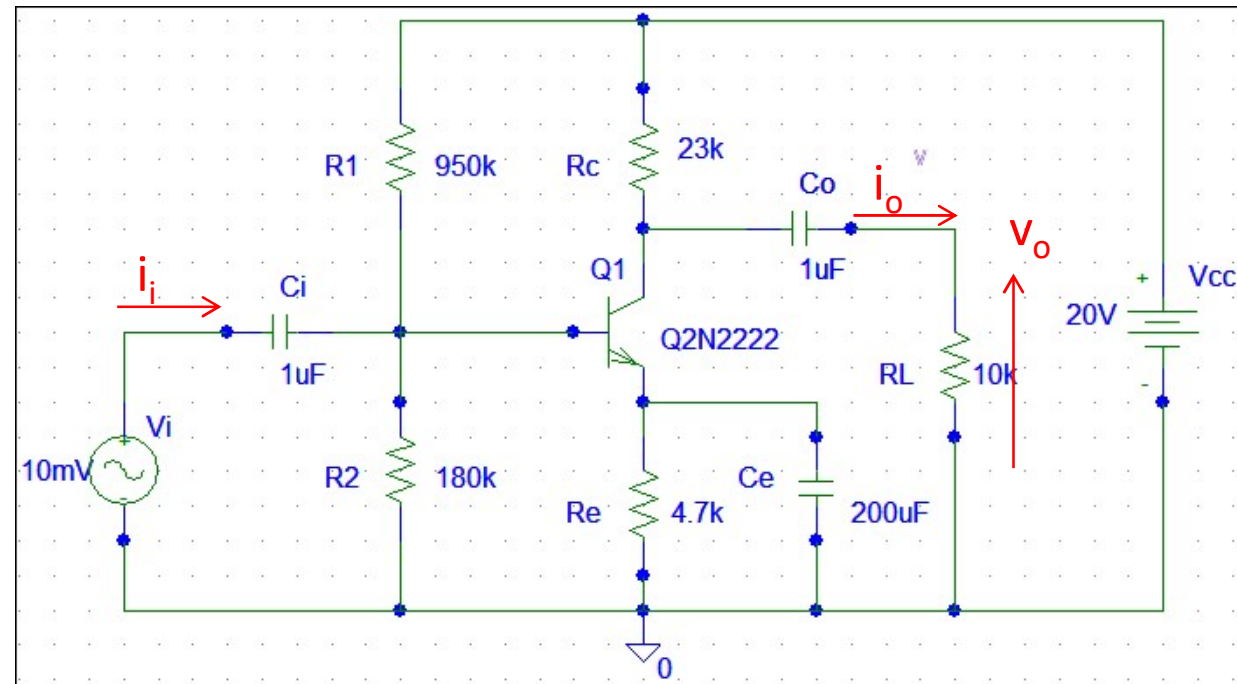


Ac sweep from 1 Hz to 100 MHz

V-Gain is 115 cf 126 (theory)

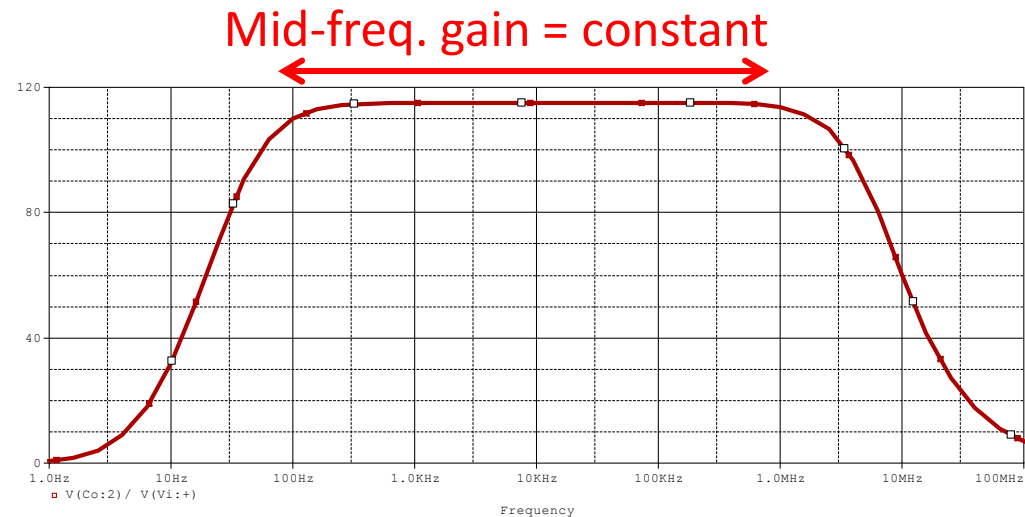

Ac sweep from 1 Hz to 100 MHz


I-Gain is 104, giving  $\beta_o = 104$

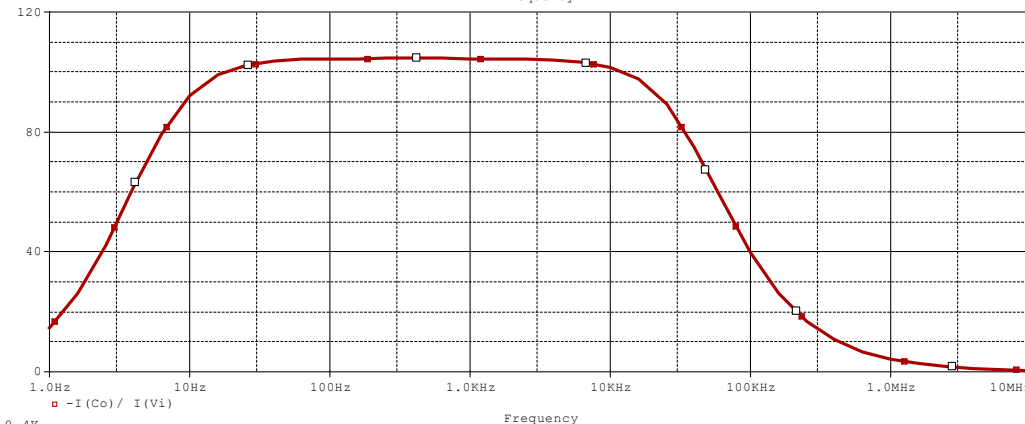


Ac sweep from 100 Hz to 10 kHz

$R_{in} = 9.1 \text{ k}\Omega$  (at 1 kHz)  
cf  $13 \text{ k}\Omega$  (theory,  $r_{be}$  )

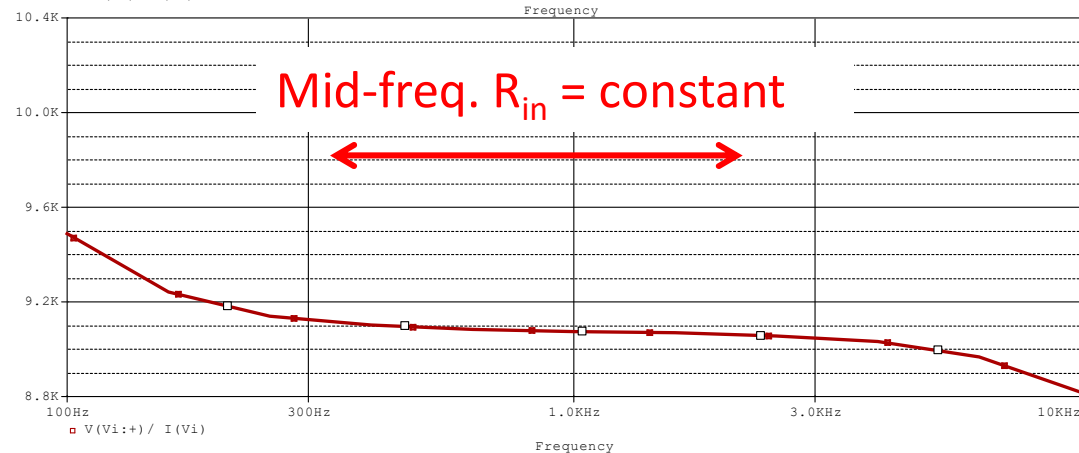(take account of base resistors,  
get  $12 \text{ k}\Omega$ )




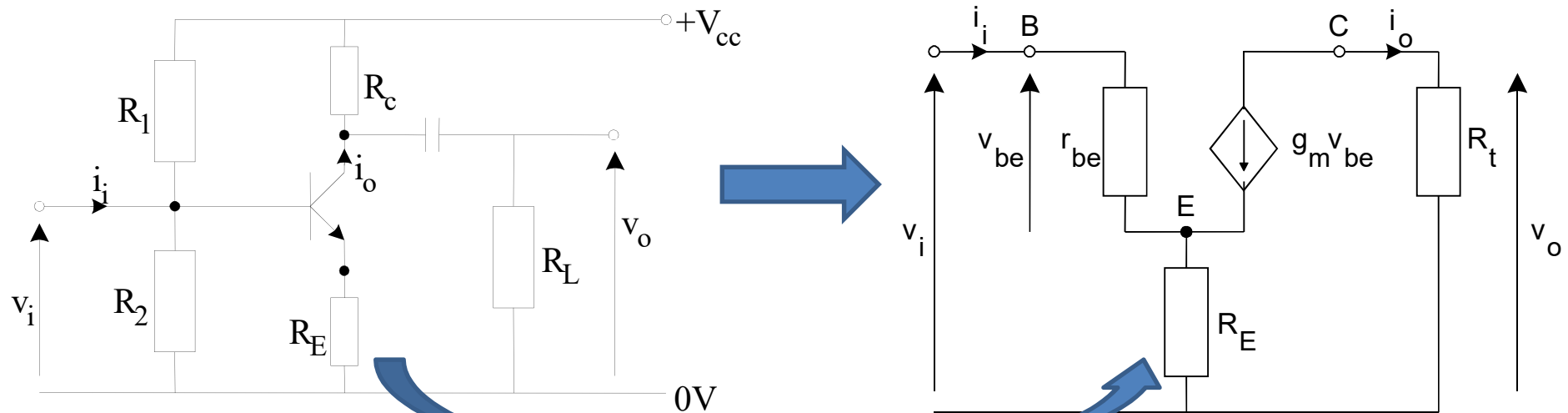
# Common-emitter with emitter degradation



Remove  $C_E$  in CE circuit

*(for analysis see exercise 2 – you do this one!)*

# Common-collector (emitter-follower)

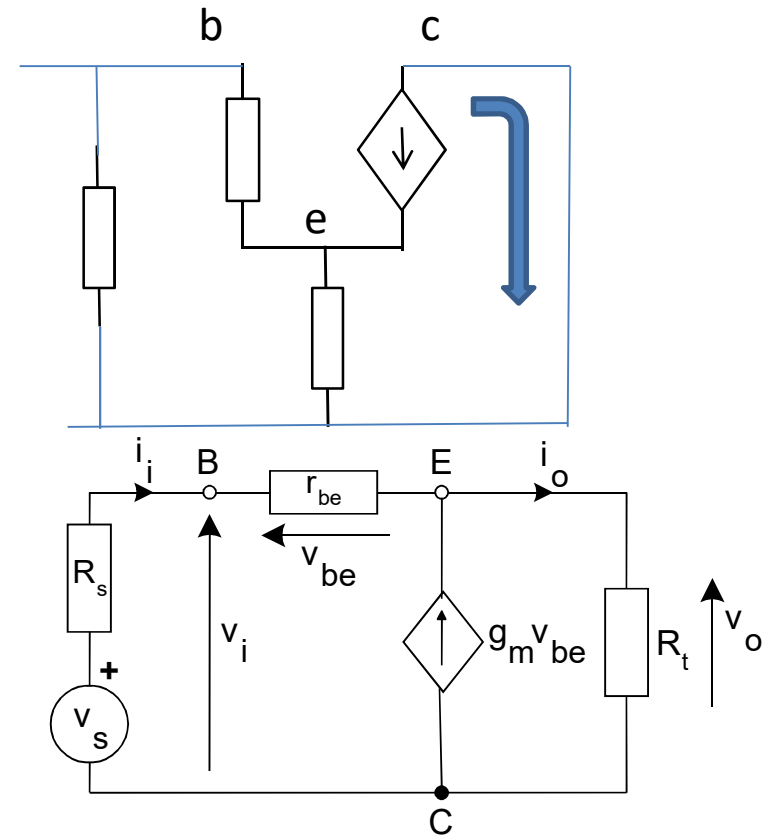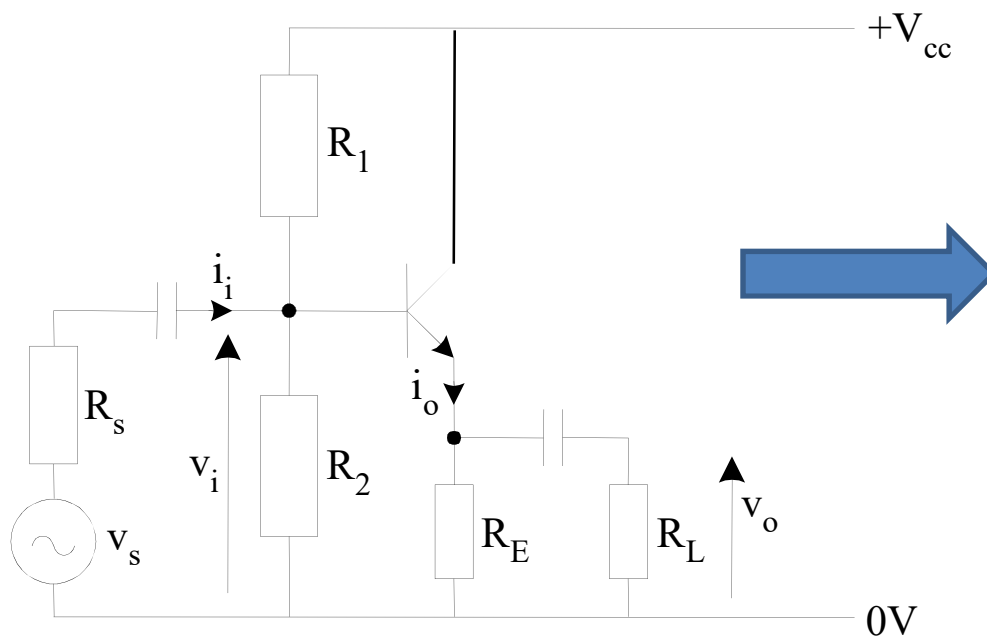

$$R_t = R_E // R_L$$

Assume  $R_1 // R_2$  very large

Q: what is meant by 'small signal'? (see earlier notes)  
Does it mean 'small amplitude' or 'small frequency'?


# Voltage Gain ( $v_o / v_i$ )

(we need to learn some techniques..)

$$v_o = i_o R_t \quad (1)$$

$$\text{KCL at node E: } i_i + g_m v_{be} = i_o = \frac{v_o}{R_t} \quad (2)$$
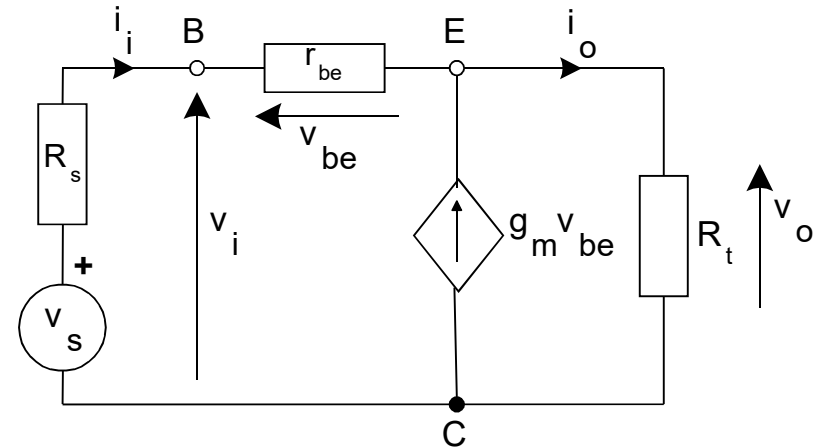
$$\text{also } v_{be} = v_i - v_o \text{ and } i_i = \frac{v_i - v_o}{r_{be}} \quad (3)$$



$$\text{Substitute for } i_i \text{ and } v_{be} \text{ in Eqn.(2): } \frac{(v_i - v_o)}{r_{be}} + g_m (v_i - v_o) = \frac{v_o}{R_t}$$

$$\text{Multiply across by } r_{be}: v_i - v_o + \beta_o v_i - \beta_o v_o = v_o \frac{r_{be}}{R_t}$$

$$\text{Re-arranging gives: } v_o + \beta_o v_o + v_o \frac{r_{be}}{R_t} = +v_i + \beta_o v_i \quad \begin{matrix} \text{(where we've used)} \\ (\beta_o = g_m r_{be}) \end{matrix}$$

(note the technique; we have gathered all the terms involving  $v_o$  on the LHS and those involving  $v_i$  on the RHS)

$$v_o \left( 1 + \beta_o + \frac{r_{be}}{R_t} \right) = v_i (1 + \beta_o) \quad \Rightarrow \quad A_V \equiv \frac{v_o}{v_i} = \frac{(1 + \beta_o)}{1 + \beta_o + \frac{r_{be}}{R_t}}$$

## Interpretation (CC)

$$A_V \equiv \frac{v_o}{v_i} = \frac{(1 + \beta_o)}{(1 + \beta_o) + \frac{r_{be}}{R_t}}$$

**We notice straight away that the voltage gain must be less than 1!**

Assuming now, that  $\beta_o \gg 1$ ,

$$A_V = \frac{v_o}{v_i} = \frac{\beta_o}{\beta_o + \frac{r_{be}}{R_t}}$$

an approximate but quite accurate estimate for the voltage gain

Which can also be written as

$$A_V \equiv \frac{v_o}{v_i} = \frac{g_m \times R_t}{1 + g_m \times R_t} \quad \text{for the common-collector gain.}$$

$(\beta_o = g_m r_{be})$

**Q: What use is an amplifier with voltage gain less than 1!**

**Let's look at the input resistance.....**




# Input resistance of the CC amplifier

This is defined as:  $R_i \equiv \frac{v_i}{i_i}$

Take a KVL:  $v_i = i_i r_{be} + v_o$  (1)

Where  $v_o = i_o R_t$  (2)

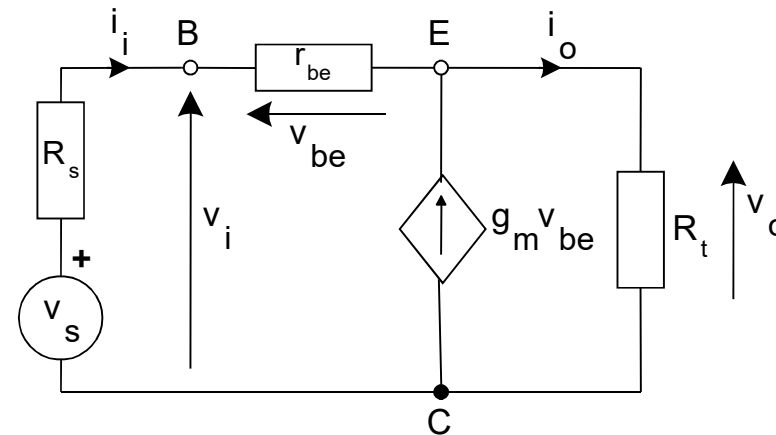

Now take KCL at node 'E':  $i_o = i_i + g_m v_{be}$

Which can also be written as  $i_o = i_i + \beta_o i_i \Rightarrow i_o = i_i (1 + \beta_o)$  (3)

Sub. (3) into (2):  $v_o = i_i R_t (1 + \beta_o)$

Sub. into (1):  $v_i = i_i r_{be} + i_i R_t (1 + \beta_o)$  (note again the technique; we have gathered all the terms involving  $v_i$  on the LHS and those involving  $i_i$  on the RHS)

$$R_i \equiv \frac{v_i}{i_i} = r_{be} + R_t (1 + \beta_o)$$

# Interpretation

$$R_i \equiv \frac{v_i}{i_i}$$
$$= r_{be} + R_t(1 + \beta_o)$$

- Recall the input resistance of the CE amp ( $r_{be}$ ).
- So the input resistance of the CC amp is **boosted by the factor  $R_t(1 + \beta_o)$ !**
- The CC amp has high input resistance!

Q: Is this any use??

Let's also look at the output resistance – a rather long analysis .....

# Common Collector, Output resistance

## Set up the analysis

Suppress (ie short out), the signal source  $v_s$ .

Apply a voltage source to the output – to force a current into the amplifier.

The output resistance is then given by

$$R_o = \frac{v}{i}$$

**We must find this by appropriate circuit analysis.**

We can write 
$$i = \frac{v}{R_E} + i_X \quad (1)$$


Apply KCL at 'E': 
$$i_X + \beta_o i_i + i_i = 0$$

$$\therefore i_X = -(1 + \beta_o) i_i \quad (2)$$

Need to get rid of  $i_i$ ! : write,  $v = -i_i (R_S + r_{be})$

Sub for  $i_X$  in (1) 
$$i = \frac{v}{R_E} - (1 + \beta_o) i_i$$

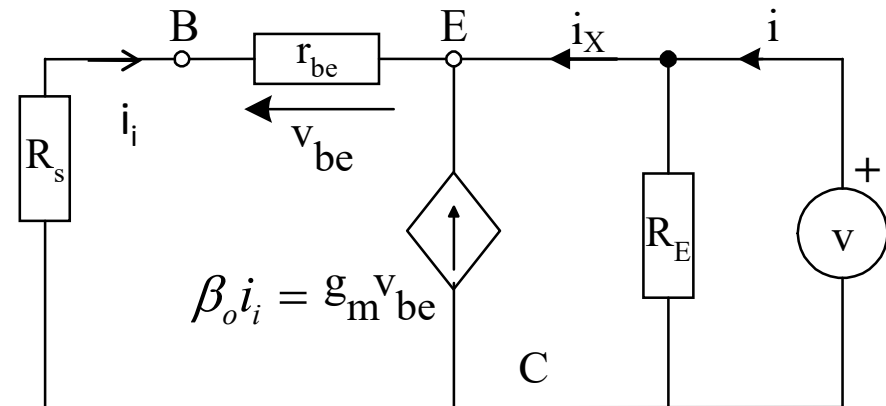Substitute (3) to get 
$$i = \frac{v}{R_E} + \frac{(1 + \beta_o)}{R_S + r_{be}} v \quad (4)$$



# Common Collector, Output resistance $R_o = \frac{v}{i}$

From previous page  $i = \frac{v}{R_E} + \frac{(1 + \beta_o)}{R_S + r_{be}} v$  (4)

**Nearly there.... We have 'i' on RHS and terms in 'v' on RHS**

**That is (4) can be written as**  $\frac{i}{v} = \frac{1}{R_E} + \frac{1 + \beta_o}{R_S + r_{be}}$


That is,  $R_o = \frac{v}{i} = R_E // \frac{R_S + r_{be}}{1 + \beta_o}$  (Note that  $\frac{R_S + r_{be}}{1 + \beta_o}$  has units of ohms)

$\beta_o$  is large, so we can predict that  $R_o$  is small...

## Conclusions:

The CC has large (-ish) input resistance and small output resistance – but no voltage gain!

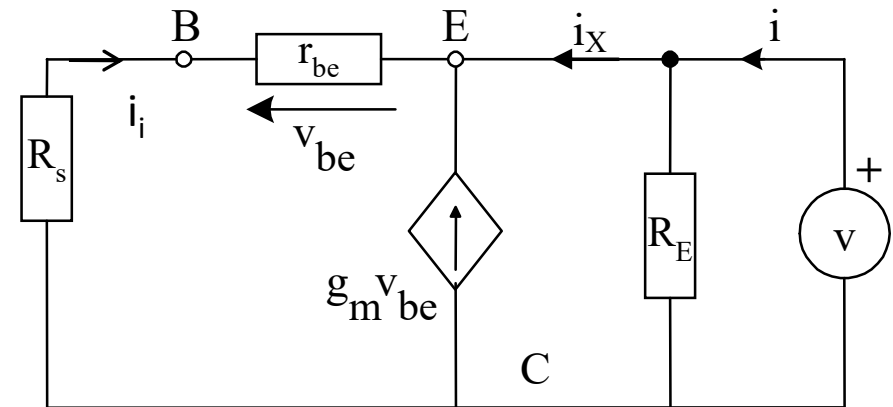**Use it to 'match' high impedance source to low impedance load stages (see 'Design an Op-amp' Expt 5 later in the year.)**



# Example of 'Matching'

Consider a voltage amplifier and Thevenin source.

Should  $R_{in}$  be big or small?


$$v_{in} = \frac{R_{in}}{R_{in} + R_g} v_g$$

Ideally, want  $V_{in} = V_g$

So want  $R_{in} \gg R_g$ , ideally infinity!

To get good coupling between source and amplifier

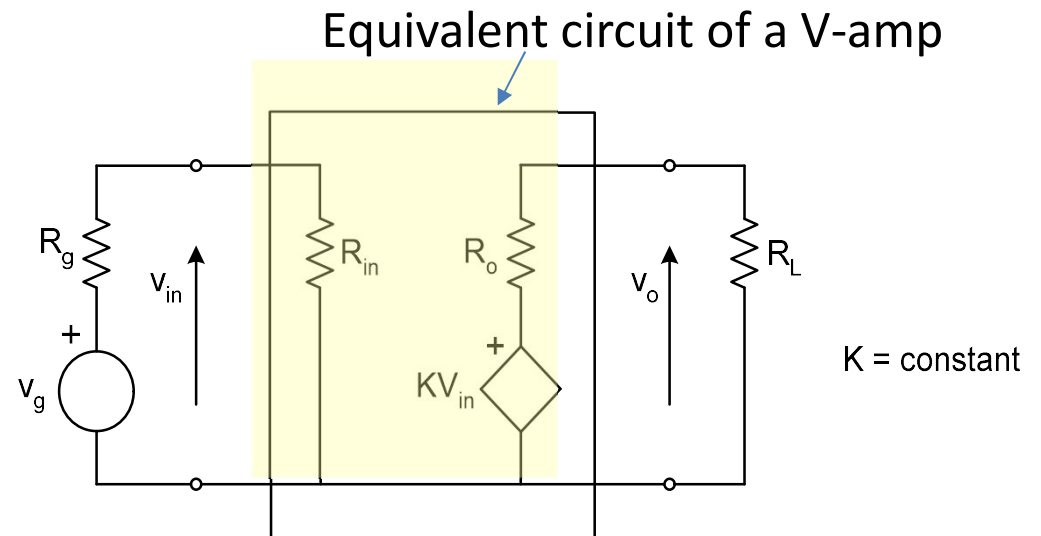All the signal,  $v_g$  is 'coupled' into the amplifier!



# Bootstrapping

Although the CC input resistance ( $R_{in}$ ) is large, the bias resistors ( $R_1$ ,  $R_2$ ) can effectively reduce it, as they appear in parallel with  $R_{in}$ . One way to get round this is to use 'bootstrapping'

- C is short circuit at freq of interest
- $R_3$  is small value (doesn't affect bias)
- change in ac current through  $R_3$  is

$$i_{R3} = \frac{v_i - v_o}{R_3}$$


And as  $v_i \sim v_o$ ,  $i_{R3} \sim 0$ !

That is, ideally, the path via  $R_3$  has infinite resistance – **all signal goes into BJT!**


In fact,  $v_i$  is not equal to  $v_o$  as the gain of the CC is not quite unity. So write

$$R_3(\text{effective}) = \frac{v_i}{i_{R3}} = \frac{R_3}{1 - A_V}$$

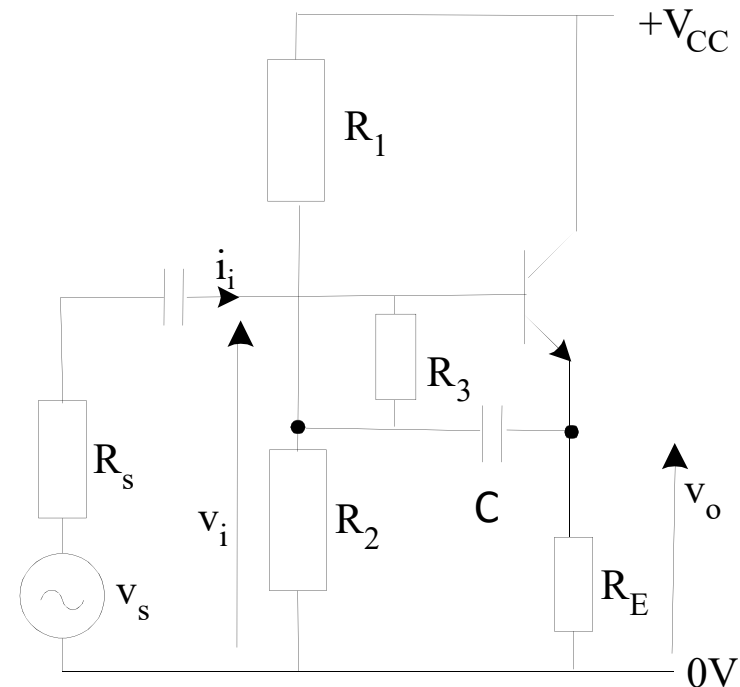Still a big value as  $(1 - A_V)$  is very small



# Common-base

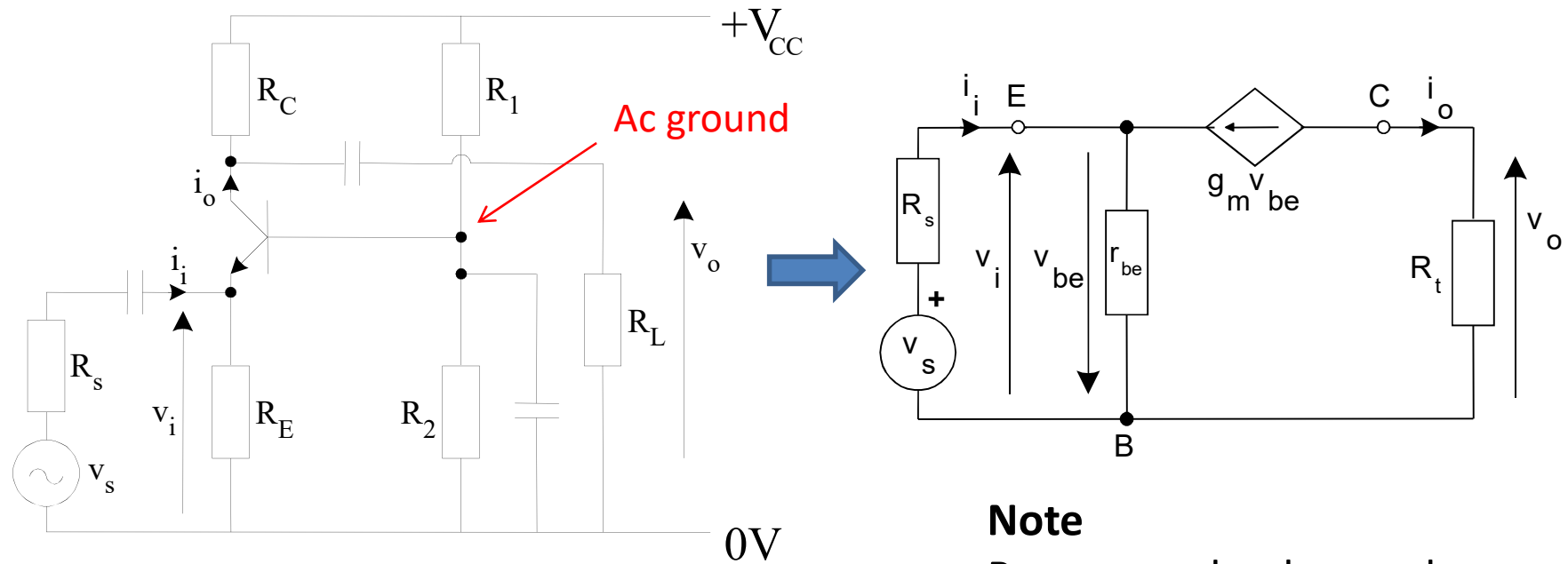

## Note


$R_E$  assumed to be much greater than  $R_{in}$  ( $= V_i / i_i$ )

*(for analysis see exercise 3 – you do this one!)*

# Glossary of amplifier properties

(provided in examinations)

## Common Emitter

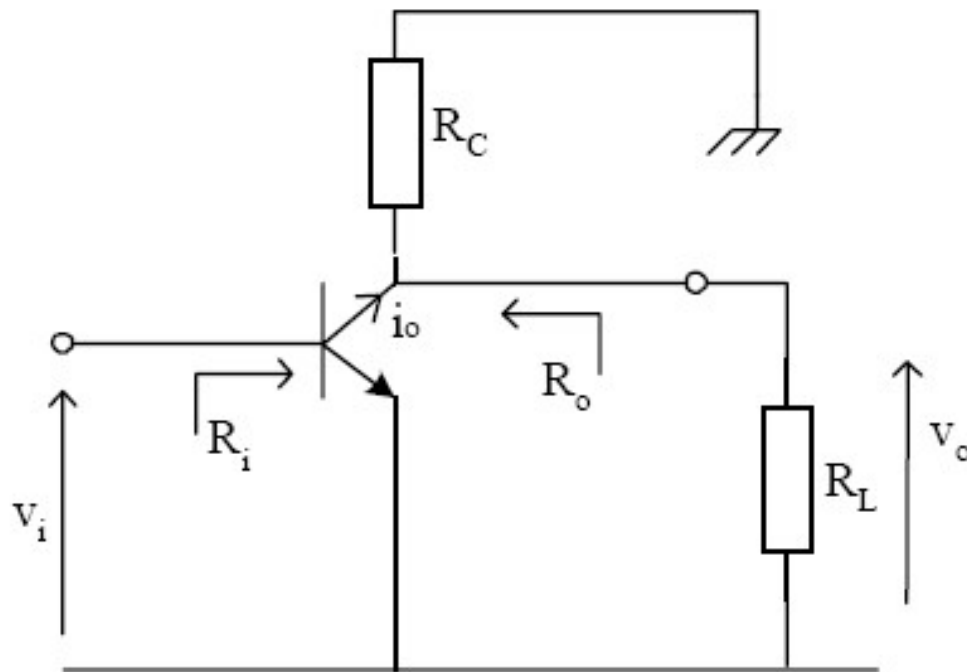

$$R_i = r_{be}$$

$$R_o = R_C$$

$$A_V = \frac{v_o}{v_i} = -g_m R_C // R_L$$

$$G_M = \frac{i_o}{v_i} = -g_m$$


$$R_M = -\beta_o R_C // R_L$$

Note:  $r_{be} \equiv r_\pi$      $v_{be} \equiv v_\pi$   
 $r_{ce} \equiv r_o$



# CE-ED

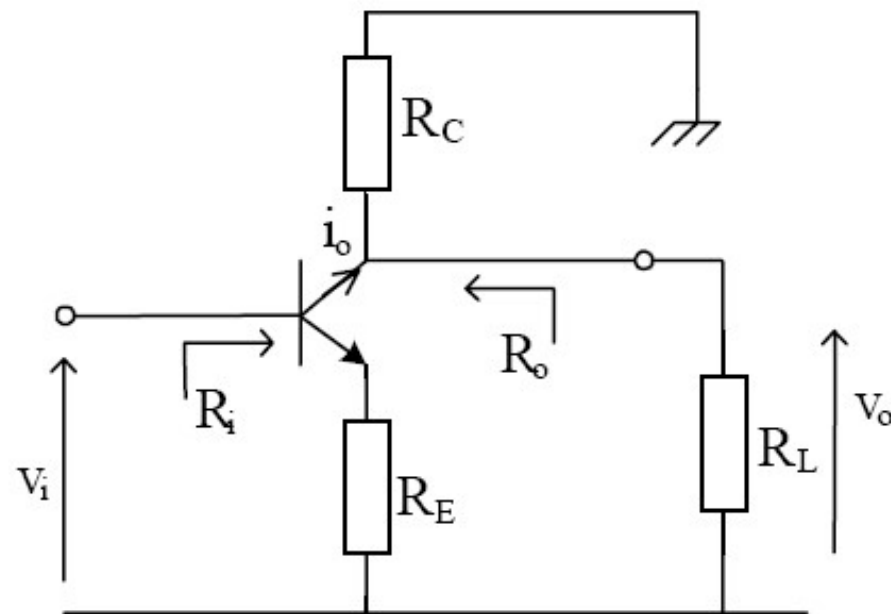**Common emitter with emitter degradation**



$$R_i = r_{be} + (1 + \beta_o)R_E$$

$$R_o = R_C$$


$$A_V = -\frac{g_m R_C // R_L}{1 + g_m R_E}$$

$$G_M = -\frac{g_m}{1 + g_m R_E}$$

$$R_M = -\beta_o R_C // R_L$$

# CC (EF)

**Common collector (Emitter follower)**

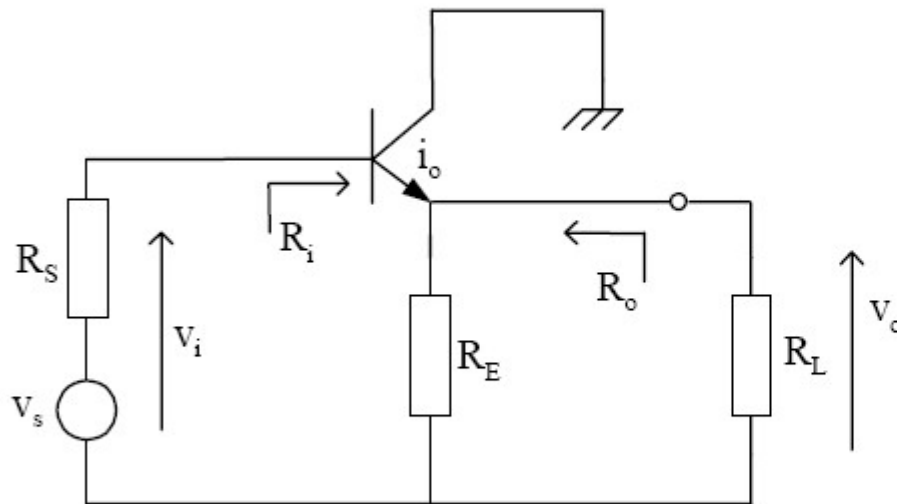

$$R_i = r_{be} + (1 + \beta_o)R_E // R_L$$

$$R_o = \frac{r_{be} + R_S}{1 + \beta_o} // R_E$$


$$A_V = \frac{g_m R_E // R_L}{1 + g_m R_E // R_L}$$

$$G_M = \frac{g_m}{1 + g_m R_E // R_L}$$

$$R_M = (1 + \beta_o)R_E // R_L$$

# CB

## Common base

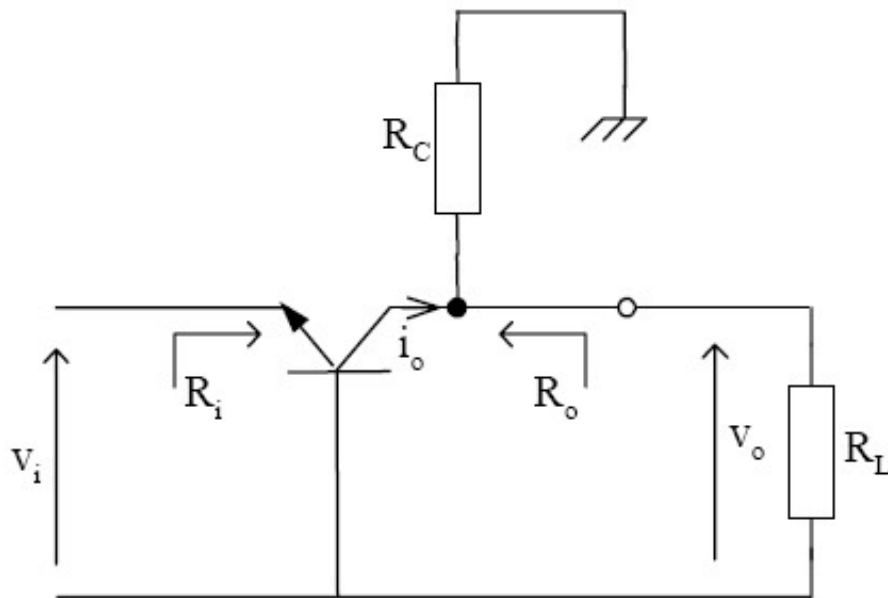

$$R_i = \frac{r_{be}}{1 + \beta_o} \approx 1 / g_m = r_e \quad R_o \sim R_C$$

$$A_V = g_m R_C // R_L$$


$$G_M = g_m \quad R_M = \frac{\beta_o R_C // R_L}{1 + \beta_o}$$

# Summary of properties of amplifier configurations

Property	$A_v$	$A_i$	$R_{in}$	$R_{out}$	Usage
<b>CE</b>	high	high	Medium	high	Most useful, general purpose
<b>CE-ED</b>	Low	high	high	low	$R_E$ constitutes feedback – sacrifice $A_v$ for increased stability: less dependent on $\beta_o$ (also temperature), increase $R_{in}$
<b>CC</b>	Low ( $< 1$ )	high	high	low	Impedance matching – high R-source to low-R load (also very linear – used in power amp. Output stages)
<b>CB</b>	high	low ( $<1$ )	low	high	Impedance matching – low R-source to high-R load (also features in Diff.Amp. – see later notes)

*Multi-stage amplifiers can thus be configured to provide, for example, very high input impedance, high voltage and current gain and low output impedance.*

# Example

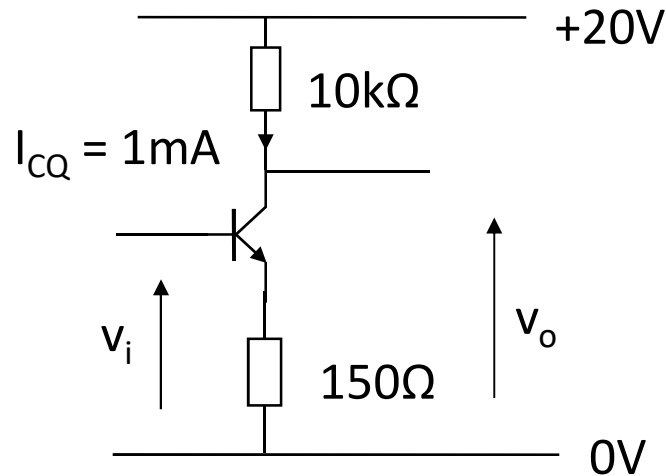

Calculate the voltage gain

Note that  $R_t = R_C$

The amplifier is CE-ED.

From the amplifier properties sheet,  $\frac{v_o}{v_i} = -\frac{g_m R_t}{1 + g_m R_E}$

For  $I_C = 1\text{mA}$ ,  $g_m = 40I_{CQ} = 40 \text{ mA/V}$

$$\therefore \frac{v_o}{v_i} = -\frac{40 \times 10^{-3} \times 10^4}{1 + 40 \times 10^{-3} \times 150} = -57$$

# Electronic circuits and systems

## ELEC271

### Design example 1

- The following is a 'rough' design with a number of approximations.
- It can be **validated** by PSPICE simulation and fine-tuning of the parameter values undertaken

# Specification

- Design a common-emitter amplifier to the following specification
  - $V_{CC} = 20V$ ,  $A_v > 100$ ,  $V_C \sim V_{CC}/2$ , a load of 10k
- Given
  - $\beta_o = 250$ , make  $R_1 // R_2 \sim 10 \times R_{in}$ ,  $V_{RE} = 10\% V_{CC}$
- Hints
  - First draw the schematic circuit
  - Estimate values for  $R_C$ ,  $I_C$ ,  $R_E$ ,  $V_B$ ,  $R_2$ ,  $R_1$

SEE VITAL for the solution – try it before the next lecture!

# A two-stage voltage amplifier

Bias resistors & coupling capacitors omitted


## Analysis:

Use the chain rule to split the overall gain into three components

$$A_{V_S} = \frac{v_{o2}}{v_s} = \frac{v_{o2}}{v_{i2}} \times \frac{v_{i2}}{v_{i1}} \times \frac{v_{i1}}{v_s}$$

But  $v_{i2} = v_{o1}$  so:-
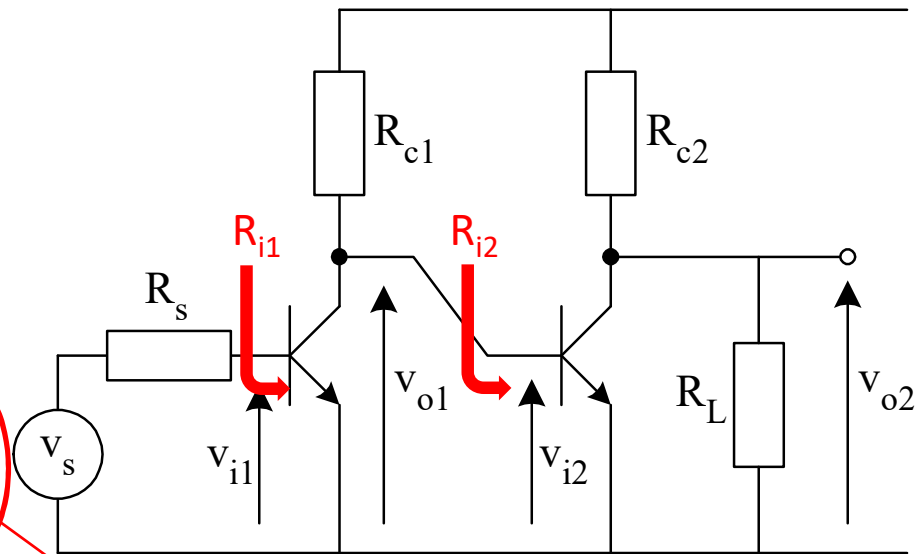
$$A_{V_S} = \frac{v_{o2}}{v_{i2}} \times \frac{v_{o1}}{v_{i1}} \times \frac{v_{i1}}{v_s}$$



Which is equal to

$$A_{V_S} = A_{V2} \times A_{V1} \times \frac{R_{i1}}{R_{i1} + R_s}$$

'Coupling' term:  $R_s$   
'loads' the input

$A_{V2} = -g_{m2} R_L \parallel R_{C2}$   
that is, ' $g_m$  x the ac load'

$A_{V1} = -g_{m1} R_{C1} \parallel R_{i2}$   
must take account of the loading effect  
of the second stage on the first ( $R_{i2}$ )

Note that  $R_{i2} = r_{be2}$ ,  $g_{m2} = 40 \times I_{C2}$ ,  $R_{i1} = r_{be1}$

( $r_{be} g_m = \beta_o$ )




# A 3-stage transconductance amplifier

**Function:** *transconductance* amplifier – turns an input voltage signal  $v_s$  into an output current signal  $i_o$  with appropriate enlargement (amplification) of the signal.

In this case the current is into the collector load  $R_{C3}$ . A practical example of the use of such an amplifier could be in driving a light emitting diode (l.e.d) which would replace the resistor.

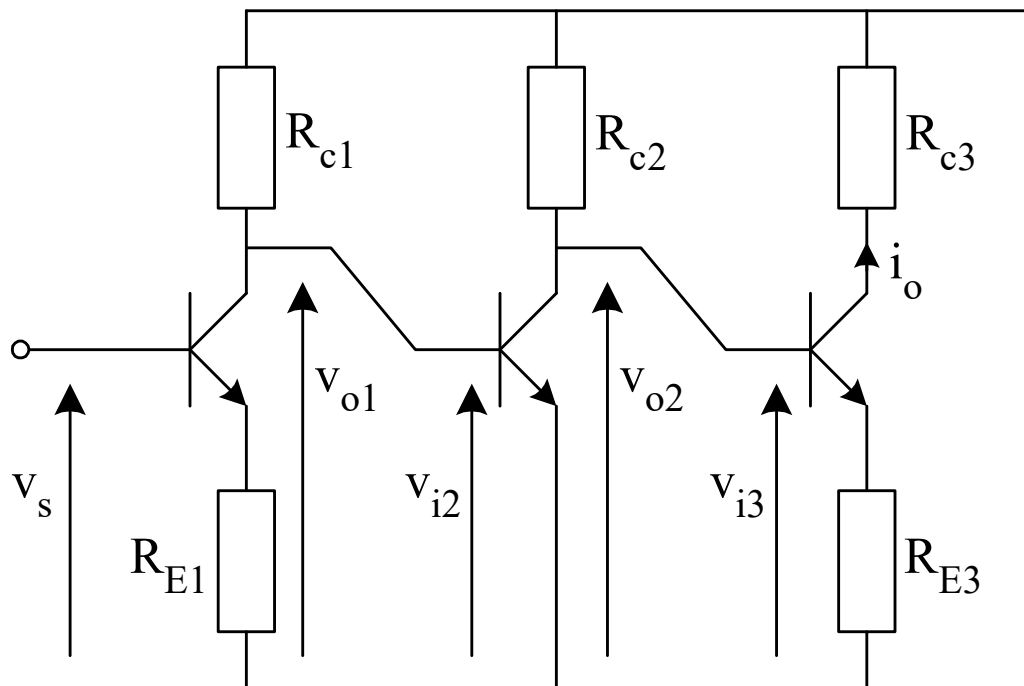- First stage provides for high input resistance and some voltage gain,
- second stage provides high voltage gain, third stage converts voltage to current.



$$G_M = \frac{i_o}{v_s} = \frac{i_o}{v_{i3}} \times \frac{v_{i3}}{v_{i2}} \times \frac{v_{i2}}{v_s}$$

$$v_{o2} = v_{i3}$$

$$v_{o1} = v_{i2}$$

$$\therefore G_M = \frac{i_o}{v_{i3}} \times \frac{v_{o2}}{v_{i2}} \times \frac{v_{o1}}{v_s}$$


# Analysis

Overall transconductance gain is

$$G_M = \frac{i_o}{v_s} = \frac{i_o}{v_{i3}} \times \frac{v_{i3}}{v_{i2}} \times \frac{v_{i2}}{v_s}$$

That is,
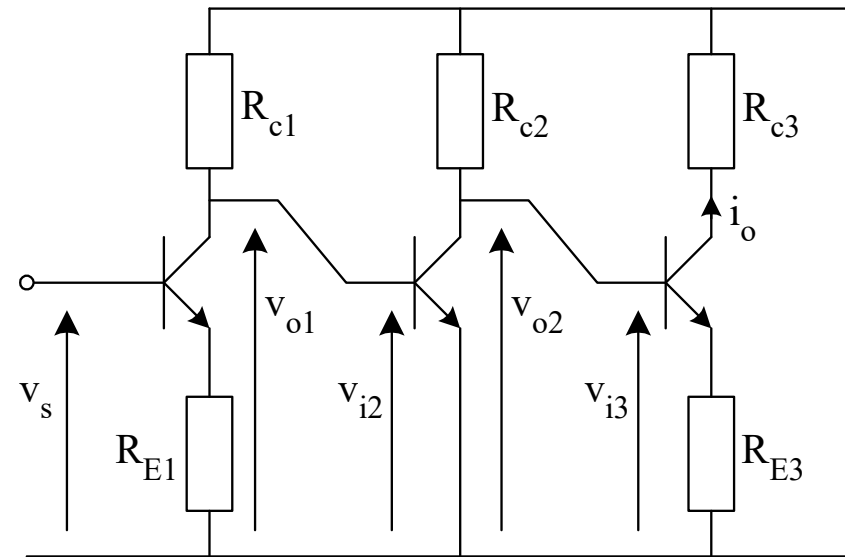
$$G_M = \frac{i_o}{v_{i3}} \times \frac{v_{o2}}{v_{i2}} \times \frac{v_{o1}}{v_{i1}}$$



or  $G_M = G_{M3} \times A_{V2} \times A_{V1}$

3<sup>rd</sup> stage is CE-ED  
want the transconductance gain

$$G_{M3} = -\frac{g_{m3}}{1 + g_{m3}R_{E3}}$$

$$A_{V2} = -g_{m2}R_{i2}$$

2<sup>nd</sup> stage is CE, loaded by stage 3

$$R_{i2} = R_{C2} // R_{i3}$$

$$A_{V1} = -\frac{g_{m1}R_{i1}}{1 + g_{m1}R_{E1}}$$

First stage is CE-ED. Must take account of the loading effect of the second stage on the first

$$R_{i1} = R_{C1} // R_{i2}$$

$R_{i2}$  is the input resistance of the 2<sup>nd</sup> stage;  $R_{i2} = r_{be2}$

# Worked example (vital)

## Part 2 notes section


biasing components have been omitted.

$$I_{C1} = 0.1 \text{ mA}$$

$$I_{C2} = 0.5 \text{ mA}$$

$$I_{C3} = 2 \text{ mA}$$

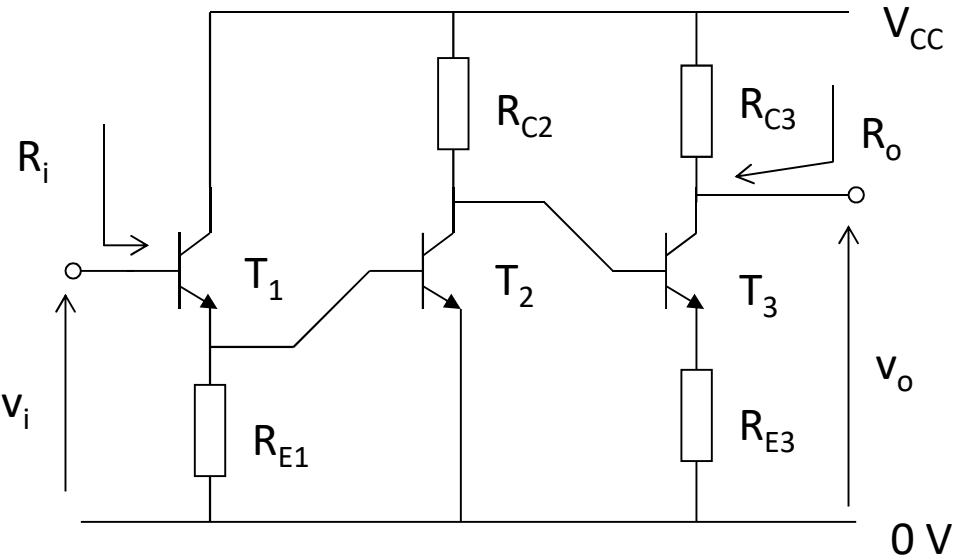1. Find  $g_m$ ,  $r_{be}$  of each transistor. ( $\beta_o = 100$ )  $v_i$
2. Find voltage gain  $v_o/v_i$
3. Find  $R_i$
4. Find  $R_o$



$R_{E1} = 1 \text{ k}\Omega$ ,  $R_{C2} = 10 \text{ k}\Omega$ ,  $R_{C3} = 2 \text{ k}\Omega$  and  $R_{E3} = 200 \text{ }\Omega$ ;  
assume  $r_{ce}$  &  $r_{b'c}$  are infinite and  $r_{bb'} = 0$ .

### Solution Method – key points

1. Use the simple formulas for  $g_m$ ,  $r_{be}$  - what are they?

$$g_m = 40 \times I_C \quad r_{be} = \beta_o / g_m$$

2. Identify the circuit blocks

#### *Start from the output side*

Work out gain of stage 3; what is the amplifier type and ac load? **CE-ED,  $R_{C3}$**

Work out gain of stage 2; what is the amplifier type and ac load? **CE,  $R_{C2} // R_{i3}$**

Work out gain of stage 1; what is the amplifier type and ac load? **CC,  $R_{E1} // R_{i2}$**

How should they be combined?  **$A_V = A_{V1} \times A_{V2} \times A_{V3}$**

## End of part 2

- Next lecture: the differential amplifier