

Design example 1

- The following is a 'rough' design with a number of approximations.
- It can be **validated** by PSPICE simulation and fine-tuning of the parameter values undertaken

Specification

- Design a common-emitter amplifier to the following specification
 - $V_{CC} = 20V$, $A_V > 100$, $V_C \sim V_{CC}/2$, a load of 10k
- Given
 - $\beta_o = 250$, make $R_1 // R_2 \sim 10 \times R_{in}$, $V_{RE} = 10\% V_{CC}$
- Hints
 - First draw the schematic circuit
 - Estimate values for R_C , I_C , R_E , V_B , R_2 , R_1

Draw schematic, find R_C , I_C

* Assume all capacitors are short circuit at frequencies of interest – see later notes for C calculations

How do we achieve a voltage gain of 100?

What is the equation for voltage gain of a CE amp?

$$|A_V| \equiv \frac{v_o}{v_i} = g_m \times ac \text{ load}$$


$$g_m = 40I_C$$

$$ac \text{ load} = \frac{R_C \times 10k}{R_C + 10k}$$

$$\Rightarrow \frac{A_v}{40.I_C} = \frac{R_C \times 10k}{R_C + 10k}$$

$$\frac{120}{40.I_C} = \frac{R_C \times 10k}{R_C + 10k}$$

$$I_C = \frac{20-10}{R_C}$$

 

$$\frac{3R_C}{10} = \frac{R_C \times 10k}{R_C + 10k}$$

$$R_C = 23k$$

$$\text{Hence } I_C = 0.43mA$$

Now consider the DC biasing

$$V_{RE} = 10\%V_{CC} \text{ (stability)}$$

Assume $I_C \sim I_E$

$$R_E = \frac{2V}{0.43mA} = 4.7k\Omega$$


Voltage at V_B ?? $V_B = 2.6V$

How to find R_1, R_2

make $R_1 // R_2 \sim 10 \times R_{in}$

R_{in} ?
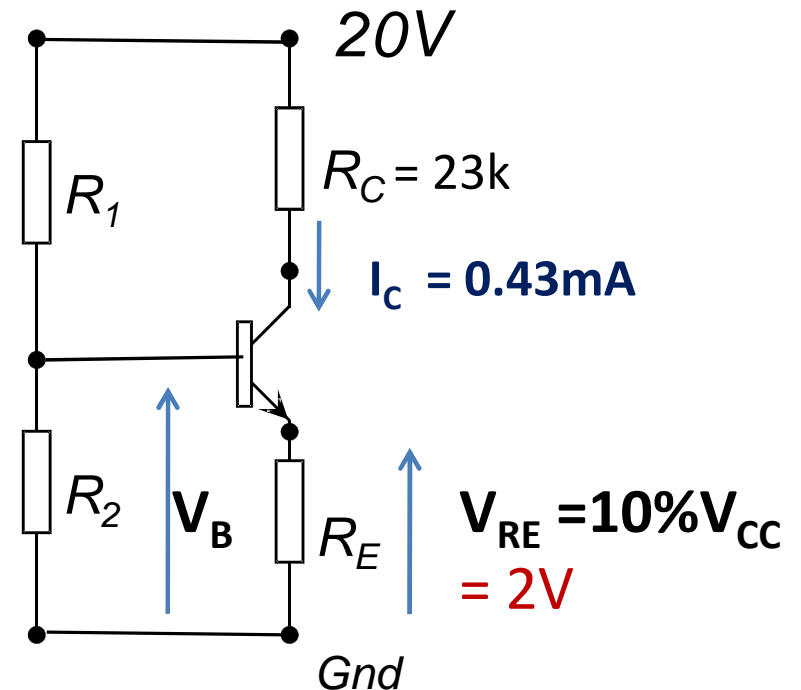
$$R_{in} = r_{be} = \frac{\beta_o}{g_m} = \frac{250}{40 \times 0.43mA} = 14.5k\Omega$$



Now consider the DC biasing

How to find R_1 , R_2

make $R_1 // R_2 \sim 145k$


$$\frac{R_1 \times R_2}{R_1 + R_2} = 145k\Omega$$

Need another equation....

Assume DC base current is small (~ 0) compared to current in bias resistors

$$\Rightarrow \frac{20 - 2.6}{R_1} = \frac{2.6}{R_2} \Rightarrow 17.4R_2 = 2.6R_1$$

Solve 2 equations to give R_1 , R_2

 

$$\begin{aligned} R_1 &= 1.1M\Omega \\ R_2 &= 167k\Omega \end{aligned}$$


SPICE simulation – DC-1

Check :

- DC levels
- approximations

I_C (spec.) = 0.43mA
 I_C (simul.) = 0.33mA

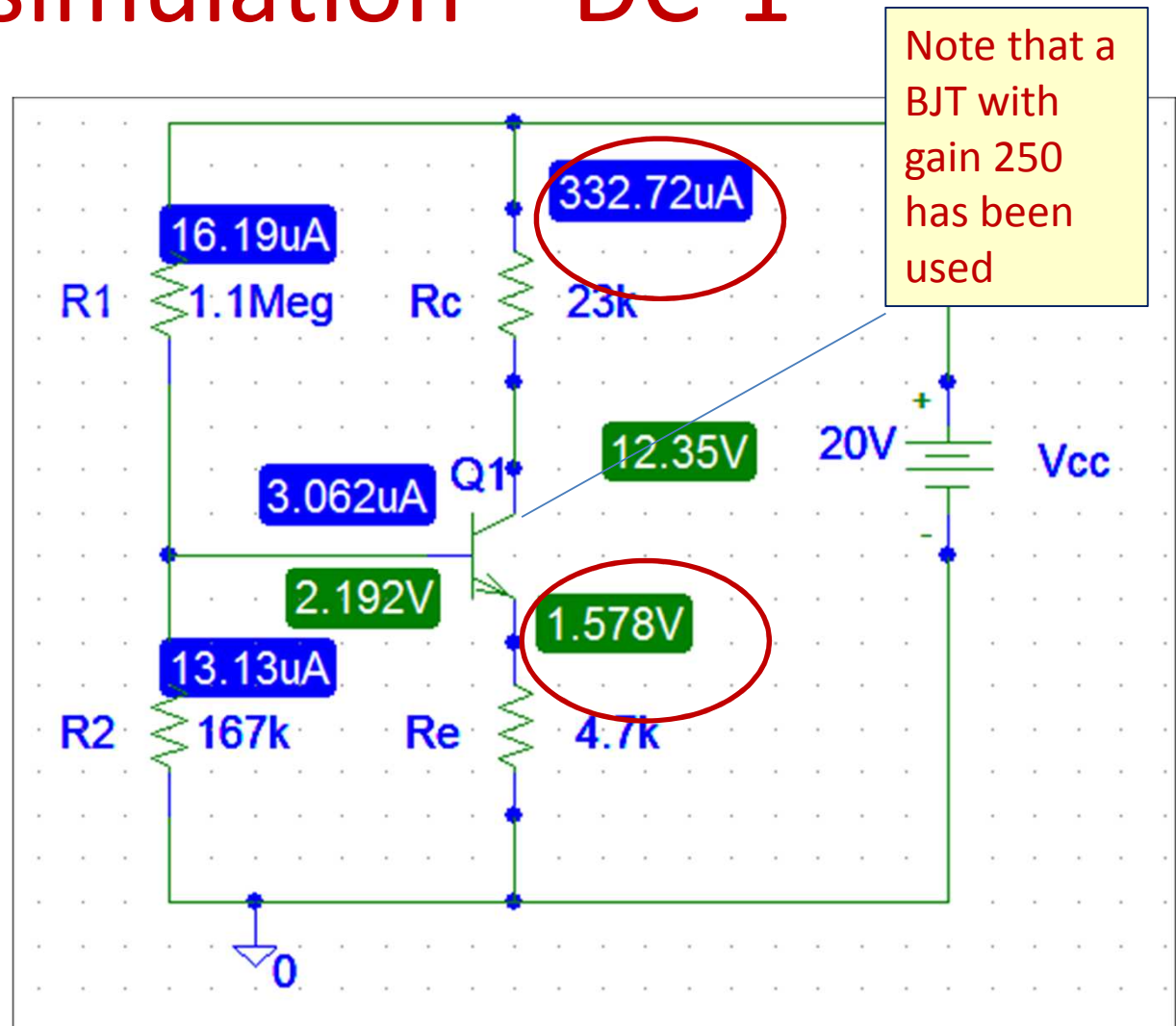Poor agreement
with target
 $I_C = 0.43\text{mA}$




Any ideas Why?? Are the approximations good?

SPICE simulation – DC-2


A more rigorous treatment of the estimate for R_1 , R_2 (or a bit of 'tweaking' to get the voltage levels required.. gives
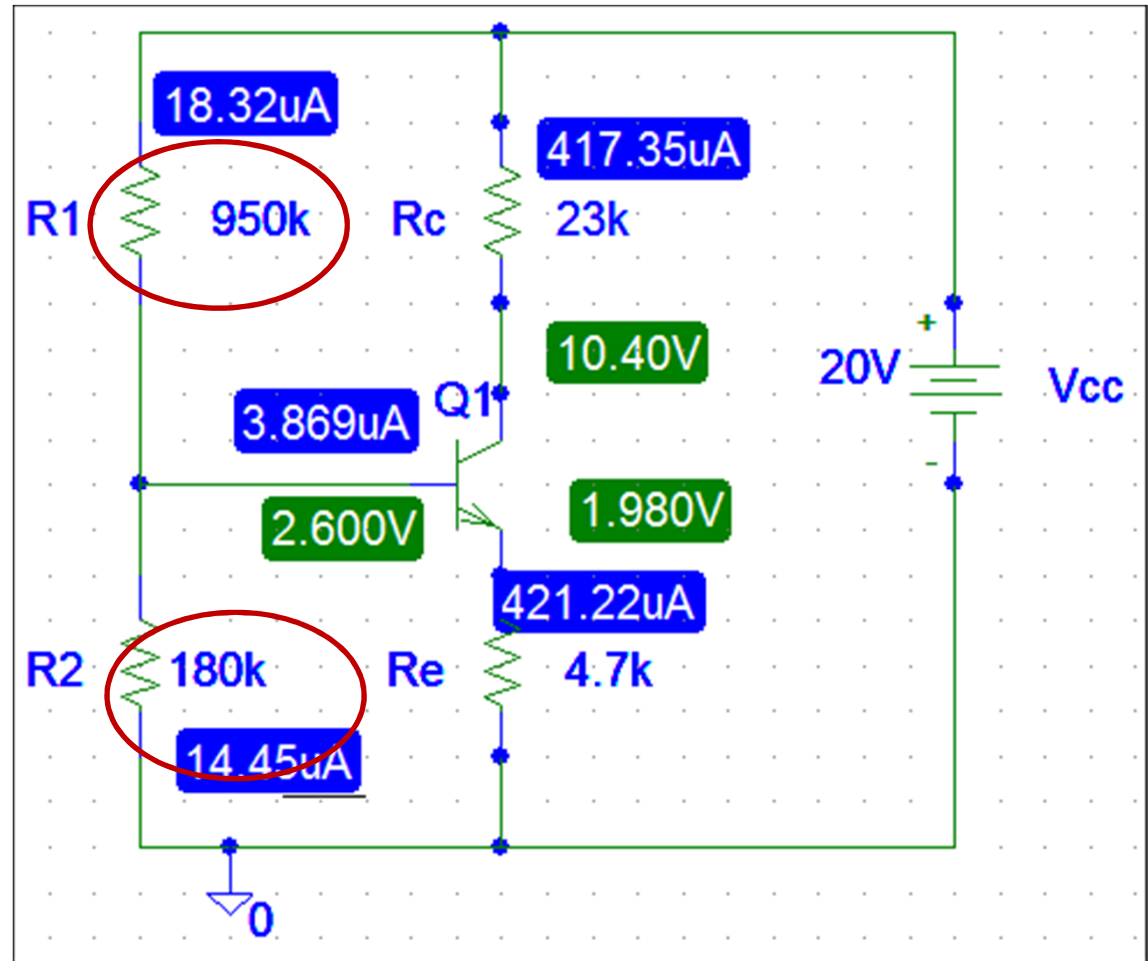
$$I_C (\text{spec.}) = 0.43\text{mA}$$
$$I_C (\text{simul.}) = 0.42\text{mA}$$



Good agreement with target $I_C = 0.43\text{mA}$

Ac simulation

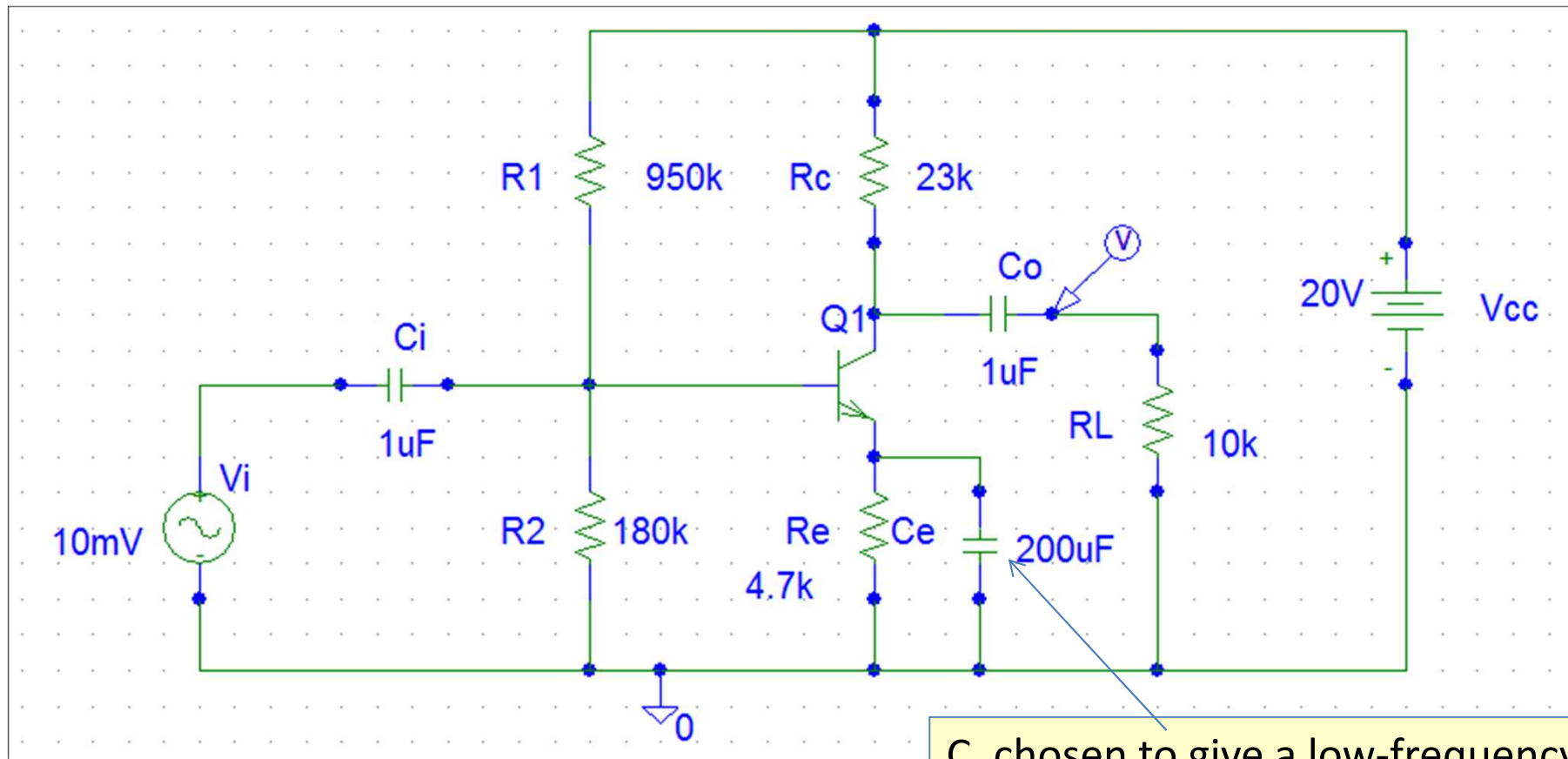


C_e chosen to give a low-frequency roll-off point of 100 Hz

See part 7 for design details for the capacitors, C_i , C_o , C_e

Ac simulation results

Voltage Gain = 108!

 

$$A_V = g_m \times a_{load} \quad \Rightarrow \quad A_V \approx 40 \times 0.42m \times (23 // 10)k\Omega$$

A_V (theory) = 117

A_V (simul.) = 108

Further work

- Find the nearest preferred values to the resistor values
- Work back through the calculations to find the new values for I_C and A_v

Design Exercise 2

Design a 2-stage voltage amplifier to meet the following criteria:

- i) an input resistance of $100\text{ k}\Omega$
- ii) an overall voltage gain > 500 , into a resistor load, R_L

Given: $V_{CC} = 20\text{V}$, $\beta_o = 200$

DC level of the first stage output needs to be set at half the supply voltage.


Allow 10% of V_{CC} across R_E)

Use CE-ED (R_E) stage for the input and a CE stage biased at 1mA

Solution.

The schematic circuit

 **omitting bias resistors and
coupling capacitors**



Design First consider input resistance spec.

$$g_m \times r_{be} = \beta_o$$

$$R_i = r_{be1} + (1 + \beta_o) R_E$$

$$\Rightarrow 100k = \frac{200}{40I_{C1}} + (1 + 200) \frac{2}{I_{C1}} \quad \leftarrow 10\% V_{CC} \text{ across } R_E$$

$$I_{C1} = 4.1mA$$

$$R_E = \frac{2}{4.1m} = 494\Omega$$


$$R_{C1} \sim \frac{20}{2} \frac{1}{4.1m} = 2.5k\Omega \quad \leftarrow V_{CC}/2 \text{ across } R_{C1}$$

Gain of 1st stage is $A_{V1} = -\frac{g_{m1} \times R_{C1} // R_{i2}}{1 + g_{m1} \times R_E}$

$$R_{i2} = r_{be2} = \frac{\beta_o}{g_{m2}} = \frac{200}{40 \times 1mA} = 5k\Omega$$

$$A_{V1} = -\frac{40 \times 0.41m}{1 + 40 \times 0.41m} \frac{2.5 \times 5}{2.5 + 5} k = 3.31$$

 Want total gain to be >500, so $A_{V2} = 500 / 3.31 = 151$; $A_{V2} = 155$ say



Design - 2

Gain of second stage is $A_{V2} = -g_{m2} R_{C2} // R_L$


$$R_{C2} = \frac{10}{1mA} = 10k\Omega \quad \text{What about } R_L ?$$

$$A_{V2} = -40 \times 1m \times \frac{R_L 10k}{R_L + 10k}$$

$$155(R_L + 10k) = -40m \times R_L \times 10k$$

$$155R_L + 1550k = 400R_L$$

$$R_L = 6.3 \text{ k}\Omega$$

 

This is a MINIMUM value to achieve the desired gain!

Note, use the nearest preferred values in a real design so use $R_{in} > 100k$, $A_v > 500$

Gain could be made higher by adding a further CE stage,
Input resistance could be improved by using **feedback**: sacrifice some gain.