

Numerical Solutions to Feedback Problems III

1a) 23, b) 4, c) 1

2. $v_o = v_{g1} + v_{g2}$

3. 5V

4. Answer given in question

5. 1V

6. 102R

7. 22

8. Answer given in question