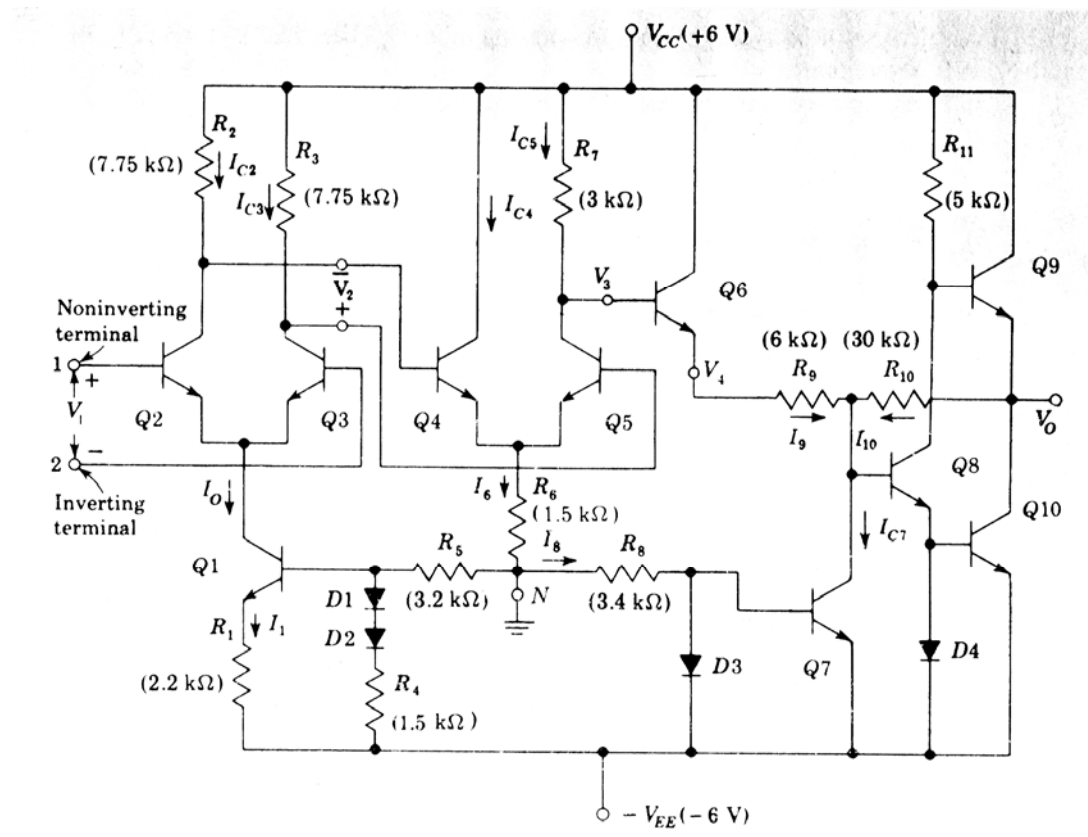


## ELEC271: Case study of a commercial op-amp.

**Exercise:** The figure below shows an early operational amplifier (Motorola MC1530). All transistors are out of saturation, therefore base currents can be neglected. Note also that the diodes  $D_1 - D_4$  are formed by transistors with the base and collector terminals connected together.



I. Identify the circuit building blocks that make up the amplifier.

II. Calculate the following d.c. currents and voltages (applied a.c. voltages at inputs 1 and 2 are both zero).

(i) Voltage at the base of  $Q_1$ , (ii) hence  $I_1$ ,  $I_O$  and  $I_{C2} = I_{C3}$ , (iii) voltage at base of  $Q_4$ , (iv)  $I_{C4} = I_{C5}$ , (v)  $V_3$ ,  $V_4$ , (vi)  $I_8$  hence  $I_{C7}$  (Hint: what is the circuit configuration formed by  $R_8$ ,  $D_3$  and  $Q_7$ ?), (vii) voltage at base of  $Q_8$ , (viii)  $I_9$ , (ix)  $I_{10}$ , (x)  $V_O$

III. Assuming  $\beta_o = 100$  for all transistors:

(xi) calculate the gain of the first stage  $A_{V1} = v_2 / v_1$  (Load is 7.75k in parallel with the input resistance of Diff. Amp. formed by  $Q_4, Q_5 : r_{be4}$ ).

(xii) find the gain of the second stage,  $A_{V2} = v_3 / v_2$

(xiii) hence find the overall gain of the amplifier,  $A_V = v_o / v_1$ . (Hint: the gain of the final stage is set by the ratio of resistors  $R_{10}, R_9$ )