

## **PART 2: Basic bipolar transistor amplifier configurations**

Having established our model for the bipolar transistor, we are in a position to analyse the basic amplifier configurations.

1. Common emitter (CE)
2. Common emitter with emitter degradation (CE-ED)
3. Common collector (CC) also known as emitter follower (EF)
4. Common base (CB)



in terms of voltage and current gains, input and output resistance etc. We will see that each configuration has particular properties that we can usefully employ when building up complex electronic circuits.

The following pages show the circuit schematic diagrams for each configuration and the associated a.c. equivalent circuit for each is shown underneath. We will go through the analyses for CE and CC in the lecture period, to illustrate the basic analytical techniques. The analyses for the other two configurations (CE-ED, CB) are left for you to try.


We will also go through examples of two and three stage amplifiers and the diagrams are given towards the end of this handout.

### **Golden Rules for drawing equivalent circuits**

1. Draw the equivalent circuit of the transistor first
2. Identify the a.c. grounds (voltage sources look like short circuits for a.c. currents!)
3. Convert capacitors to short circuits (we are interested in 'mid-frequency' regimes where the impedance of coupling/de-coupling capacitors is zero)
4. Add the other circuit components (resistors) to obtain the complete equivalent circuit.

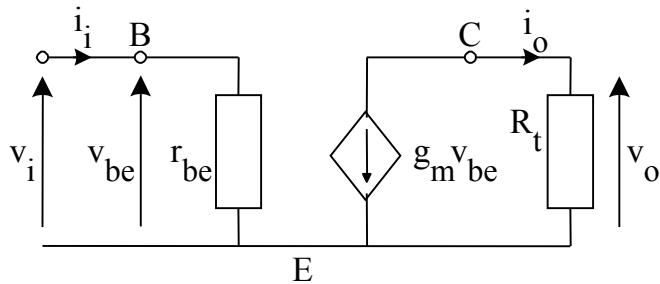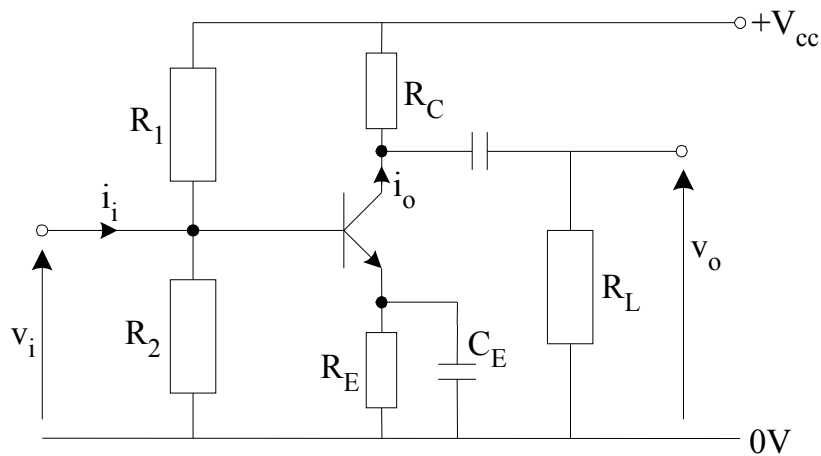**CE**

(analysed overleaf)

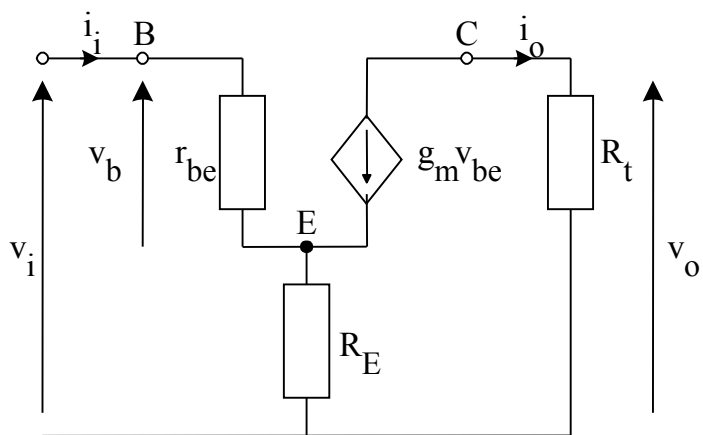**CE - ED**

Remove  $C_E$  in CE circuit above

(for analysis see exercise 2 – you do this one!)

**COMMON EMITTER AMPLIFIER**

Assume amp. biased to some current level  $I_C$  (see 1<sup>st</sup> year notes or equivalent). Knowing  $I_C$ , can calculate  $g_m$  and  $r_{be}$ ;  $\beta_0 (\equiv h_{fe})$  obtained from manufacturers specification sheet.

Simplified hybrid -  $\pi$  equivalent circuit

Voltage Gain,  $A_V$ :

$$A_V = \frac{v_o}{v_i} = \frac{v_o}{v_{be}}$$

$$v_o = i_o R_t = -g_m v_{be} R_t$$

$$\text{so } A_V = -g_m R_t$$

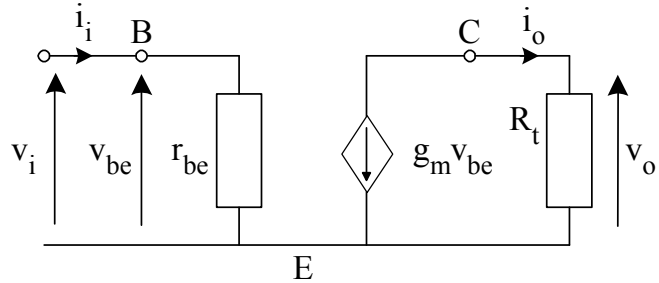


Fig.1

**Include effect of  $r_{bb'}$  and source resistance,  $R_s$  :**

$$A_V = \frac{v_o}{v_i'} = \frac{v_o}{v_{b'e}} \frac{v_{b'e}}{v_i'}$$

$$v_{b'e} = v_i' \frac{r_{b'e}}{r_{b'e} + r_{bb'} + R_s}$$

$$A_V' = -g_m R_t \frac{r_{b'e}}{r_{b'e} + r_{bb'} + R_s}$$

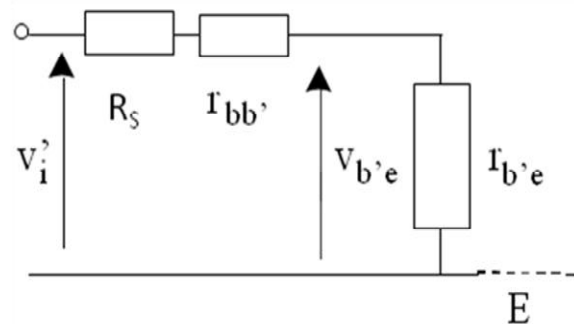


Fig.2

**Note the degradation of voltage gain**

Full treatment – include effect of bias resistors

$$R = R_1 \parallel R_2$$

$$A_V'' = \frac{v_o}{v_i''} = \frac{v_o}{v_{b'e}} \frac{v_{b'e}}{v_i'} \frac{v_i'}{v_i''}$$

$$v_{b'e} = v_i' \frac{r_{b'e}}{r_{b'e} + r_{bb'}}$$

$$v_i' = v_i'' \frac{R \parallel (r_{bb'} + r_{b'e})}{R_s + R \parallel (r_{b'e} + r_{bb'})}$$

$$A_V'' = -g_m R_t \frac{r_{b'e}}{r_{b'e} + r_{bb'}} \frac{R \parallel (r_{bb'} + r_{b'e})}{R_s + R \parallel (r_{b'e} + r_{bb'})}$$

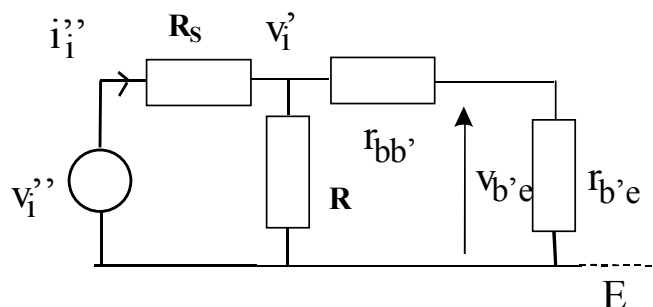


Fig.3

**Input resistance (see Fig.1)**  $R_i = \frac{v_i}{i_i} = r_{be}$  **include  $r_{bb}'$ :**  $R_i = r_{be} + r_{bb}'$  (see Fig.2)

easy to include the effect of R (bias resistors) (see Fig.3):  $R_i' = \frac{v_i'}{i_i'} = R_s + R \parallel (r_{be} + r_{bb}')$

usually make  $R \gg (r_{be} + r_{bb}')$  - so signal goes into the transistor not through the bias resistors!!


**Current gain**  $A_i = \frac{i_o}{i_i}$

We can write:

$$i_o = -g_m v_{be}$$

$$v_{be} = i_i r_{be}$$

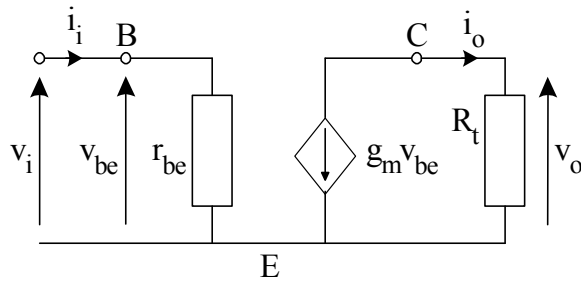
so  $A_i = \frac{i_o}{i_i} = -g_m r_{be} = -\beta_o$  (Q: what is the effect of including  $r_{bb}'$ ??)



### Output resistance:

**Technique:**

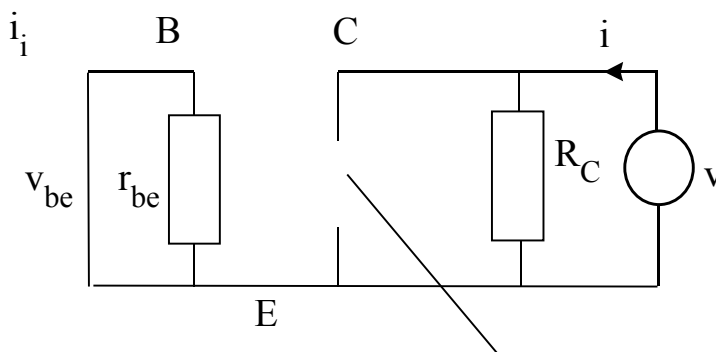1. Set i/p voltage = 0
2. Let  $R_L \rightarrow \text{infinity}$
3. Drive o/p terminal by a volt source,  $v$




Then output resistance,  $R_o \equiv \frac{v}{i} = R_C$   **$V_{be} = 0$ , so no current**

So here,  $R_o = R_C$


**Including the effect of  $r_{ce}$ :**  $R_o = R_C \parallel r_{ce}$

## COMMON COLLECTOR (emitter-follower) AMPLIFIER

The schematic circuit.

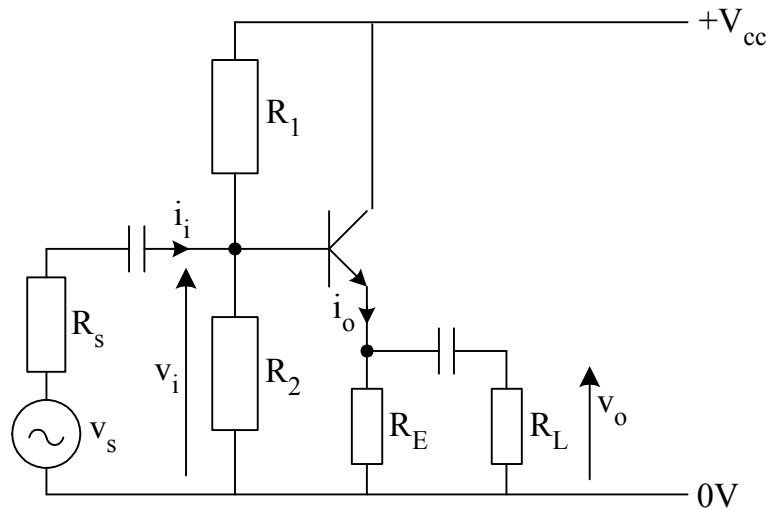

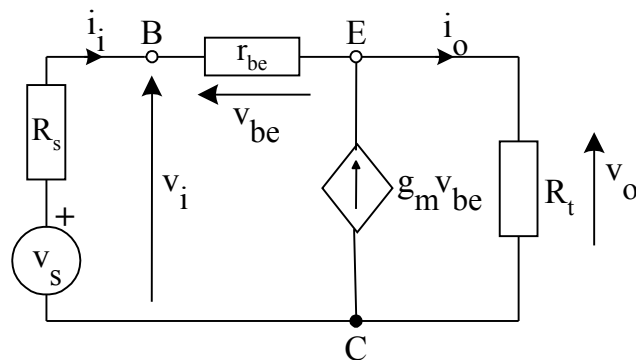The a.c., small signal equivalent circuit



$$R_t = R_E // R_L$$

Assume  $R_1 // R_2$  very large

**Q: what is meant by ‘small signal’? (see earlier notes) Does it mean ‘small amplitude’ or ‘small frequency’?**

### Voltage Gain

$$v_o = i_o R_t \quad (1)$$

$$\text{KCL at node E: } i_i + g_m v_{be} = i_o = \frac{v_o}{R_t} \quad (2)$$

$$\text{also } v_{be} = v_i - v_o \quad \text{and } i_i = \frac{v_i - v_o}{r_{be}} \quad (3)$$

$$\text{Substitute for } i_i \text{ and } v_{be} \text{ in Eqn.(2): } \frac{(v_i - v_o)}{r_{be}} + g_m (v_i - v_o) = \frac{v_o}{R_t}$$

$$\text{Multiply across by } r_{be}: v_i - v_o + \beta_o v_i - \beta_o v_o = v_o \frac{r_{be}}{R_t} \quad (\text{where } \beta_o = g_m r_{be} \text{ is used - see part 1 notes})$$

Rearranging:  $v_o + \beta_o v_o + v_o \frac{r_{be}}{R_t} = v_i + \beta_o v_i$

(note the technique; all the terms involving  $v_o$  are gathered on the LHS and those involving  $v_i$  on the RHS)

$$v_o \left( 1 + \beta_o + \frac{r_{be}}{R_t} \right) = v_i (1 + \beta_o) \quad \text{and finally, } A_V \equiv \frac{v_o}{v_i} = \frac{(1 + \beta_o)}{1 + \beta_o + \frac{r_{be}}{R_t}}$$

**Notice straight away that the voltage gain must be less than 1!**

Assuming now, that  $\beta_o \gg 1$ ,

get an approximate but quite accurate estimate for the voltage gain:  $A_V \approx \frac{v_o}{v_i} = \frac{\beta_o}{\beta_o + \frac{r_{be}}{R_t}}$

Which can also be written as  $A_V \equiv \frac{v_o}{v_i} = \frac{g_m R_t}{1 + g_m R_t}$  for the common-collector gain.

**Q: What use is an amplifier with gain less than 1!**

Let's look at the **input resistance**

This is defined as:  $R_i \equiv \frac{v_i}{i_i}$

Take a KVL:  $v_i = i_i r_{be} + v_o$  (1)

Where  $v_o = i_o R_t$  (2)

Now take KCL at node 'E'

$$i_o = i_i + g_m v_{be}$$

Which can also be written as

$$i_o = i_i + \beta_o i_i \quad (3)$$

Sub. (3) into (2):  $v_o = i_i R_t (1 + \beta_o)$


Sub. into (1):  $v_i = i_i r_{be} + i_i R_t (1 + \beta_o)$

(note again the technique; we have gathered all the terms involving  $v_i$  on the LHS and those involving  $i_i$  on the RHS)

and so:  $R_i \equiv \frac{v_i}{i_i} = r_{be} + R_t (1 + \beta_o)$

Recall the input resistance of the CE amp ( $r_{be}$ ). So the input resistance of the CC amp is boosted by the factor  $R_t (1 + \beta_o)$ ! The CC amp has high input resistance!

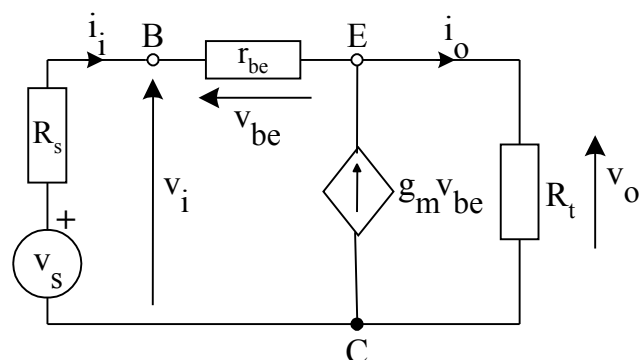**Q: Is this any use?? Let's also look at the output resistance – a rather long analysis .....**




(Diagram repeated from previous page for clarity)

### Common Collector, Output resistance
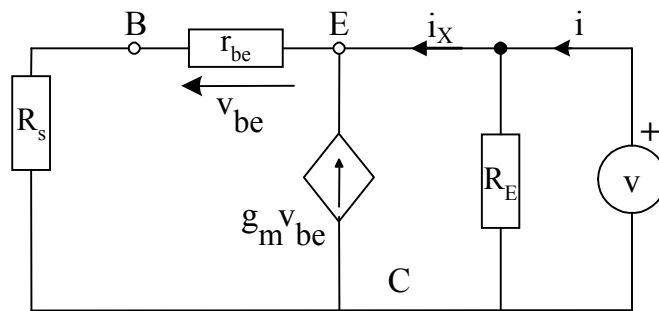
#### Set up the analysis

Suppress (ie short out), the signal source  $v_s$ .

Apply a voltage source to the output – to force a current into the amplifier. The output resistance is then given by  $R_o = \frac{v}{i}$ . We must find this by appropriate circuit analysis.



We can write  $i = \frac{v}{R_E} + i_X$  (1)

Apply KCL:  $i_X + \beta_o i_i + i_i = 0$ ,  $\therefore i_X = -(1 + \beta_o) i_i$  (2)

Need to get rid of  $i_i$ ! write,  $v = -i_i (R_s + r_{be})$  (3)

(1) implies,  $i = \frac{v}{R_E} - (1 + \beta_o) i_i$  which is  $i = \frac{v}{R_E} + i_X$  from (2)

Substitute (3) to get,  $i = \frac{v}{R_E} + \frac{(1 + \beta_o)}{R_s + r_{be}} v$  (4)

(\* Nearly there! - we have 'i' on LHS and terms in 'v' on RHS – which is what we wanted!



We can write (4) in the form:  $\frac{i}{v} = \frac{1}{R_E} + \frac{1 + \beta_o}{R_s + r_{be}}$

That is,  $R_o = \frac{v}{i} = R_E // \frac{R_s + r_{be}}{1 + \beta_o}$  (Note that  $\frac{R_s + r_{be}}{1 + \beta_o}$  has units of ohms)


$\beta_o$  is large, so we can predict that  $R_o$  is small...

**Conclusions: The CC has large (ish) input resistance and small output resistance – but no voltage gain!**

Use it to 'match' high impedance source to low impedance load stages (see 'Design an Op-amp' assignment later in the year.)

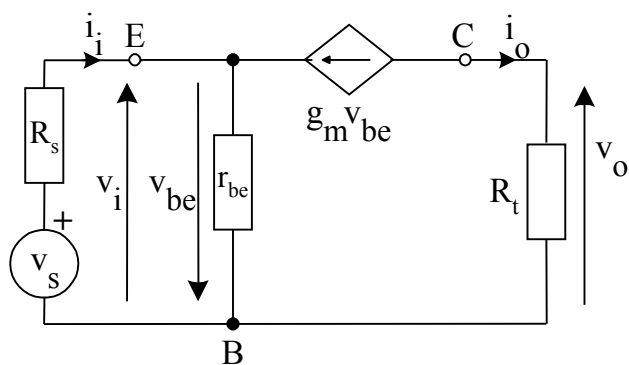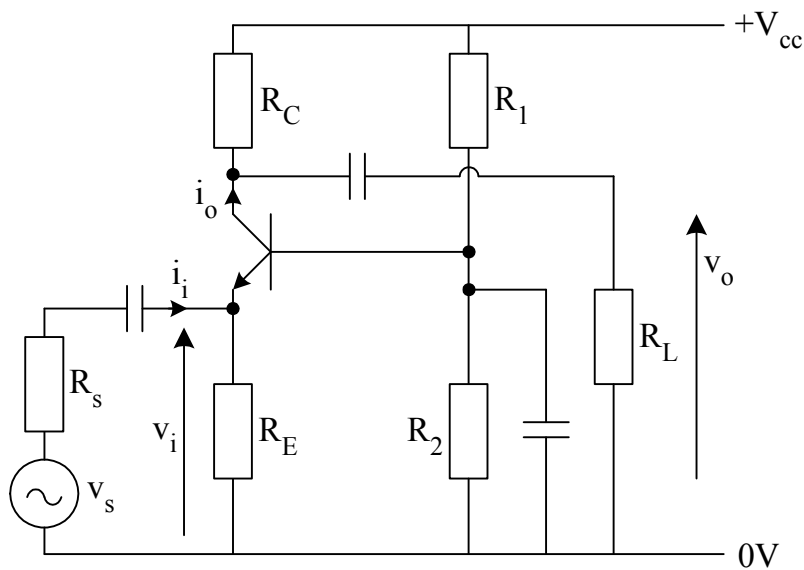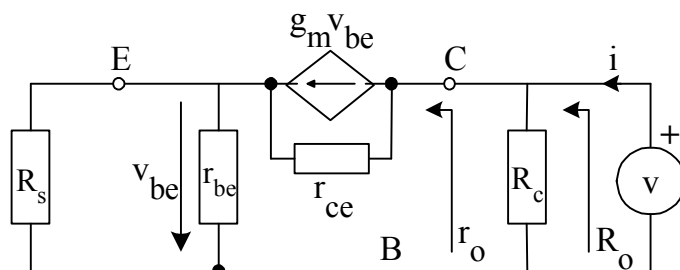**CB****Note**

$R_E$  assumed to be much greater than  $R_{in}$




Equivalent circuit for finding output resistance,  $R_o$

*(for analysis see exercise 3 – you do this one!)*



## Glossary of amplifier properties

### Common Emitter

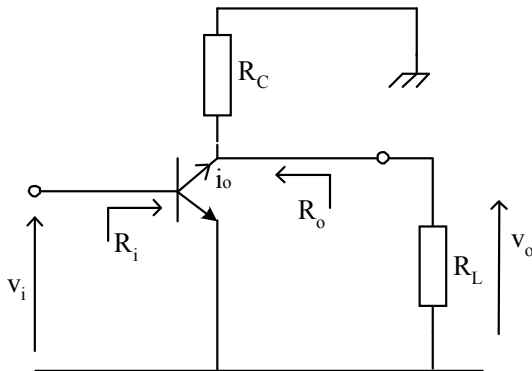

$$R_i = r_{be}$$


$$R_o = R_C$$

$$A_V = \frac{v_o}{v_i} = -g_m R_C // R_L$$

$$G_M = \frac{i_o}{v_i} = -g_m$$

$$R_M = -\beta_o R_C // R_L$$
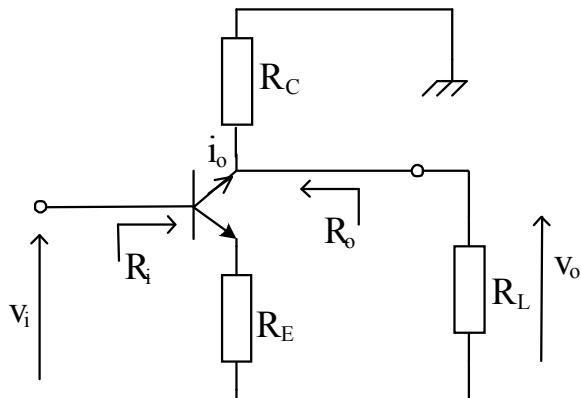
### Common emitter with emitter degradation



$$R_i = r_{be} + (1 + \beta_o) R_E$$


$$R_o = R_C$$

$$A_V = -\frac{g_m R_C // R_L}{1 + g_m R_E}$$

$$G_M = -\frac{g_m}{1 + g_m R_E}$$

$$R_M = -\beta_o R_C // R_L$$

### Common collector (Emitter follower)

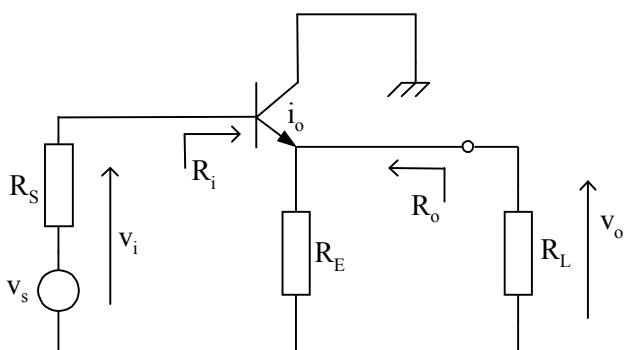


$$R_i = r_{be} + (1 + \beta_o) R_E // R_L$$

$$R_o = \frac{r_{be} + R_S}{1 + \beta_o} // R_E$$

$$A_V = \frac{g_m R_E // R_L}{1 + g_m R_E // R_L}$$

$$G_M = \frac{g_m}{1 + g_m R_E // R_L}$$

$$R_M = (1 + \beta_o) R_E // R_L$$

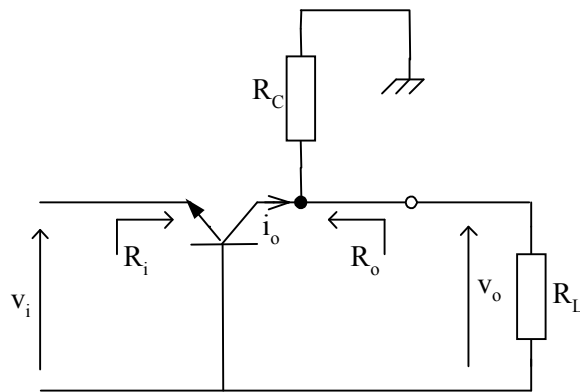**Common base**

$$R_i = \frac{r_{be}}{1 + \beta_o} \approx 1 / g_m = r_e \quad R_o \sim R_C$$


$$A_V = g_m R_C // R_L$$

$$G_M = g_m \quad R_M = \frac{\beta_o R_C // R_L}{1 + \beta_o}$$

### Summary of properties of amplifier configurations

Property	$A_V$	$A_I$	$R_{in}$	$R_{out}$	Usage
<b>CE</b>	high	high	Medium	high	Most useful, general purpose
<b>CE-ED</b>	Low	high	high	high	$R_E$ constitutes feedback – sacrifice $A_V$ for increased stability: less dependent on $\beta_o$ (also temperature), increase $R_{in}$
<b>CC</b>	Low ( $< 1$ )	high	high	low	Impedance matching – high R-source to low-R load (also very linear – used in power amp. Output stages)
<b>CB</b>	high	low ( $< 1$ )	low	high	Impedance matching – low R-source to high-R load (also features in Diff.Amp. – see later notes)

Multi-stage amplifiers can thus be configured to provide, for example, very high input impedance, high voltage and current gain and low output impedance.

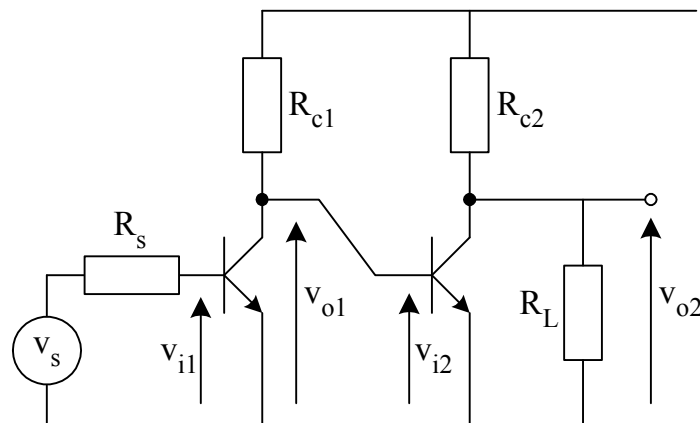**Example of a two stage amplifier**

Function: Voltage amplification - both stages have large voltage gain

Overall voltage gain is  $A_{V_s} = \frac{v_{o2}}{v_s} = \frac{v_{o2}}{v_{i2}} \times \frac{v_{i2}}{v_{i1}} \times \frac{v_{i1}}{v_s}$

But  $v_{i2} = v_{o1}$  so:-  $A_{V_s} = \frac{v_{o2}}{v_{i2}} \times \frac{v_{o1}}{v_{i1}} \times \frac{v_{i1}}{v_s}$

that is,  $A_{V_s} = A_{V2} \times A_{V1} \times \frac{R_{i1}}{R_{i1} + R_s}$

'Coupling' term:  $R_s$   
'loads' the input

$$A_{V2} = -g_{m2} R_L // R_{C2}$$


that is, ' $g_m$  x the ac load'

$$A_{V1} = -g_{m1} R_{C1} // R_{i2}$$

must take account of the loading  
effect of the second stage on the  
first ( $R_{i2}$ )

Note that  $R_{i2} = r_{be2}$ ,  $g_{m2} = 40 I_{C2}$ ,  $R_{i1} = r_{be1}$

( $r_{be} g_m = \beta_o$ )

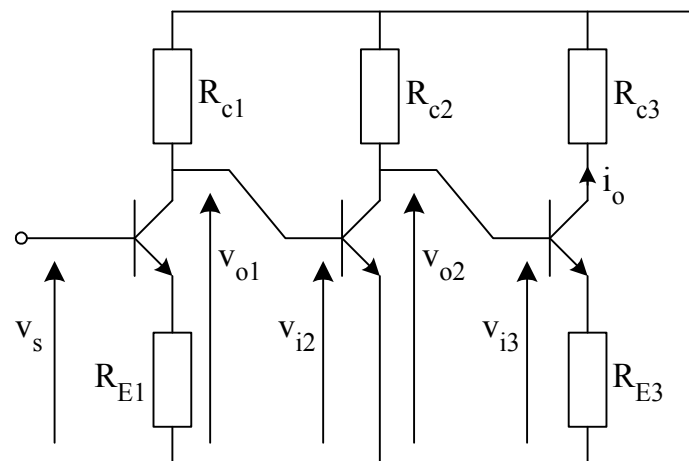**Example of a three stage amplifier**

**Function:** *transconductance amplifier* – turns an input voltage signal  $v_s$  into an output current signal  $i_o$  with appropriate enlargement (amplification) of the signal. In this case the current is into the collector load  $R_{C3}$ . A practical example of the use of such an amplifier could be in driving a light emitting diode (l.e.d) which would replace the resistor. First stage provides for high input resistance and some voltage gain, second stage provides high voltage gain, third stage converts voltage to current.

Overall transconductance gain is 
$$G_M = \frac{i_o}{v_s} = \frac{i_o}{v_{i3}} \times \frac{v_{i3}}{v_{i2}} \times \frac{v_{i2}}{v_s}$$

That is, 
$$G_M = \frac{i_o}{v_{i3}} \times \frac{v_{o2}}{v_{i2}} \times \frac{v_{o1}}{v_{i1}}$$

or 
$$G_M = G_{M3} \times A_{V2} \times A_{V1}$$

$$A_{V1} = -\frac{g_{m1}R_{t1}}{1 + g_{m1}R_{E1}}$$

First stage is CE-ED. Must take account of the loading effect of the second stage on the first

$$R_{t1} = R_{C1} // R_{i2}$$

$R_{i2}$  is the input resistance of the 2<sup>nd</sup> stage;  $R_{i2} = r_{be2}$

3<sup>rd</sup> stage is CE-ED  
want the transconductance gain

$$G_{M3} = -\frac{g_{m3}}{1 + g_{m3}R_{E3}}$$

$$A_{V2} = -g_{m2}R_{t2}$$


2<sup>nd</sup> stage is CE, loaded by stage 3

$$R_{t2} = R_{C2} // R_{i3}$$

## Exercises

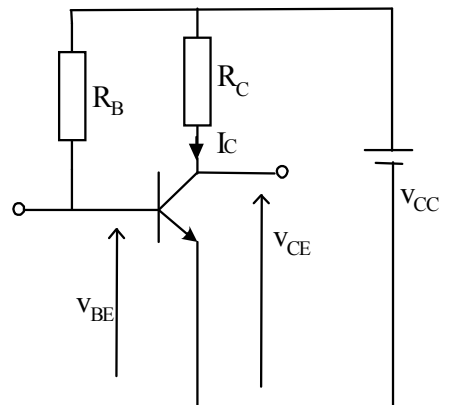1. Consider the circuit shown opposite.

- What are the disadvantages of the biasing arrangement?
- The circuit is to be designed such that  $V_{CE}$  is fixed at  $\sim V_{CC}/2$ . Why would this be desirable?
- What is the voltage gain of the circuit?
- What is the effect on the voltage gain of increasing  $R_C$  subject to the constraint of b)?



2. For the common emitter amplifier with emitter degradation show that:-

- $A_i = i_o/i_i = -\beta_o$
- $R_i = v_i/i_i = r_{be} + (1+\beta_o)R_E$
- $$A_v = \frac{v_o}{v_i} = \frac{-\beta_o R_t}{r_{be} + (1+\beta_o)R_E}$$

$$\approx \frac{-g_m R_t}{1 + g_m R_E}$$

$$\approx -\frac{R_t}{R_E} \text{ if } g_m R_E \gg 1$$

d)  $R_o \approx R_c$

e)

$$G_M = \frac{i_o}{v_i} = \frac{-\beta_o}{r_{be} + (1+\beta_o)R_E}$$

$$\approx \frac{-g_m}{1 + g_m R_E}$$

f)  $R_M = \frac{v_o}{i_i} = -\beta_o R_t$

For circuit see handout.

(NOTE: this is the so-called 'transconductance gain')

(NOTE: this is the so-called 'transresistance gain')

3. For the common base amplifier show that:-

- $A_i = i_o/i_i = \beta_o/(\beta_o + 1)$
- $R_i = v_i/i_i = r_e = r_{be}/(1 + \beta_o)$
- $A_v = \frac{v_o}{v_i} = g_m R_t; R_t = R_c // R_L$
- $R_o = R_c // r_o$  where  $r_o = r_{ce} [1 + g_m(r_{be} // R_s)]$
- $G_M = i_o/v_i = g_m$
- $R_M = v_o/i_i = \beta_o R_t/(1 + \beta_o)$

For circuit consult handout.

4. In figure 1 below, the biasing components have been omitted. The transistors are identical with  $\beta_o = 200$ .  $I_{c1} = 1 \text{ mA}$  and  $I_{c2} = 5 \text{ mA}$ .  $R_{c1} = 5 \text{ k}\Omega$ ,  $R_{c2} = 1 \text{ k}\Omega$ ,  $R_{E2} = 150 \Omega$ ,  $R_s = 1 \text{ k}\Omega$ .

Calculate  $g_{m1}$ ,  $g_{m2}$ ,  $r_{be1}$  and  $r_{be2}$ .

Calculate  $R_i$ ,  $R_o$ ,  $A_v = v_o/v_i$  and  $A_{vs} = v_o/v_s$ .

(Ans  $R_i = 5 \text{ k}\Omega$ ,  $R_o = 1 \text{ k}\Omega$ ,  $A_v = +1111$ ,  $A_{vs} = +926$ ).

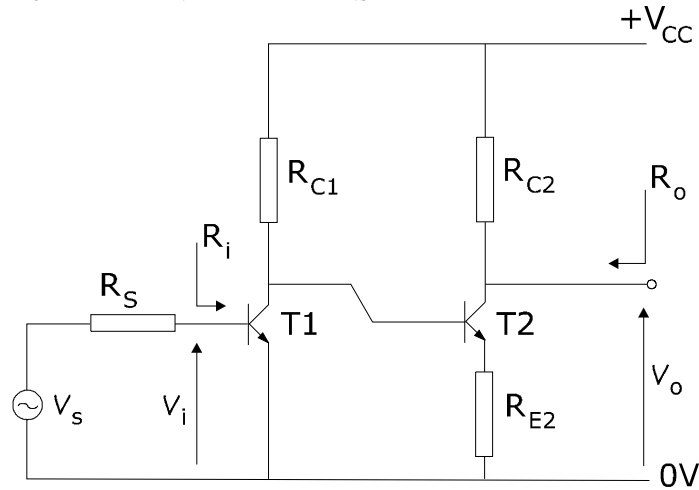


Figure 1

5. In figure 2 the biasing components have been omitted. The transistors are identical with  $\beta_o = 99$  and  $r_{be} = 2 \text{ k}\Omega$ .  $R_c = 3 \text{ k}\Omega$ ,  $R_E = 50 \Omega$  and  $R_s = 600 \Omega$ .

Calculate the transresistance gain  $v_o/i_s$ .

(Ans -  $34.2 \times 10^3 \Omega$ ).

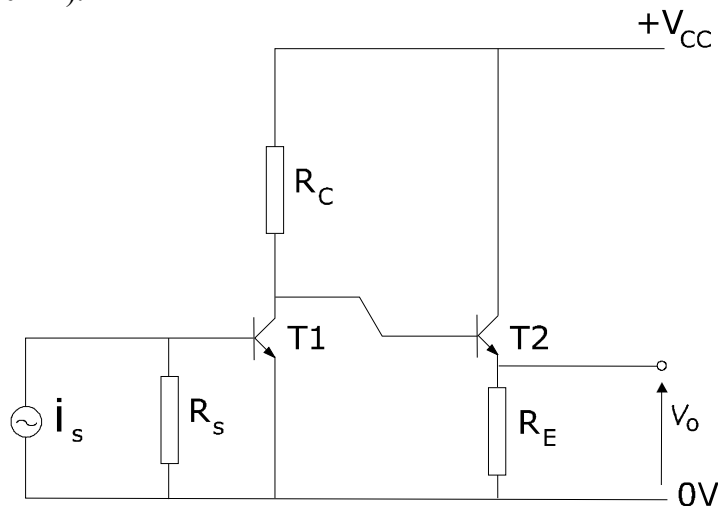


Figure 2

**Hint:** Apply the chain rule to find the components of the overall gain; you should find

$$R_M = A_{V2} \times A_{V1} \frac{R_s \times r_{be1}}{R_s + r_{be1}}$$