 


### Differential amplifier with active loads – explanation of operation and summary of analysis

Now address the problem of achieving a large load resistor,  $R_C$  for high gain without upsetting d.c. conditions. Consider the circuit below where the collector resistors have been replaced by a current mirror:



We investigate the operation by first considering the inputs grounded (d.c. operation). Current mirror action in  $T_3$  and  $T_4$  means that  $I_{C3} = I_{C4}$  always. Also, assuming base currents are negligible,  $I_{C3} = I_{C1}$ . With grounded inputs and assuming perfectly matched transistors,  $I_{C1} = I_{C2} \approx I_O/2$ . Hence  $i_o = 0$  (as  $I_{C4} = I_{C1}$ ). With a differential signal applied such that  $v_{i1}$  is going more positive and  $v_{i2}$  is going less positive,  $I_{C1}$  ( $= I_{C3}$ ) will rise and hence so will the current  $I_{C4}$ , by current mirror action. However,  $I_{C2}$  will fall hence

$$i_o = I_{C4} - I_{C2} = I_{C1} - I_{C2} \\ = g_m v_{i1} - g_m v_{i2} = g_m (v_{i1} - v_{i2}) = g_m v_{id} \text{ (as 'I}_C = g_m v_{in}\text{')}$$

the configuration is thus best thought of as a *transconductance* amplifier:

$$G_m = \frac{i_o}{v_{id}}$$

#### Voltage gain

Recall that for the voltage gain of a diff. amp. with resistors  $R_C$ , the differential voltage gain was  $g_m R_C$ . As the ' $R_C$ ' is now the *dynamic* resistance 'looking up' into the collectors of the current mirror. We might 'guess' that the voltage gain now becomes

$$A_{vd} = g_m (r_{ce4} // r_{ce2} // R_L) \\ \sim g_m (r_{ce4} // r_{ce2}) \text{ if } R_L \text{ is very big (infinity say)}$$

Voltage gain is thus large without the need for a very large (area consuming) discrete resistor.

**Exercise:** Assuming that the guess is correct, show that  $A_{Vd}$  can be expressed in terms of the Early voltages ( $V_{An}$ ,  $V_{Ap}$ ):

$$A_{Vd} = \frac{1}{V_T} \frac{V_{An} V_{Ap}}{V_{An} + V_{Ap}} \quad [\text{recall that } g_m = I_C/V_T \text{ and } r_{ce} = V_A/I_C]$$

**Solution**

The output resistance of  $T_2 = V_{An}/I_C$


The output resistance of  $T_4 = V_{Ap}/I_C$

$$\text{Without } R_L \text{ we have } A_{Vd} = g_m (r_{ce2} // r_{ce4}) = \frac{I_C}{V_T} \frac{\frac{V_{An}}{I_C} \frac{V_{Ap}}{I_C}}{\frac{V_{An}}{I_C} + \frac{V_{Ap}}{I_C}} = \frac{1}{V_T} \frac{V_{An} V_{Ap}}{V_{An} + V_{Ap}} \text{ as required}$$

**Note that:-**

 1. We have assumed above that the amplifier is driving an infinitely large resistance load  $R_L$ . In reality, the 'load' resistance would be  $R_L // r_{ce2} // r_{ce4} \rightarrow R_L$  (if  $R_L \ll r_{ce}$ ) and the high gain can therefore be severely reduced by the loading of the following stage. However, we could ensure a high resistance for the following stage by making it an emitter follower (high input resistance) and thus high voltage gain could be realised.
2. The d.c. output voltage level is a ' $V_{BE}$  (on)' drop less than the supply rail  $V_{CC}$ . Thus the d.c. output voltage is  $(V_{CC} - 0.7 \text{ V})$ . This implies that only a very small (a.c.) voltage swing is allowed at  $v_o$ . However, it must be recalled that in the main purpose of achieving very high gain amplifiers is to 'trade' the gain for feedback to stabilise and enhance the overall performance (input and output resistance etc.). Thus a large amount of negative feedback is generally used and this tends to make  $v_{in1} \rightarrow v_{in2}$ . (See 2<sup>nd</sup> semester notes on feedback.)
3. Both high transconductance (gain) and high input resistance are required and this constitutes a design trade-off. (See earlier notes for ways of increasing input resistance.)
4. greatly improved common mode rejection because of the large dynamic resistance of the current source  $I_o$
5. the current mirror effectively provides the 'subtraction' of the outputs so the output can be taken single ended.

We will derive the expression for gain again, by considering the a.c. equivalent circuit. We seek an equivalent circuit for the current mirror load: what ‘resistance’ is seen looking up into the current mirror?




$$R_o = r_{be4} // r_{be3} // \frac{1}{g_m} // r_{ce3} \approx \frac{1}{g_m}$$

[illegible]
$$\text{So } v_o = g_m v_{id} R_L$$

$$v_{i1} = i_i r_{be}; \quad v_{i2} = -i_i r_{be} \quad \text{so} \quad v_{id} = i_i r_{be} - (-i_i r_{be}) \quad \text{and} \quad \text{Diff. input resistance, } R_{id} = \frac{v_{id}}{i_i} = 2r_{be}$$

### Include the effect of $r_{ce}$ 's

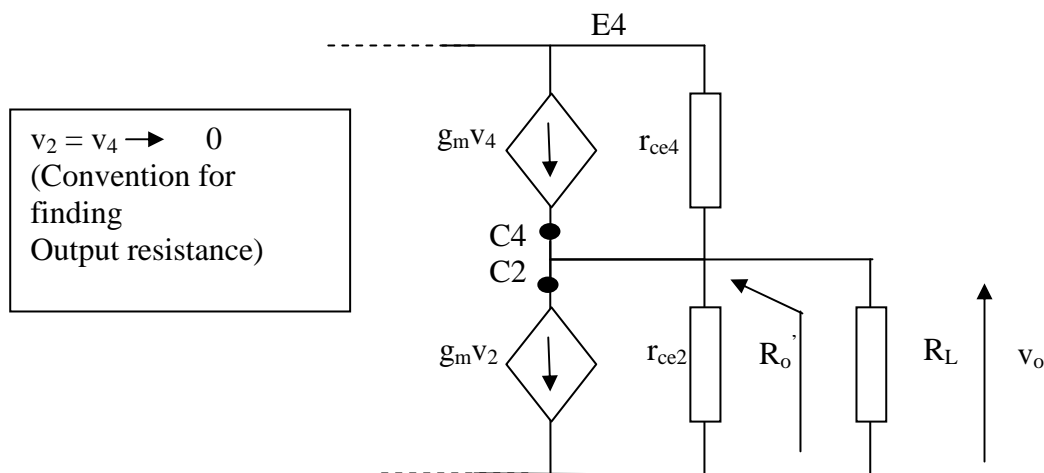

As  $v_2$  and  $v_4$  are set to zero (by convention for finding output resistance, the a.c. load is by inspection,  $R_o = r_{ce4}/r_{ce2}$  and  $R_o = r_{ce4}/r_{ce2}/R_L$

**So without  $R_L$   $A_{Vd} = g_m(r_{ce4} // r_{ce2})$  - VERY HIGH**

**But with  $R_L$ ,  $A_{Vd} = g_m (r_{ce4} // r_{ce2} // R_L)$**

and if  $R_L \ll r_{ce4} // r_{ce2}$ , then  $A_{Vd} \sim g_m R_L$  - VOLTAGE GAIN MUCH REDUCED if  $R_L$  small

→ so ensure that the differential amplifier with active loads is not fed into a low impedance stage.


### Common Mode Gain

**Currents in left and right- hand sides of the circuit are the same (by CM action), so**

$$\dot{\mathbf{i}}_o = \mathbf{0}$$

$$\mathbf{v}_0 = \mathbf{0}$$

$$\mathbf{A}_{\text{vc}} = \mathbf{0}$$

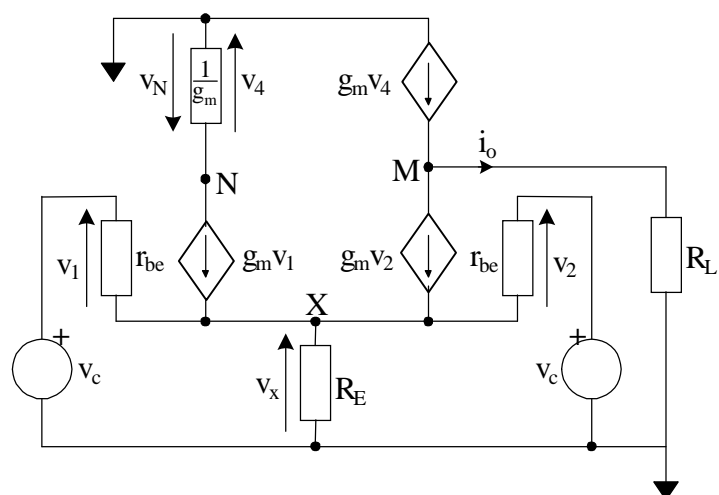


Note that  $\mathbf{g}_m \mathbf{v}_1 = \mathbf{g}_m \mathbf{v}_2$  - also,  $\mathbf{v}_4 = \mathbf{v}_1$  (see previous page); hence  $\mathbf{i}_0 = 0$  and  $\mathbf{v}_0 = 0$ ;  $\mathbf{A}_{cm} = 0$ !

**Conclusion:** By the use of active loads and a current source, we have achieved the objective of both high gain and large CMRR. We have ‘de-coupled’ the a.c. and d.c. roles of the biasing components.

We are now in a position to analyse a ‘real’ operational amplifier using our knowledge of d.c. biasing techniques, a.c. equivalent circuits and multi-stage amplifiers (see Ex.2).

**Exercises**

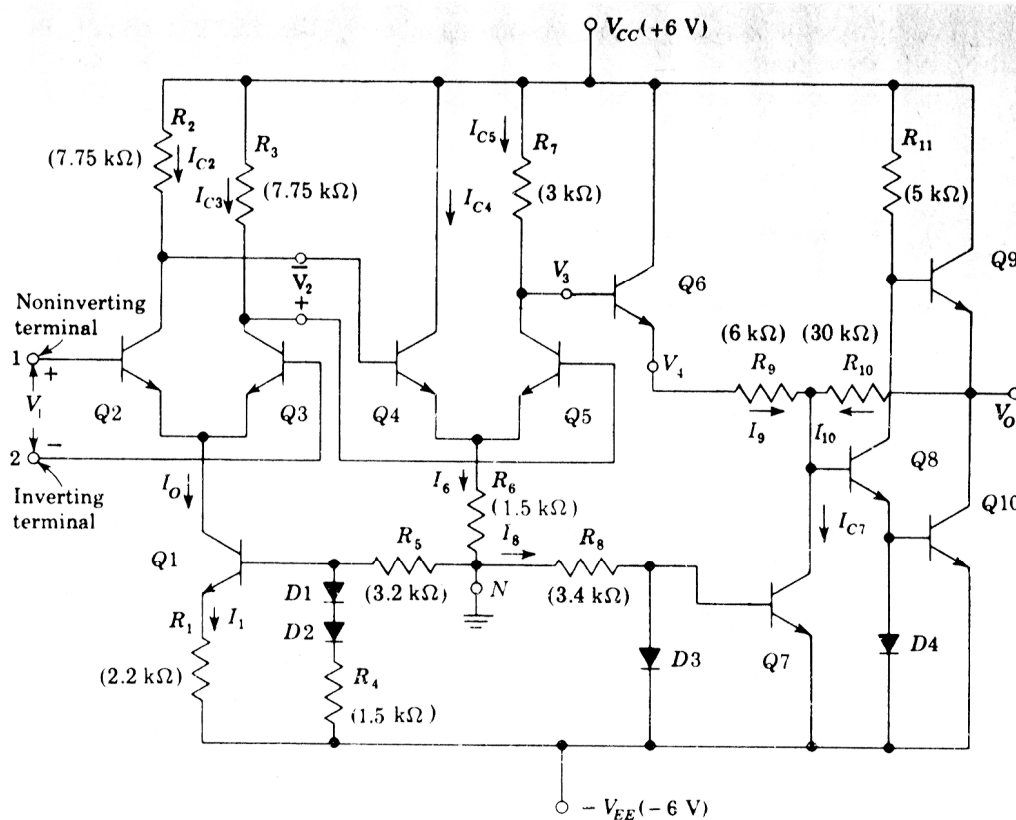1. Consider a common-emitter amplifier with a current mirror load. Work out an expression for the voltage gain in terms of the Early voltages.
2. The figure below shows an early operational amplifier (Motorola MC1530). All transistors are out of saturation, therefore base currents can be neglected. Note also that the diodes  $D_1 - D_4$  are formed by transistors with the base and collector terminals connected together.



I. Identify the circuit building blocks that make up the amplifier.

II. Calculate the following d.c. currents and voltages (applied a.c. voltages at inputs 1 and 2 are both zero).

- (i) Voltage at the base of  $Q_1$ , (ii) hence  $I_1$ ,  $I_O$  and  $I_{C2} = I_{C3}$ , (iii) voltage at base of  $Q_4$ , (iv)  $I_{C4} = I_{C5}$ , (v)  $V_3$ ,  $V_4$ , (vi)  $I_8$  hence  $I_{C7}$  (Hint: what is the circuit configuration formed by  $R_8$ ,  $D_3$  and  $Q_7$ ?), (vii) voltage at base of  $Q_8$ , (viii)  $I_9$ , (ix)  $I_{10}$ , (x)  $V_O$

III. Assuming  $\beta_o = 100$  for all transistors:

(xi) calculate the gain of the first stage  $A_{V1} = v_2/v_1$  (Load is 7.75k in parallel with the input resistance of Diff. Amp. formed by  $Q_4, Q_5 : r_{be4}$ ).

(xii) find the gain of the second stage,  $A_{V2} = v_3/v_2$

(xiii) hence find the overall gain of the amplifier,  $A_V = v_O/v_1$ . (Hint: the gain of the final stage is set by the ratio of resistors  $R_{10}, R_9$ )