


## Exercises

1. Calculate  $g_m$ ,  $r_e$  and  $r_{be}$  when  $I_C = 10 \mu A$  and when  $I_C = 0.25mA$ . Comment on the values ( $\beta_o = 200$ )

$$g_m = 40I_C \quad r_e = 1/g_m \quad r_{be} = \beta_o / g_m$$

$I_C$	$g_m$	$r_e$	$r_{be}$
<b>10<math>\mu A</math></b>	<b>0.4 mA/V</b>	<b>2.5k<math>\Omega</math></b>	<b>500k<math>\Omega</math></b>
<b>0.25mA</b>	<b>10mA/V</b>	<b>0.1k<math>\Omega</math></b>	<b>20k<math>\Omega</math></b>
<b>1mA</b>	<b>40mA/V</b>	<b>0.025k<math>\Omega</math></b>	<b>5k<math>\Omega</math></b>

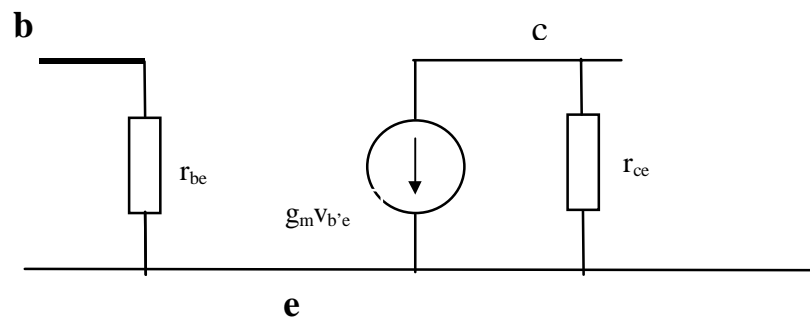2. Why is the small-signal equivalent circuit of a battery (d.c. voltage source) taken to be a short circuit?
3. What would be the small signal equivalent circuit of an ideal current source?
4. What are the equivalent circuit parameters for a transistor whose  $\beta_o = 200$  and whose Early voltage is 150V when it is operating at  $I_C = 0.1mA$  and  $V_{CE} = 5V$ ?



$$g_m = 40I_C \quad r_{ce} = \frac{V_A + V_{CE}}{I_C} \quad r_{be} = \beta_o / g_m$$

$$\mathbf{4 \text{ mA/V}}$$

$$\mathbf{1.55M\Omega}$$

$$\mathbf{50k\Omega}$$

5. Calculate the values of  $I_C$ ,  $I_E$  and  $I_B$  of a transistor in the common emitter configuration, when  $V_{CE} = 8V$  and  $V_{BE} = 0.63V$ ; given that  $I_S = 10^{-13} A$  at  $V_{CE} = 5V$ ,  $\beta = 200$  and  $V_A = 150V$ .

$$I_C = I_{CO} \left[ 1 + \frac{V_{CE}}{V_A} \right] \quad \text{Where} \quad I_{CO} = I_S \exp \left( \frac{V_{BE}}{V_T} \right)$$

$$\text{so when } V_{BE} = 0.63V, I_S = 10^{-13} A;$$

$$\mathbf{I_{CO} \sim 9mA}$$

$$(\text{note that } I_C \text{ at } V_{CE} = 5V \text{ is given by } I_C = 9mA \left[ 1 + \frac{5}{150} \right] = 9.1 \text{ mA})$$


**We need to find  $I_C$ ,  $I_B$  and  $I_E$  at  $V_{CE} = 8V$**

- we're on the same  $V_{BE}$  characteristic so  $I_{CO}$  is the same.

$$\text{Therefore } I_C = 9mA \left[ 1 + \frac{8}{150} \right] \sim \mathbf{9.3 \text{ mA}}$$

$$\beta = \frac{I_C}{I_B} = 200 \quad \text{so} \quad I_B \sim 50 \mu\text{A}$$
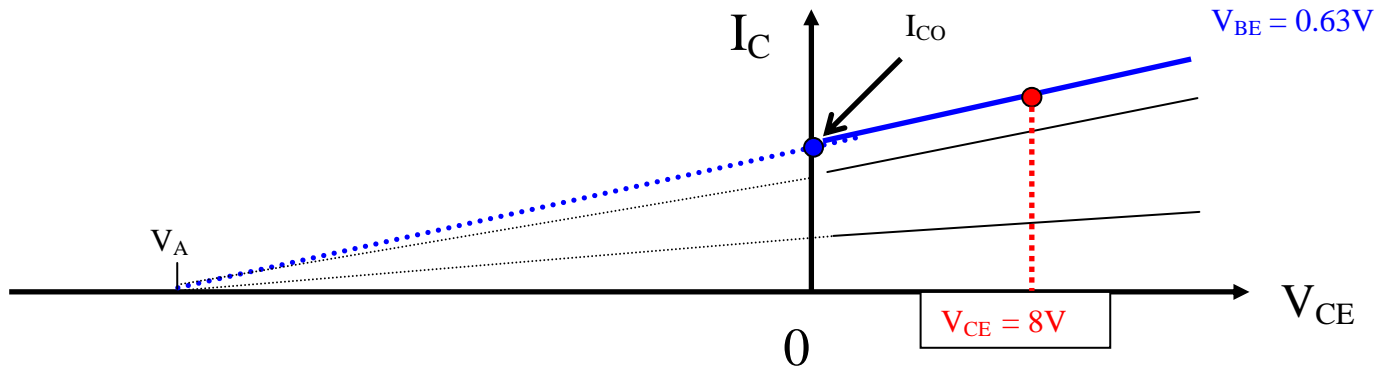
$$I_E = I_C + I_B \quad \text{so} \quad I_E \sim 9.35 \text{ mA}$$



6. What is the output resistance of the transistor at the operating point in 5 above?

**Operating point is  $V_{CE} = 8\text{V}$ ,  $I_C = 9.3\text{mA}$**

**So**

$$r_{ce} = \frac{V_A + V_{CE}}{I_C}$$

$$r_{ce} = \frac{150 + 8}{9.3 \cdot 10^{-3}} = 17 \text{ k}\Omega$$

**or**

$$r_{ce} = \frac{V_A}{I_{CO}}$$

$$r_{ce} = \frac{150}{9 \cdot 10^{-3}} = 17 \text{ k}\Omega$$